



# Gateway Classes

**Semester -I & II****Common to All Branches****BEE101/201: FUNDAMENTALS OF ELECTRICAL ENGG.****UNIT-2 ONE SHOT : Steady State Analysis**

## Gateway Series for Engineering

- Topic Wise Entire Syllabus**
- Long - Short Questions Covered**
- AKTU PYQs Covered**
- DPP**
- Result Oriented Content**

**For Full Courses including Video Lectures**



# Gateway Classes



**BEE101 / BEE201: FUNDAMENTALS OF ELECTRICAL ENGINEERING**

## **Unit-2**

### **Introduction to Steady State Analysis**

### **Syllabus**

**Representation of Sinusoidal waveforms – Average and effective values, Form and peak factors. Analysis of single phase AC Circuits consisting R-L-C combination (Series and Parallel) Apparent, active & reactive power, Power factor. Concept of Resonance in series & parallel circuits, bandwidth and quality factor. Three phase balanced circuits, voltage and current relations in star and delta connections.**



**Download App**

**For Full Courses including Video Lectures**





# AKTU

## Electrical Engg

# One Shot


## UNIT - II



- **Unit-2: (Steady State Analysis of Single Phase AC Circuits)**

- Representation of Sinusoidal waveforms – Average and effective values, Form and peak factors.
- Analysis of single phase AC Circuits consisting R-L-C combination (Series and Parallel) Apparent, active & reactive power, Power factor. Concept of Resonance in series & parallel circuits, bandwidth and quality factor.
- Three phase balanced circuits, voltage and current relations in star and delta connections.

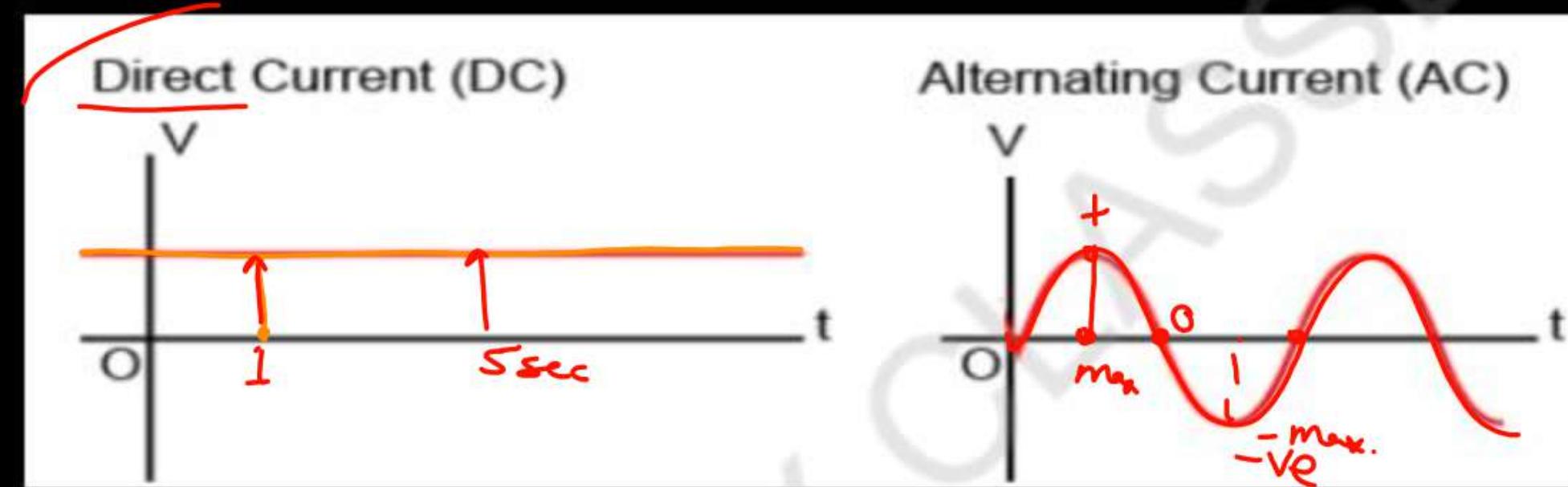**Direct Current (D.C.) Supply:-** A DC power supply is one that provides a constant magnitude and direction with respect to time.



**Alternating Current (A.C.) Supply:-** Alternating supply is one whose magnitude and direction changes periodically with time.

#### *Advantage of AC over DC*

1. *Varying voltage level of AC by using transformer.*
2. *More Economical than DC*
3. *Generation of high voltage AC is much easier & Cheaper than DC*
4. *AC can be easily converted to DC.*
5. *AC machine are more simple in construction and requires less maintenance*

## Why We should use Pure Sine Wave ?

2 marks

- Easy to write equation for pure sine wave.
- Any other wave form can be obtained by a series of sine or cosine wave form.
- Sine or cosine wave can pass through linear circuit without any distortion.
- Analysis of electrical networks with sine inputs is very easy.

## Alternating Quantity

**Equation of Alternating Quantity (AKTU-2002-03):-**

For a pure sine wave

$$I = I_m \sin \omega t$$

*instantaneous  
Equation*

$$V = V_m \sin \omega t$$

*Max. Value*      *Angular freq.*


**Important Terms related to Alternating Quantity -**

Instantaneous Value:- Value of alternating quantity at any instant of time.

Waveform Cycle:- Each repetition of positive and negative instantaneous values of the AC Quantity.

Time period:- Time taken to complete one cycle.

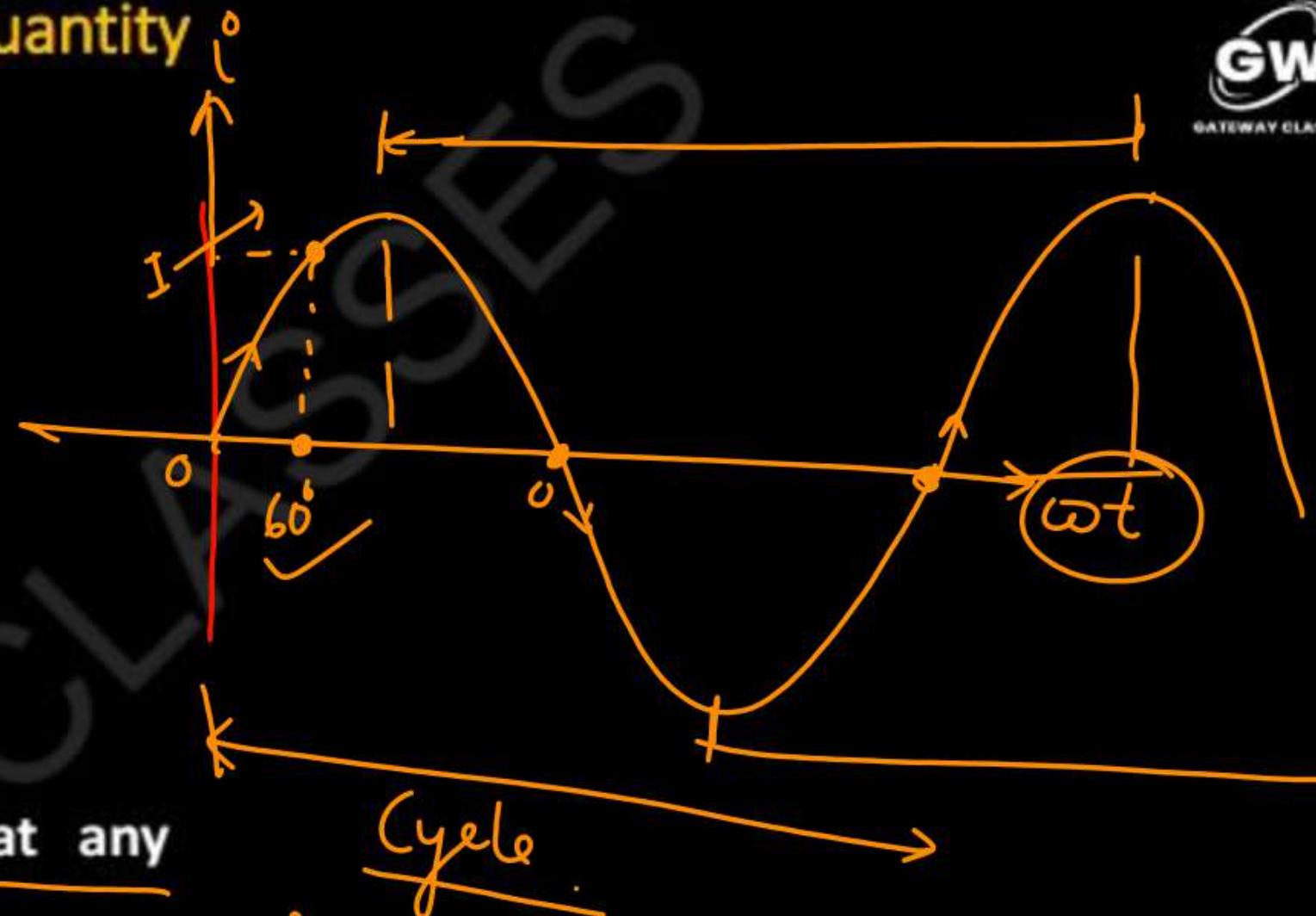Frequency:- Reciprocal of Time period or no of cycle in a second.



frequency = No. of Cycle / sec

## Alternating Quantity


- **Amplitude**:- Maximum value attained by AC quantity during positive and negative cycle.

- **Angular Frequency**:- Frequency expressed in radian /sec.

$$\omega = 2\pi f$$

- **Peak to Peak Value**:- Value of AC quantity from positive maximum value to negative maximum Value.
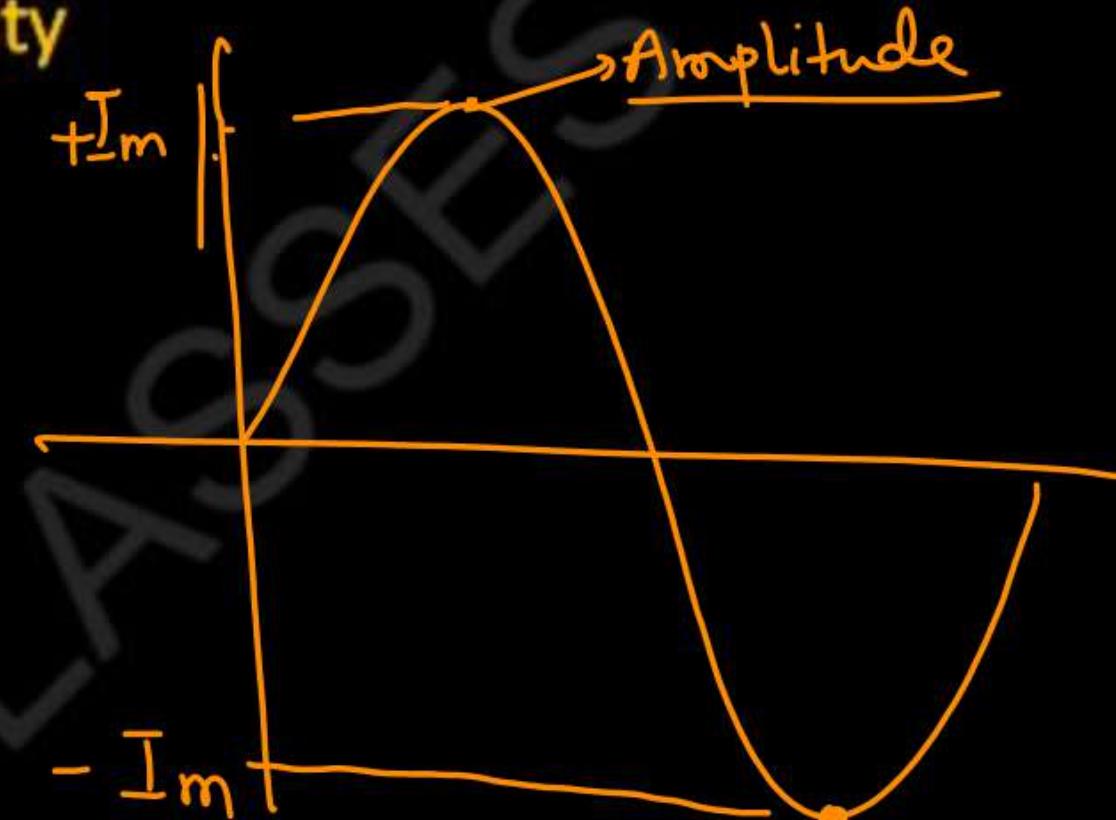
$$\text{Amplitude} = \frac{\text{Peak to Peak Value}}{2}$$



$$P.P = 2I_m$$

$$\text{Amplitude } I_m = \frac{P.P}{2}$$

## Examples of Alternating Quantity

Ex-1 A sinusoidally varying alternating current of frequency 60 Hz has a maximum value of 15 amp.

(i) Write equation for instantaneous value, Find the value of current after 1/200 second

(ii) Find the time to reach 10 amperes for the first time?

(AKTU-2002-03)

Sol |  $f = 60 \text{ Hz}$ ,  $I_m = 15 \text{ amp}$  (i),  $i^\circ = 10 \text{ amp}$ ,  $t = ?$

$$\omega = 2\pi f = 2\pi \times 60 = 120\pi$$

(i)  $i^\circ = I_m \sin \omega t$

$$i^\circ = 15 \sin(120\pi)t$$

Put  $t = \frac{1}{200} \text{ s}$

$$i^\circ = 15 \sin(120\pi \cdot \frac{1}{200}) \\ = 14.26 \text{ amp}$$

$$10 = 15 \sin 120\pi t$$

$$\left(\frac{10}{15}\right) = \sin 120\pi t$$

$$120\pi t = \sin^{-1}\left(\frac{10}{15}\right)$$

$$t = \frac{\sin^{-1}\left(\frac{10}{15}\right)}{120\pi} = 1.93 \text{ ms. Ans.}$$

## Examples of Alternating Quantity

2 marks

Ex-2 The equation of an alternating current is  $i = 42.42 \sin 628t$  Determine Maximum Value, Frequency, rms value, average value, form factor (AKTU-2017-18, similar question in 2002-03, 2003-4, 2005-06, 2007-08)

Sol.-

$$i = 42.42 \sin 628t$$
$$i = I_m \sin \omega t$$

$$I_m = 42.42 \text{ amp}$$

$$\omega = 628 = 2\pi f$$

$$f = \frac{628}{2\pi} = 100 \text{ Hz}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{42.42}{\sqrt{2}} =$$

Pending


$$I_{av} = \frac{2I_m}{\pi} :$$

## Average Value (Mean Value)


The average of all the instantaneous values of an alternating voltage and currents over one complete cycle is called **Average Value**.

Or

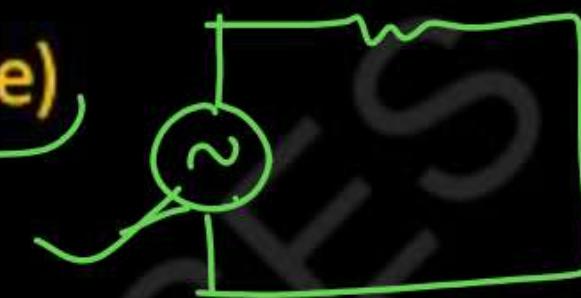The Average Value (also known as Mean Value) of an Alternating Current (AC) is expressed by that Direct Current (DC) which transfers across any circuit the same amount of charge as is transferred by that Alternating Current (AC) during the same time




q charge

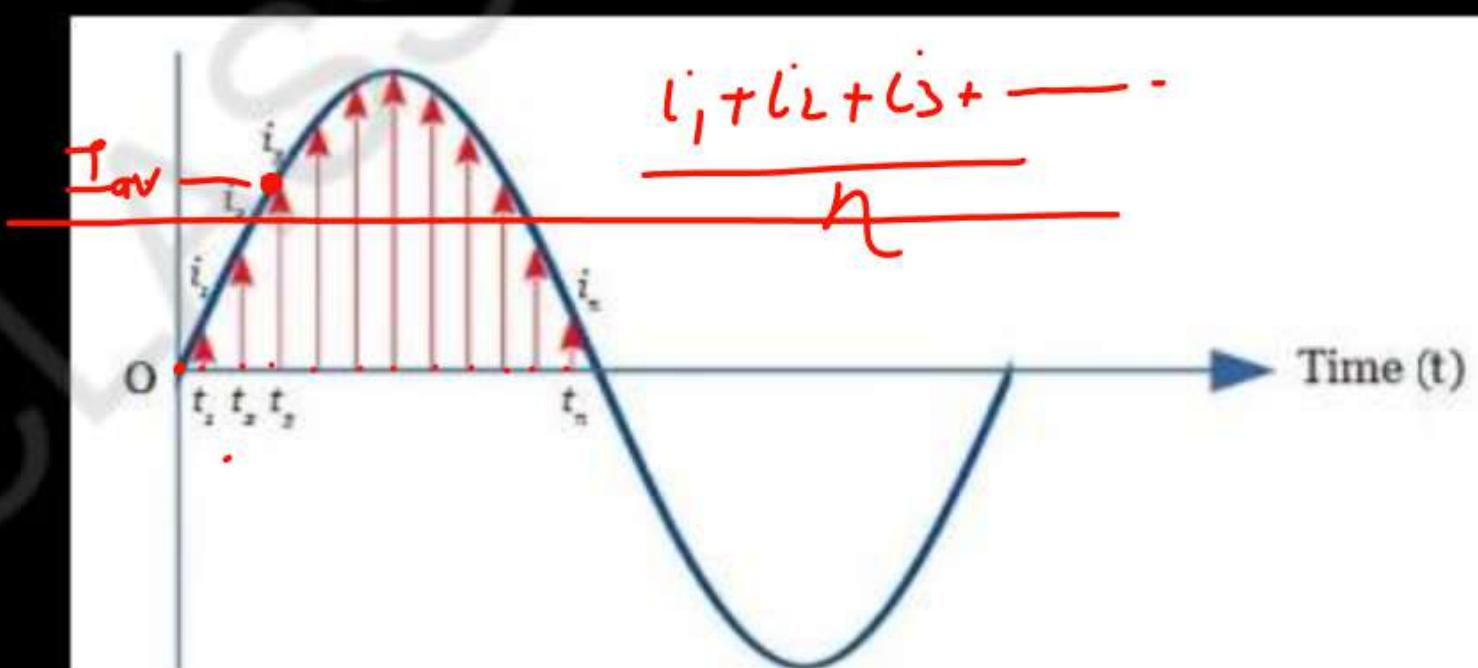

Average Value by Graphical Method:-

$$\text{Average value} = \frac{\text{Sum of all instantaneous values over one cycle}}{\text{Number of instants}}$$
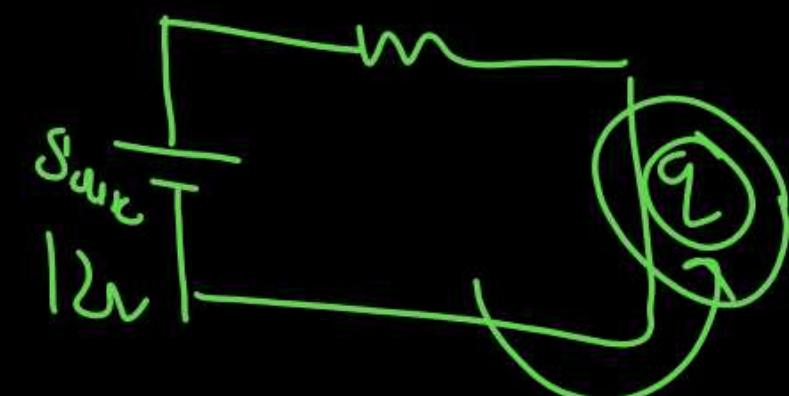
$$I_{AV} = \frac{i_1 + i_2 + i_3 + \dots + i_n}{n}$$



## Average Value (Mean Value)

Average Value by Analytical Method:-

$$I_{av} = \frac{\text{Area under the curve for half cycle}}{\text{Length of base over half cycle}}$$


$$i = I_m \sin \theta$$

$$I_{av} = \frac{\int_0^{\pi} i d\theta}{\pi} = \frac{1}{\pi} \int_0^{\pi} I_m \sin \theta d\theta$$

$$= \frac{I_m}{\pi} \int_0^{\pi} \sin \theta d\theta = \frac{I_m}{\pi} \left[ -\cos \theta \right]_0^{\pi}$$

$$= -\frac{I_m}{\pi} \left[ -\cos \pi + \cos 0 \right]$$

$$= \boxed{\frac{2I_m}{\pi} = I_{av}}$$

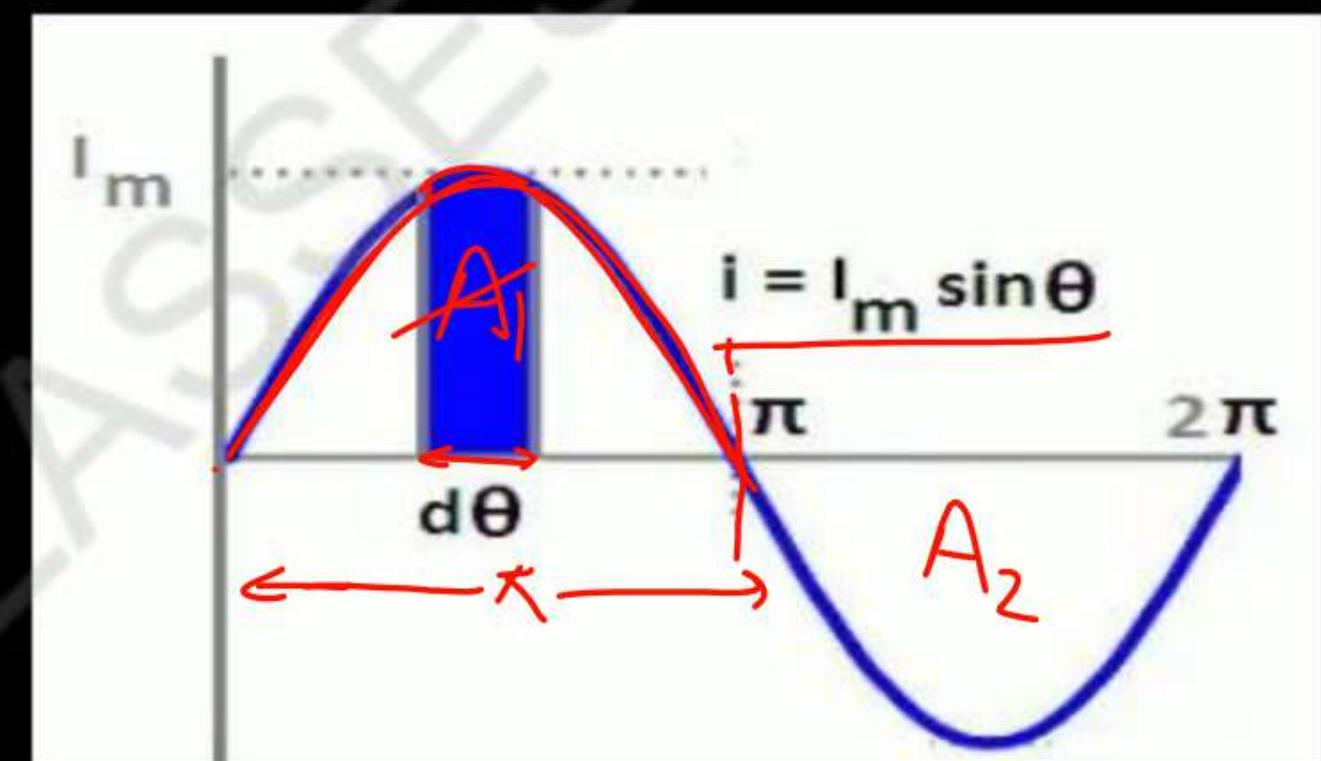


Root Mean Square (R.M.S.) Value/ Effective Value

③    ②    ①

Definition: The RMS value of AC current is equal to that amount of DC current which produces the same heating effect flowing through the same resistance for the same time.

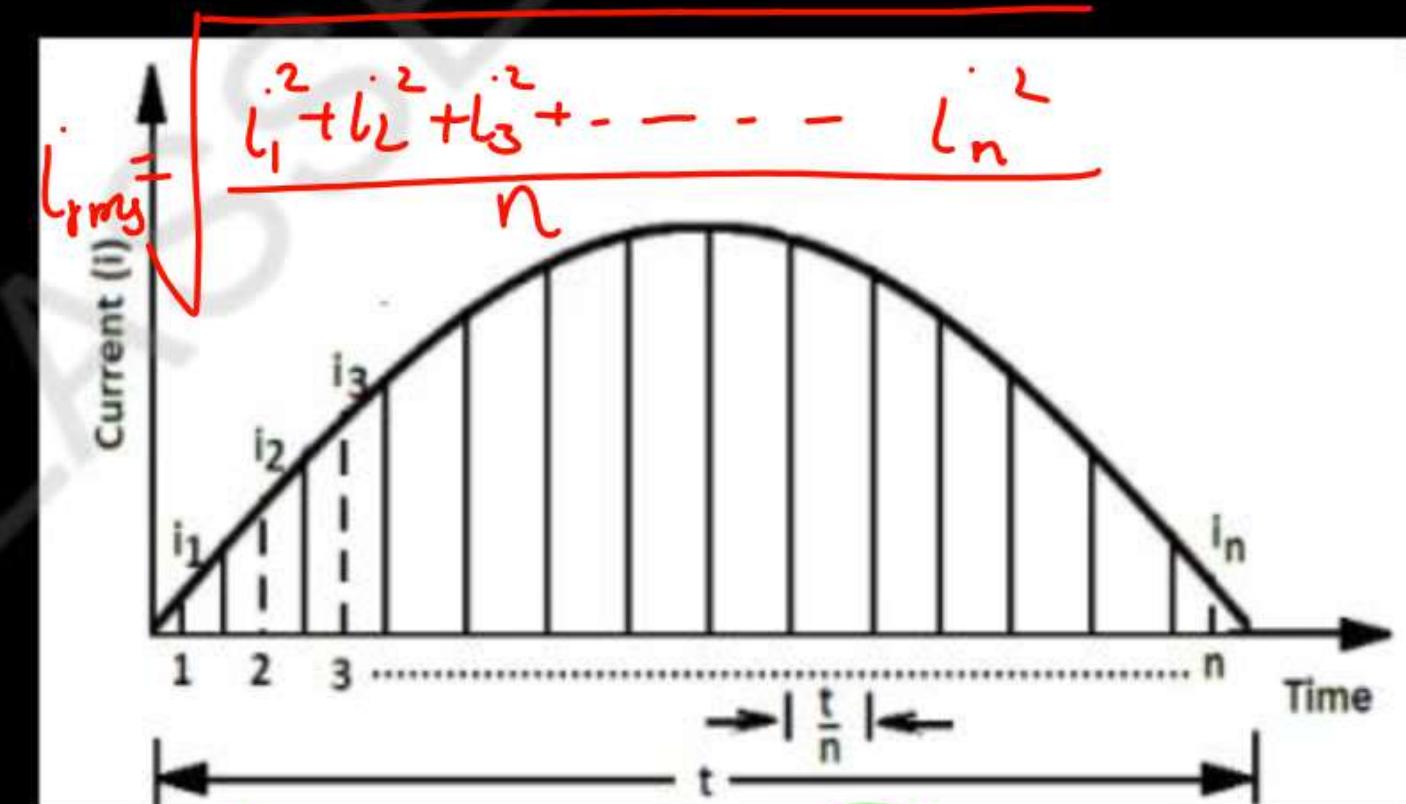For example, if 3A (RMS) AC current is flowing through a circuit, And it will produce the same amount of heat (energy) as will be produced by 3A DC current.



$$\begin{aligned} \text{RMS value of alternating current } (I) &= \sqrt{\text{mean value of } i^2} \\ &= \sqrt{\frac{i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2}{n}} \end{aligned}$$



# Root Mean Square (R.M.S.) Value/ Effective Value

**Analytical Method:-**

$$I_{RMS} = \sqrt{\frac{\text{Area of half cycle squared wave}}{\text{base length of half cycle}}}$$

$$i = I_m \sin \theta$$

$$i^2 = I_m^2 \sin^2 \theta$$


$$I_{RMS} = \sqrt{\int_0^{\pi} I_m^2 \sin^2 \theta d\theta}$$

$$\begin{aligned} I_{RMS}^2 &= \frac{I_m^2}{\pi} \int_0^{\pi} \sin^2 \theta d\theta = \frac{I_m^2}{\pi} \int_0^{\pi} \frac{1 - \cos 2\theta}{2} d\theta \\ &= \frac{I_m^2}{2\pi} \int_0^{\pi} (1 - \cos 2\theta) d\theta \end{aligned}$$

$$\begin{aligned} I_{RMS}^2 &= \frac{I_m^2}{2\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_0^{\pi} \\ &= \frac{I_m^2}{2\pi} \left[ \pi \right] \left[ \frac{\sin 2\pi}{2} - 0 + \frac{\sin 0}{2} \right] \end{aligned}$$

$$I_{RMS}^2 = \frac{I_m^2}{2\pi} \cancel{\pi} = \frac{I_m^2}{2}$$

$$I_{RMS} = \frac{I_m}{\sqrt{2}}$$

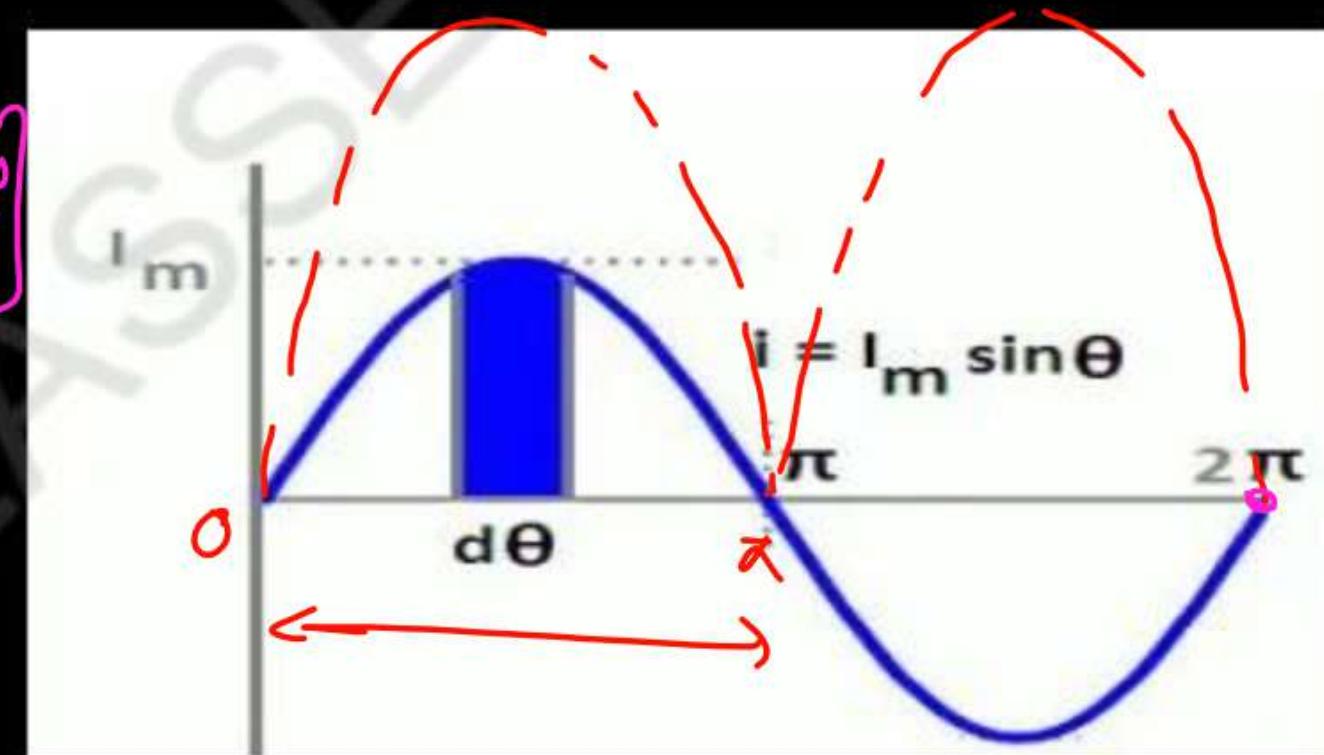

$$I_{RMS} = 0.707 I_m$$

$$= 70.7 \% I_m$$

- **Form Factor:-** The ratio of the root mean square value to the average value of an alternating quantity (current or voltage) is called **Form Factor**.

$$\text{Form Factor} = \frac{\checkmark I_{\text{r.m.s}}}{I_{\text{av}}} \text{ or } \frac{E_{\text{r.m.s}}}{E_{\text{av}}}$$

For a sine wave,

$$\text{form factor : } \frac{I_m/\sqrt{2}}{2I_m/\pi} = 1.11$$

**Peak Factor/ Crest Factor :-** Peak Factor is defined as the ratio of maximum value to the R.M.S value of an alternating quantity.

$$K_p = \underline{\text{Peak value / RMS value}}$$

For a sine Wave

$$\text{Peak factor} = \frac{I_m}{\underline{I_m/\sqrt{2}}} = \sqrt{2} A_p$$

**Ex-3 Determine Form Factor and Peak Factor for Full wave rectified Signal ( $V_m = 10\text{volt}$ ) ? (AKTU- 2002-03)**

$$v = V_m \sin \theta$$

$$v = 10 \sin \theta$$

$$V_{av} = \frac{1}{\pi} \int_0^{\pi} 10 \sin \theta d\theta$$


$$= \frac{10}{\pi} \left[ -\cos \theta \right]_0^{\pi} = \frac{10}{\pi} \left[ -(\cos \pi + \cos 0) \right]$$

$$= \frac{10}{\pi} \cdot 2 = \boxed{\frac{20}{\pi} = V_{av}}$$

$$\sqrt{V_{rms}^2} = \frac{1}{\pi} \int_0^{\pi} 10 \sin^2 \theta d\theta$$

$$= \frac{100}{2\pi} \int_0^{\pi} (1 - \cos 2\theta) d\theta = \frac{100}{2\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_0^{\pi}$$

$$0 \longleftrightarrow \pi$$

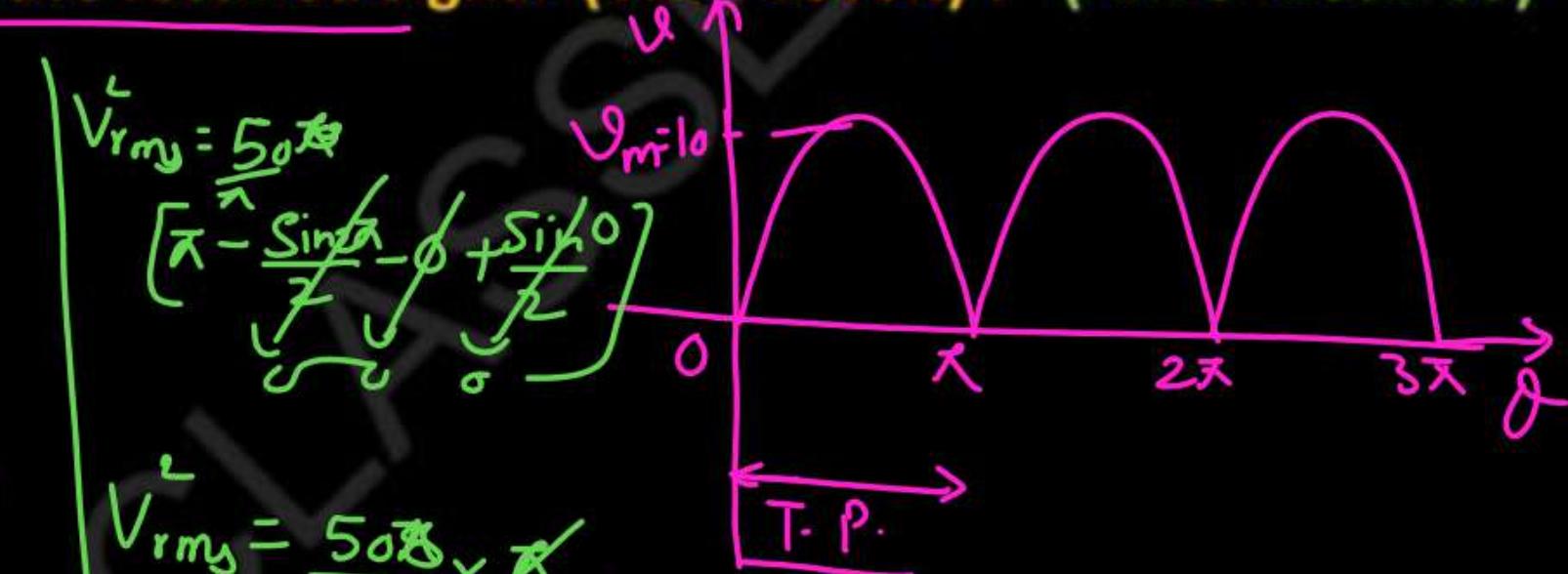

$$F.F = \frac{V_{av}}{V_{rms}} = \frac{20/\pi}{\sqrt{50}} = \boxed{1.11}$$


$$P.F = \frac{V_m}{V_{rms}}$$

Ex-4 Determine Form Factor and Peak Factor for Half wave rectified Signal (  $V_m = 10\text{volt}$  ) ? (AKTU- 2003-04, 2020-21)

$$v = V_m \sin \theta \quad 0 - \pi$$

$$V = \bigcirc \quad \pi - 2\pi$$
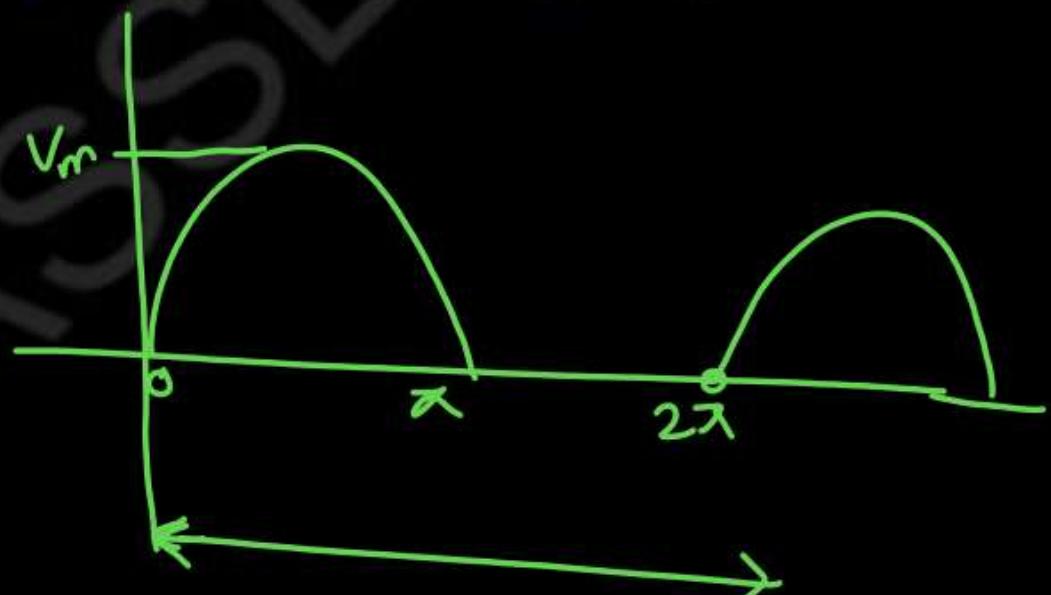
$$\begin{aligned} V_{av} &= \int_0^{2\pi} v d\theta \\ &= \frac{\left[ \int_0^{\pi} V_m \sin \theta d\theta + \int_{\pi}^{2\pi} 0 d\theta \right]}{2\pi} \end{aligned}$$



$$f.f = 1.57$$

$$P.F = 2$$

Ex-5 Determine Form Factor and Peak Factor for the given Signal ? (AKTU- 2004-05, 2017-18)

$$\text{Sol}^h \quad y = mx + c$$

$$V = 10t + 0$$

$$V = 10t$$

for (1-2 sec)

$$V = -10t + C$$

$$at t=2, V=0$$

$$0 = -10 \times 2 + C$$

$$C = 20$$

$$\boxed{V = -10t + 20}$$


$$1 > t > 0$$

$$\left| \begin{array}{l} V_{AV} = \frac{1}{2} \int_0^2 V \cdot dt \\ = \frac{1}{2} \left[ \int_0^1 10t \cdot dt + \int_1^2 (-10t + 20) dt \right] \\ = \frac{1}{2} \left[ \frac{1}{2} \times 10 \times 1 + \frac{1}{2} \times 10 \times 1 \right] = 5 \text{ volt.} \end{array} \right.$$

$$\left| \begin{array}{l} V_{RMS}^2 = \frac{1}{2} \left[ \int_0^1 (10t)^2 dt + \int_1^2 (-10t + 20)^2 dt \right] \end{array} \right.$$

$$V_{RMS}^2 = \frac{1}{2} \left[ 100 \left[ \frac{t^3}{3} \right]_0^1 + \int_1^2 (100t^2 + 400 - 400t) dt \right]$$
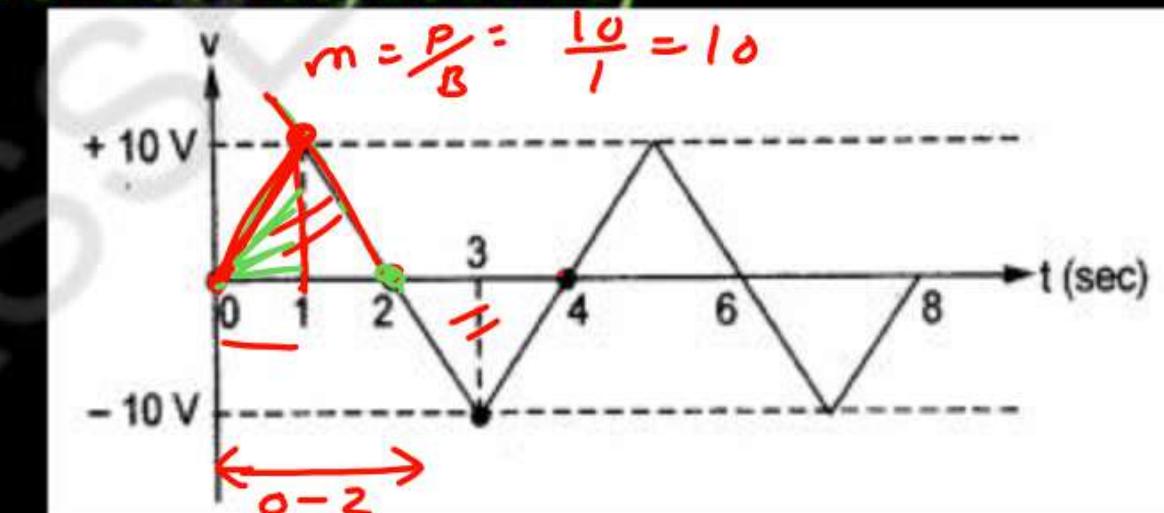
$$V_{RMS}^2 = \frac{1}{2} \left[ 100 \left[ \frac{1}{3} \right] + \left[ 100 \frac{t^3}{3} + 400t - 400t^2 \right]_1^2 \right]$$



$$\left| \begin{array}{l} V_{RMS} = \sqrt{\dots} \\ V_{RMS} = 5\sqrt{7} \text{ Volt} \end{array} \right.$$


Ex-6 Determine Form Factor and Peak Factor for the given Signal ? (AKTU- 2004-05, 2017-18)

$$V = \frac{\omega}{2} t$$

O - 2

$$V = 1 \omega t$$

O - 2


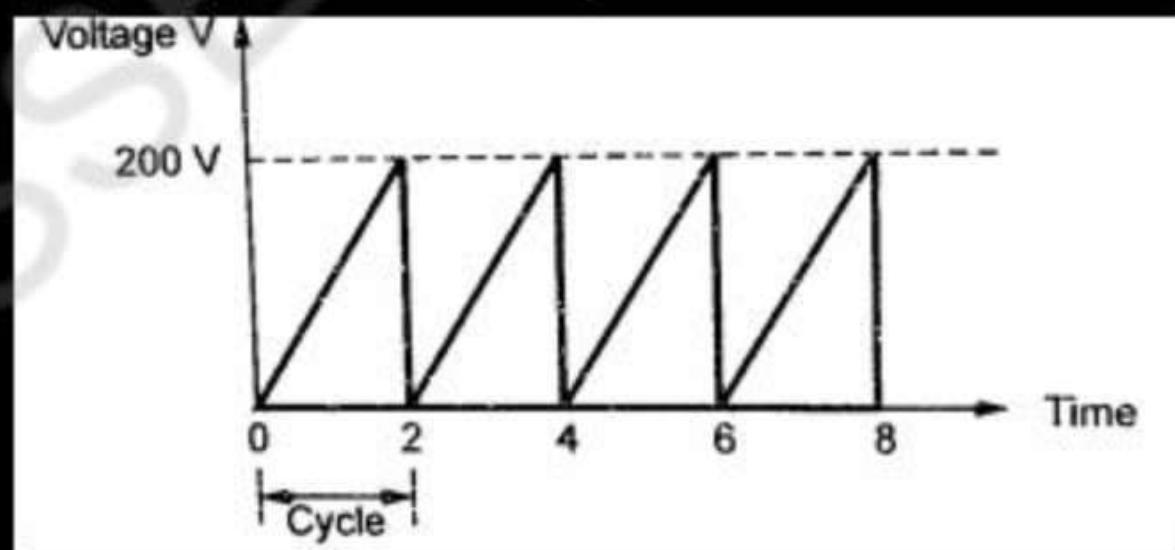


## Concept of Phase and Phase Difference

- **Phase :-** The Phase of an AC quantity is the angle travelled by phasor representing that alternating quantity up to the instant of consideration , measured from reference.

$$i = I_m \sin(\omega t + \phi)$$

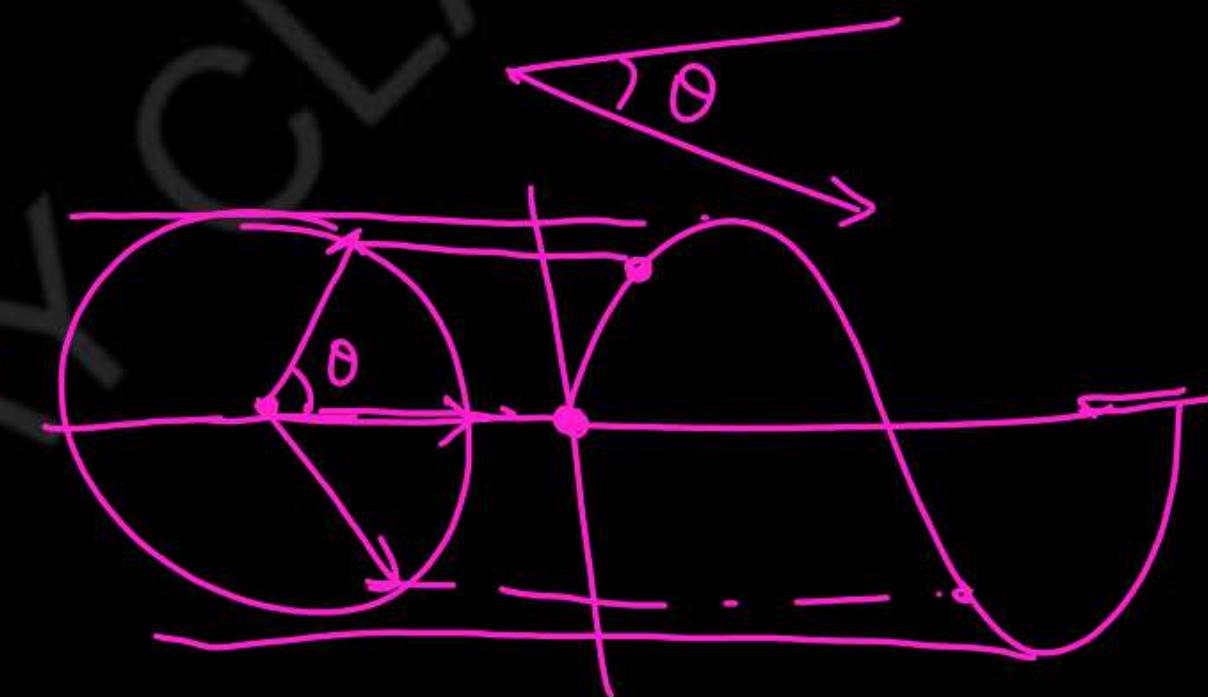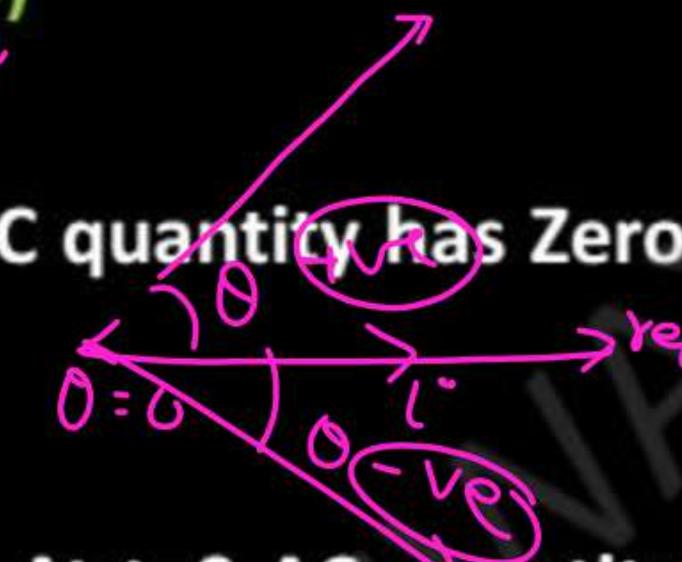
- **when  $\phi = 0$ :** At  $t=0$  AC quantity has Zero instantaneous Value.
- **When  $\phi$  is positive :** At  $t=0$  AC quantity has some positive instantaneous Value.
- **When  $\phi$  is negative :** At  $t=0$  AC quantity has some negative instantaneous Value.


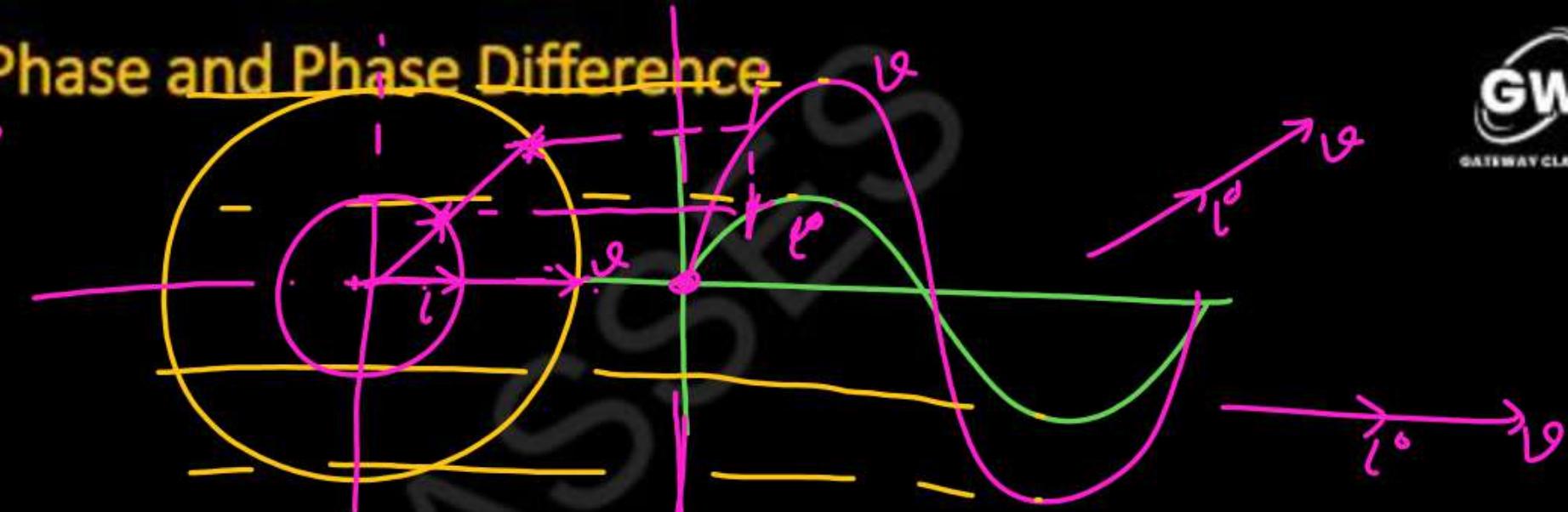
## Concept of Phase and Phase Difference

- **Phase difference :-** The difference between the phase of two Alternating Quantities of same frequency is known as phase difference.


$$\begin{aligned} V &=? \\ \angle &=? \end{aligned}$$



- **Zero Phase difference :-**

$$\begin{aligned} V &= V_m \sin \omega t \\ I &= I_m \sin \omega t \end{aligned}$$

- **Leading Phase Difference :-**

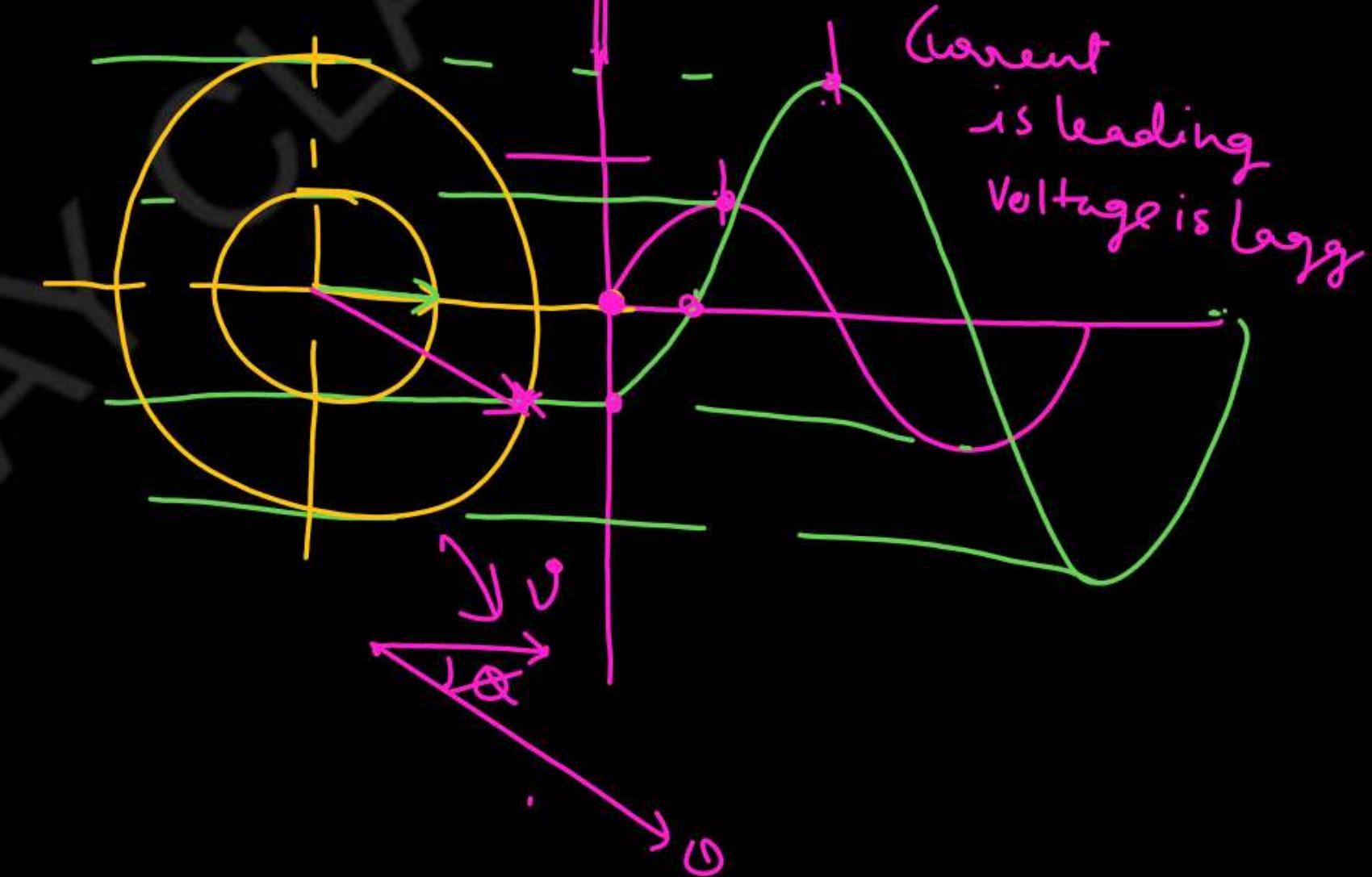

- **Lagging Phase Difference :-**

## Numerical

- Ex-7  $V_1 = 50 \sin \omega t$ ,  $V_2 = 25 \sin(\omega t + 40)$ ,  $V_3 = 40 \cos \omega t$ ,  $V_4 = \sin(\omega t - 45)$ . Find Resultant voltage and phase angle.

$$V_1 = 50 \sin \omega t$$

$$V_2 = 25 \sin(\omega t + 40^\circ)$$

$$V_3 = 40 \cos \omega t = 40 \sin(\omega t + 90^\circ)$$

$$V_4 = 20 \sin(\omega t - 45^\circ)$$

$$V_x = 50 + 25 \cos 90^\circ + 20 \cos 45^\circ = ?$$

$$V_y = 40 + 25 \sin 90^\circ - 20 \sin 45^\circ = ?$$

$$V_{\text{Result}} = \sqrt{V_x^2 + V_y^2} = ?$$

$$\theta = \tan^{-1} \frac{V_y}{V_x}$$




## Concept of Polar & Rectangular System

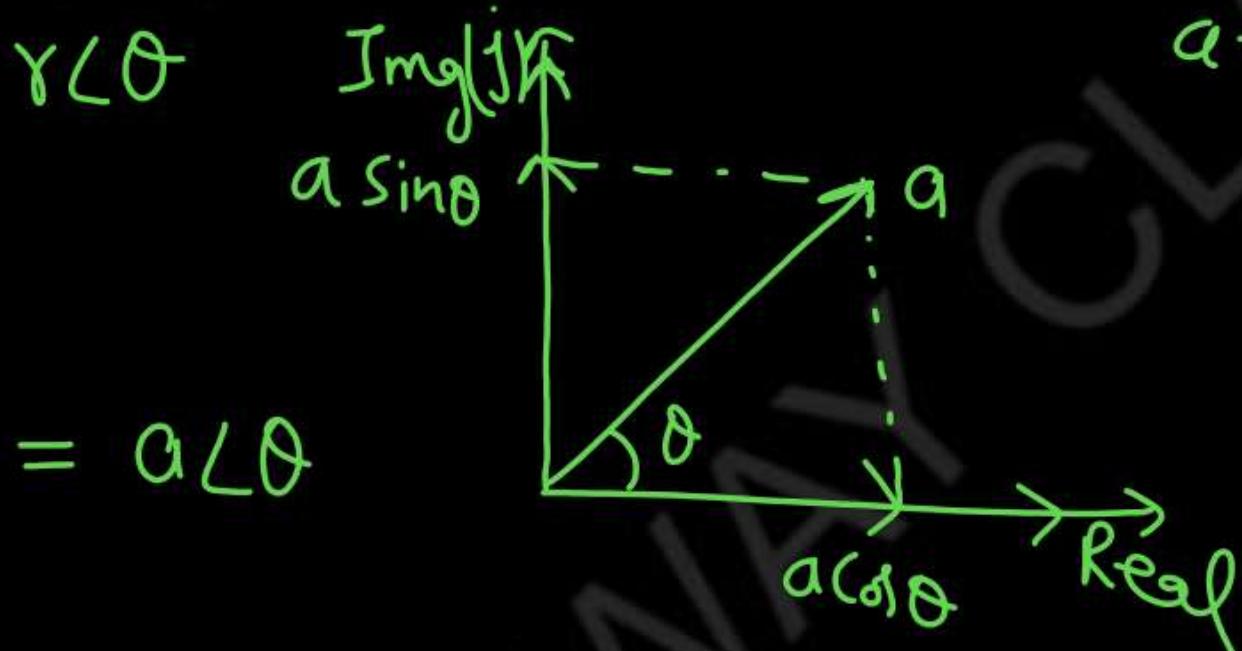**Concept of Polar System:-**

Polar  
 $y < 0$


$$\underline{\text{Polar}} = a \angle \theta$$



Complex

Rectangular  
 $a+ib$
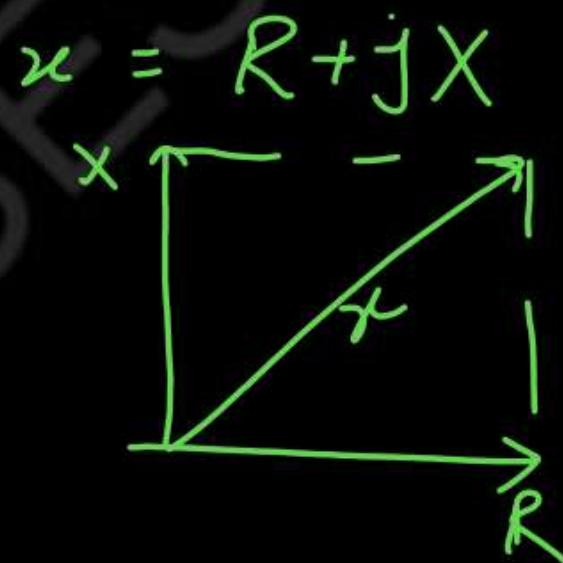
$$\frac{a(\cos \theta + j \sin \theta)}{b + jc}$$




$$x = R + jX$$

## Concept of Polar &amp; Rectangular System

Concept of Rectangular System:-

Mode → Complx.

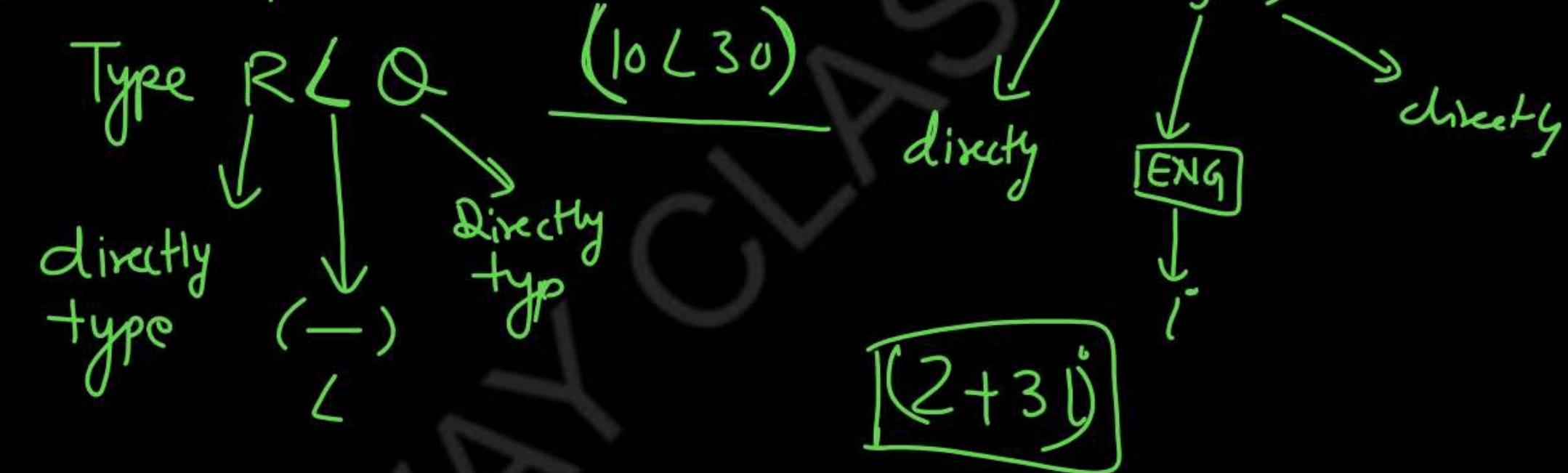

$y(10)$ , at  $i(b)$   
 Shift =

Polar to Rectangular conversion & Vice versa

### Polar to Rectangular conversion

Type

$(2 \angle 60)$  [Shift]  $\rightarrow$   $=$   $\rightarrow$   $=$

$(2 \angle 60)$   $=$   $(a)$   $\downarrow$  Shift  $=$   $b$   $j$   $17.88^\circ$

### Rectangular to Polar conversion

$a$   
 Shift  $\rightarrow$   $=$   
 $b$   $j$

$$(2 \angle 60) \times (3+7j) = \text{Ans}$$

$$\frac{(3+7j)}{(2 \angle 60)}$$

$$3+7j / 2 \angle 60$$

$$(3+7j) \rightarrow \text{Shift} \rightarrow + \rightarrow = - \text{Shift} + =$$

$r = 7.6 \quad \theta = 66.8^\circ$


$$(3+7j) \angle 66.8^\circ$$

# Mathematics of Polar and Rectangular System:-

Ex-8 Two a.c. voltages are represented by  $V_1(t) = 30 \sin(314t + 45^\circ)$  and  $V_2(t) = 60 \sin(314t + 60^\circ)$ . Calculate the resultant Voltage  $v(t)$  and express in the form  $v(t) = V_m \sin(314t + \phi)$ . (AKTU-2003-04)

$$R = ? = V_m$$
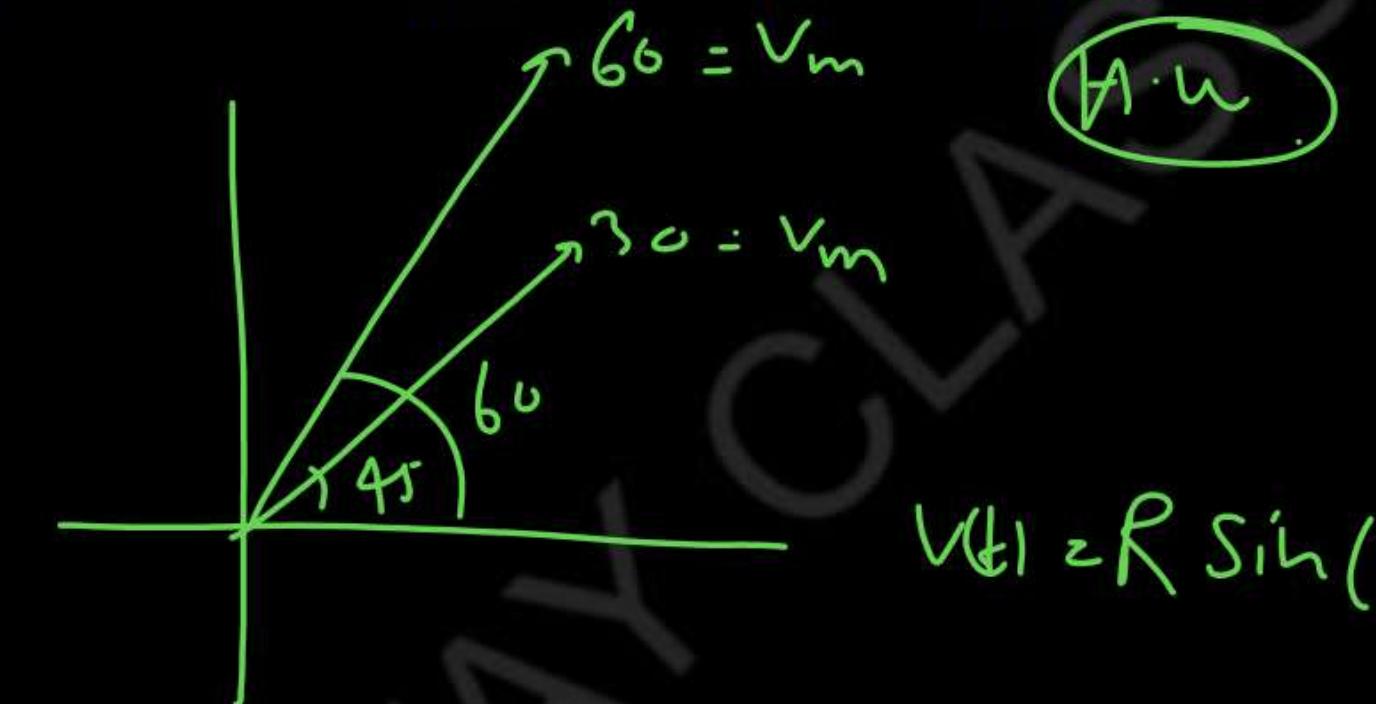
$$\theta = ? = \tan^{-1} \frac{V_2}{V_1}$$



$$v(t) = R \sin(314t + \phi)$$

**Current & Voltage Equations**

**Reactance and Impedance**

**Phase Relationship**

**Power in AC Circuits**

**Waveform Analysis**

## A.C. Through Pure Resistive Circuit

$$\vartheta = V_m \sin \omega t \quad \text{--- ①}$$

$$I^o = \frac{\vartheta}{R} = \frac{V_m \sin \omega t}{R} \quad \left. \begin{array}{l} \text{Compare} \\ i = I_m \sin \omega t \end{array} \right\}$$

$$i^o = I_m \sin \omega t \quad \text{--- ②}$$

$$I_m = \frac{V_m}{R}$$

So Voltage & Current are in same phase.

$$P = V \cdot I$$


$$= V_m \sin \omega t \cdot I_m \sin \omega t$$

$$= V_m I_m \sin^2 \omega t$$

$$= \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

over a complete period its average value is zero
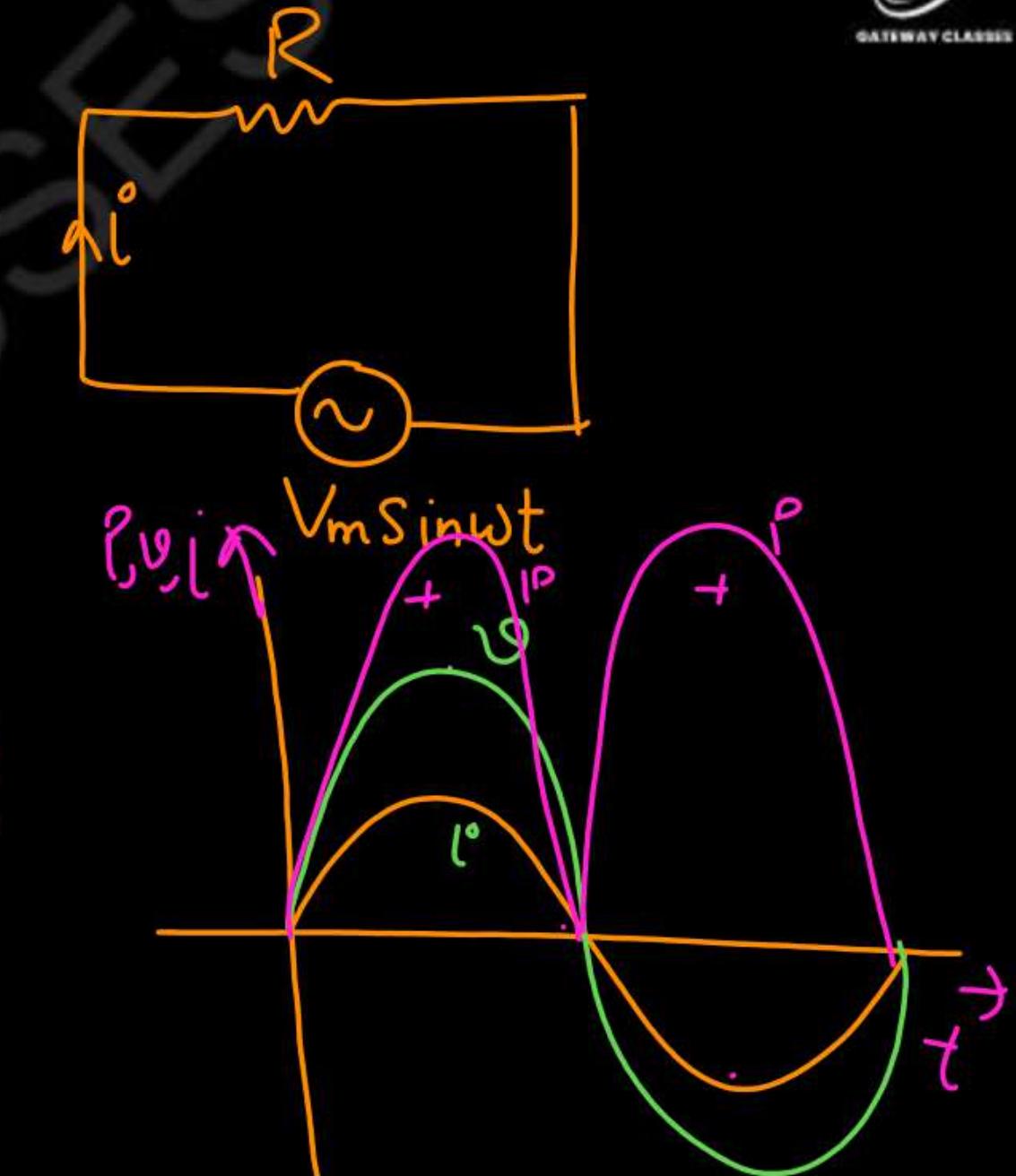
$$\begin{aligned} P &= \frac{V_m I_m}{2} \\ P &= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \\ P &= V_{rms} \cdot I_{rms} \end{aligned}$$



# A.C. Through Pure Inductive Circuit

$$V = V_m \sin \omega t$$

$$e = -L \frac{di}{dt}$$

$$V_L = -e = L \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{V}{L} = \frac{V_m \sin \omega t}{L}$$

$$i^o = \frac{V_m}{L} \int \sin \omega t$$

$$i^o = \frac{V_m}{L} \frac{\cos \omega t}{\omega}$$

$$i^o = \frac{V_m}{\omega L} \sin(\omega t - \frac{\pi}{2})$$

$$i^o = I_m \sin(\omega t - \frac{\pi}{2})$$

$$I_m = \frac{V_m}{\omega L}$$

$$\frac{V_m}{I_m} = \omega L$$

$$X_L = \omega L$$

This is known as  
Inductive Reactance

$$P = V \cdot i^o$$


$$= V_m \sin \omega t \cdot I_m (\cos \omega t)$$

$$P = \frac{V_m I_m}{2} [2 \sin \omega t \cdot \cos \omega t]$$

$$P = \frac{V_m I_m}{2} \sin 2\omega t$$

over a Comp. Cycle

$$P_{avg} = 0$$

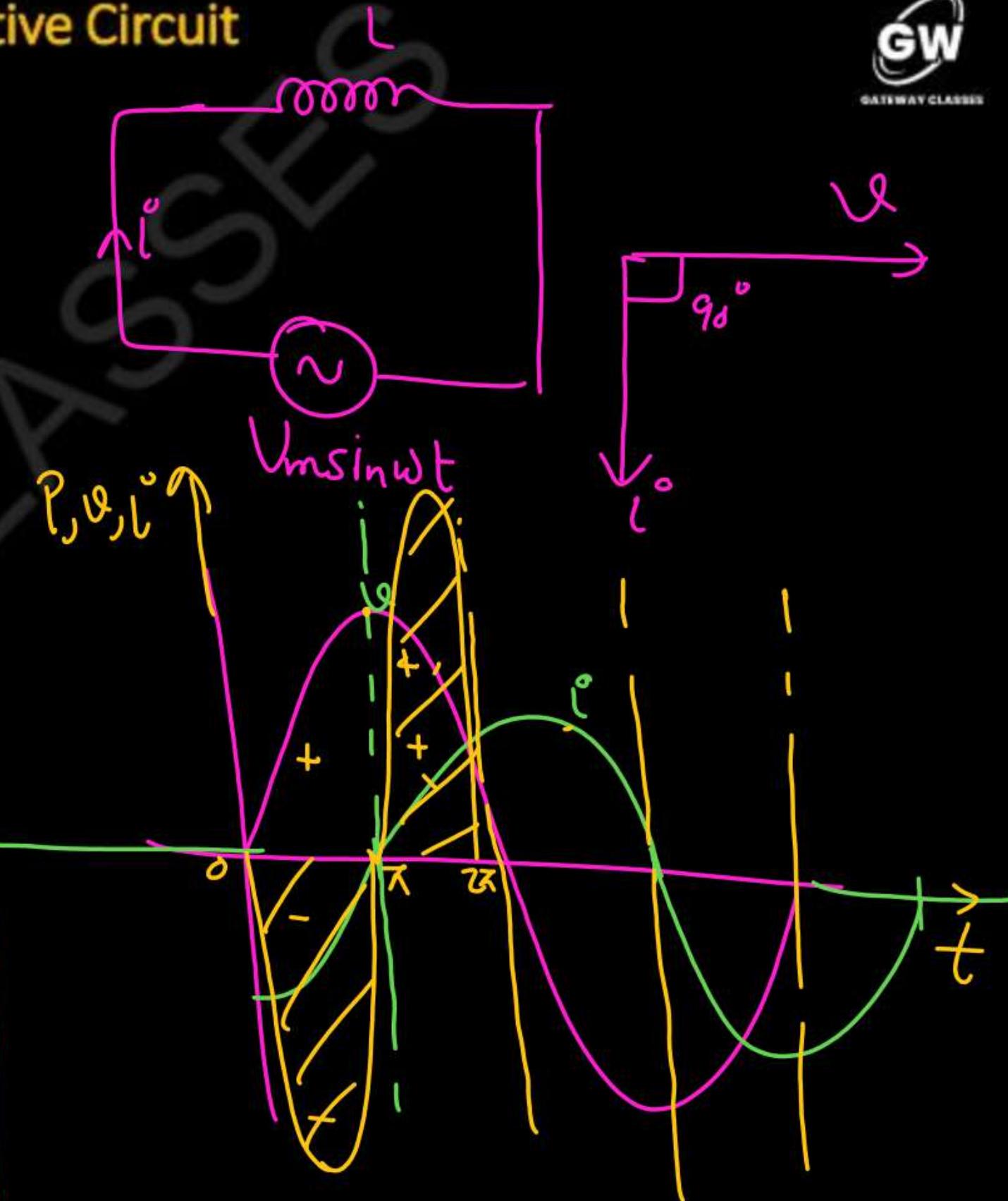

# A.C. Through Pure Capacitive Circuit

$$V = V_m \sin \omega t \quad \text{--- (1)}$$

$$q = C V = C V_m \sin \omega t$$

$$I^o = \frac{dq}{dt} = C V_m (\cos \omega t) \cdot \omega$$

$$I^o = +\omega C V_m \cos \omega t$$

$$I^o = \omega C V_m \sin(\omega t + \frac{\pi}{2})$$

$$I^o = I_m \sin(\omega t + \frac{\pi}{2}) \quad \text{--- (2)}$$

$$I_m = \omega C V_m$$

$$\frac{V_m}{I_m} = \frac{1}{\omega C} = X_C$$

Capacitive Reactance.

Power:



$$P = VI$$

$$= V_m \sin \omega t \cdot I_m \cos \omega t$$

$$P = \frac{V_m I_m}{2} \sin \omega t \cos \omega t$$

$$P = \frac{V_m I_m}{2} \sin \omega t$$

$$P_{avg} = 0$$

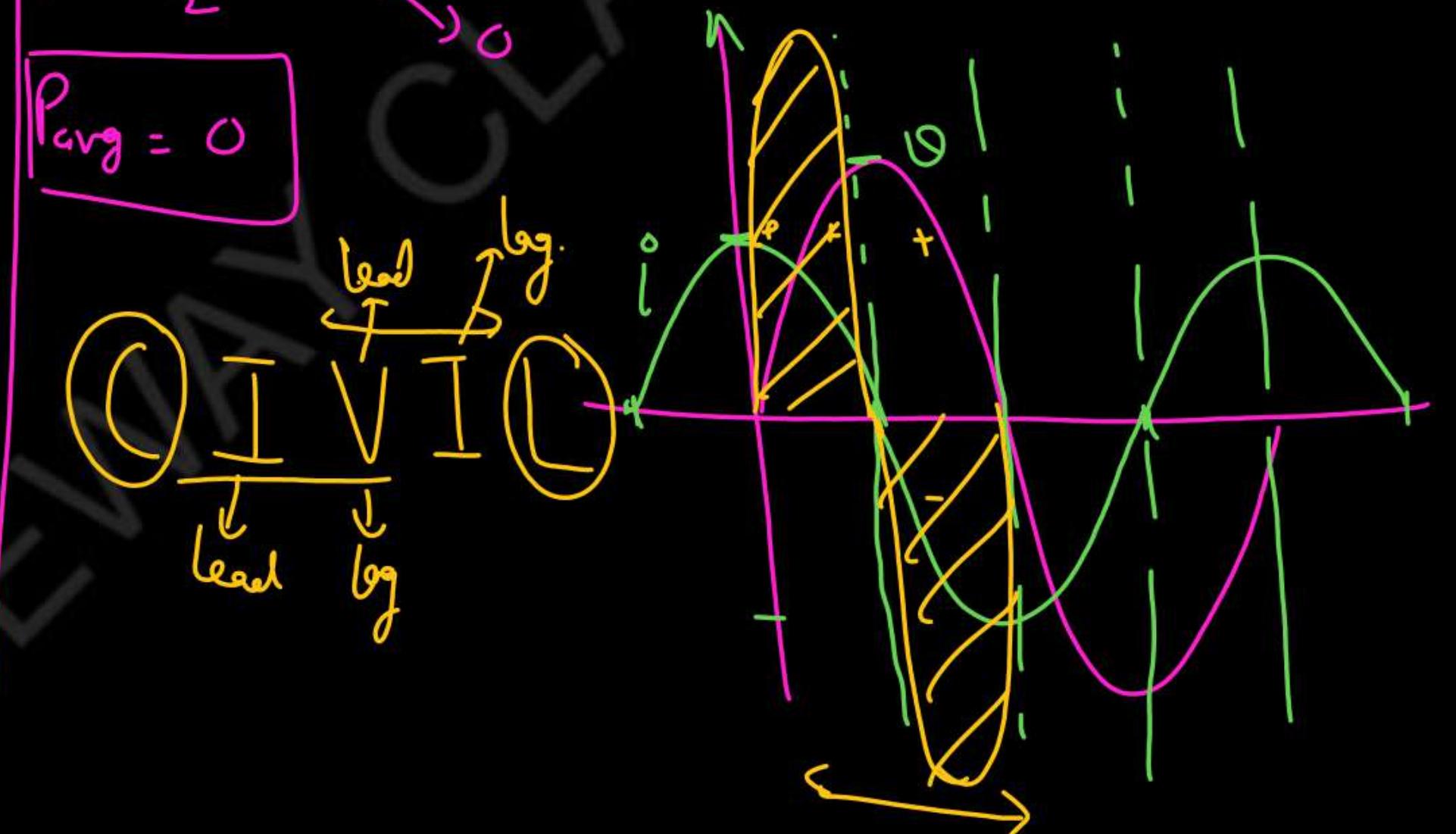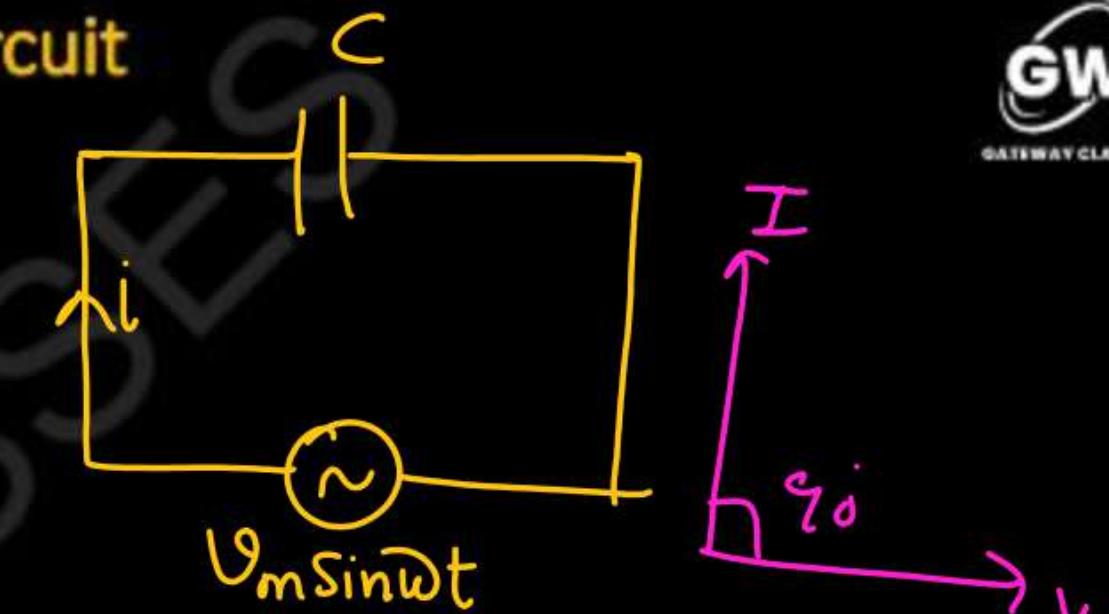

## Concept of Impedance


Impedance = Resistance & Reactance  
Combination

R-L

$$Z = R + jX_L$$

R-C

$$Z = R - jX_C$$

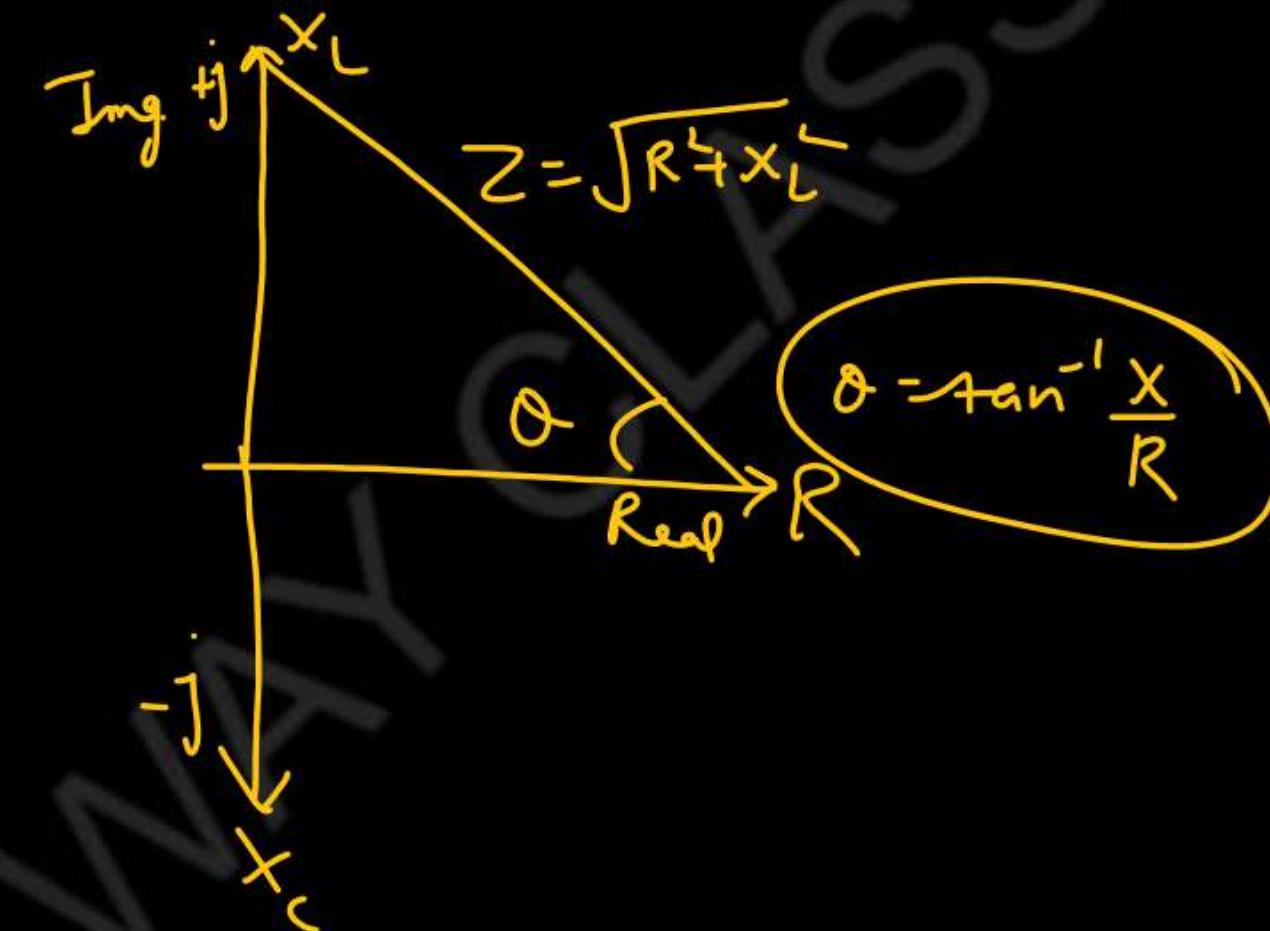

## A.C. Through Series R-L Circuit

$$\vec{V} = \vec{V}_R + \vec{V}_L$$

$$IZ = IR + IX_L$$

$$IZ = \sqrt{(IR)^2 + (IX_L)^2}$$

Imp.

$$\boxed{Z = \sqrt{R^2 + X_L^2}}$$

$$\phi = \tan^{-1} \frac{X_L}{R}$$

$$V = V_m \sin \omega t$$

$$I = I_m \sin(\omega t - \phi)$$

$$P = VI$$




$$= V_m \sin \omega t \cdot I_m \sin(\omega t - \phi)$$

$$= \frac{V_m I_m}{2} [2 \sin \omega t \cdot \sin(\omega t - \phi)]$$

$$= \frac{V_m I_m}{2} [\cos(\omega t - \omega t + \phi) - \cos(\omega t + \omega t - \phi)]$$

$$= \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t - \phi)]$$
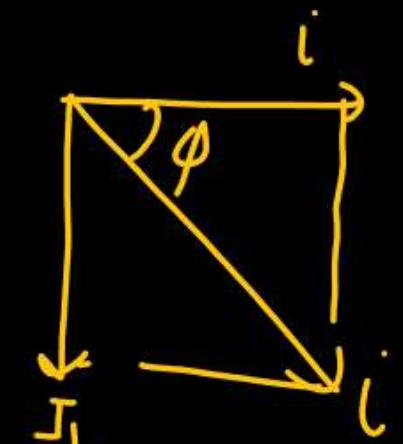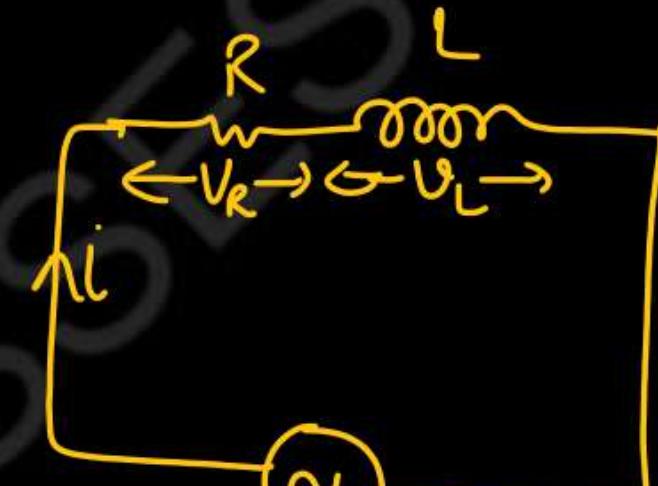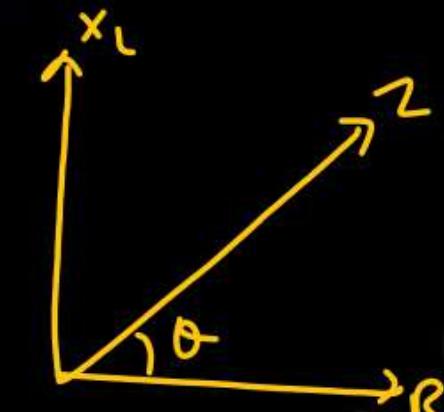
$$\therefore \frac{V_m I_m}{2} \omega \phi = VI_{avg}$$



# A.C. Through Series R-C Circuit

$$\vec{V} = \vec{I}(R + jX_C)$$

$$|Z| = \sqrt{(R^2 + X_C^2)}$$

Imp.  $\boxed{|Z| = \sqrt{R^2 + X_C^2}}$

$$\phi = \tan^{-1}\left(\frac{-X_C}{R}\right)$$

$$\theta = V_m \sin \omega t$$

$$I^o = I_m \sin(\omega t + \phi)$$


$$P = VI^o$$

$$= \frac{V_m I_m}{2} \sin \omega t \cdot \sin(\omega t + \phi)$$



$$= \frac{V_m I_m}{2} \left[ \cos(\omega t - \omega t - \phi) - \cos(\omega t + \omega t + \phi) \right]$$

$$= \frac{V_m I_m}{2} \left[ \cos(-\phi) - \cancel{\cos(2\omega t + \phi)} \right]$$

$\boxed{P = VI \cos \phi}$

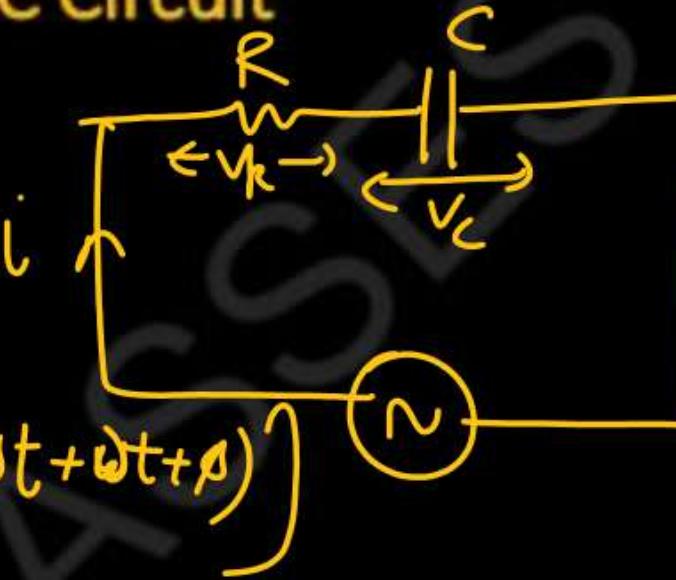

## A.C. Through Series R-L-C Circuit

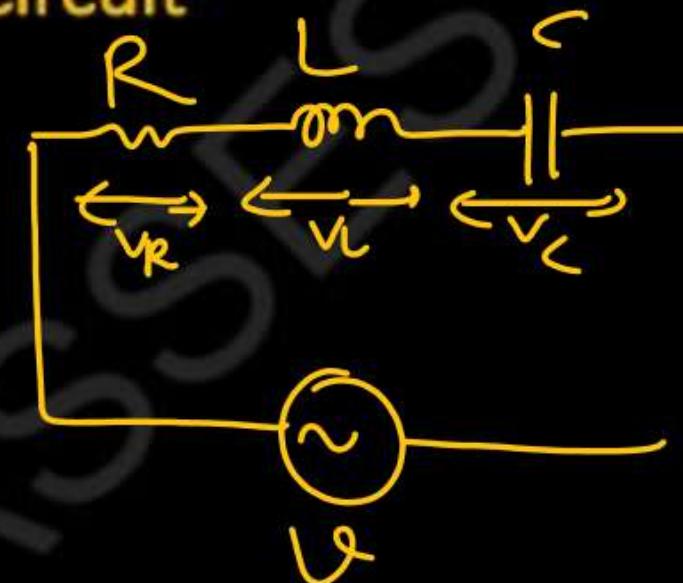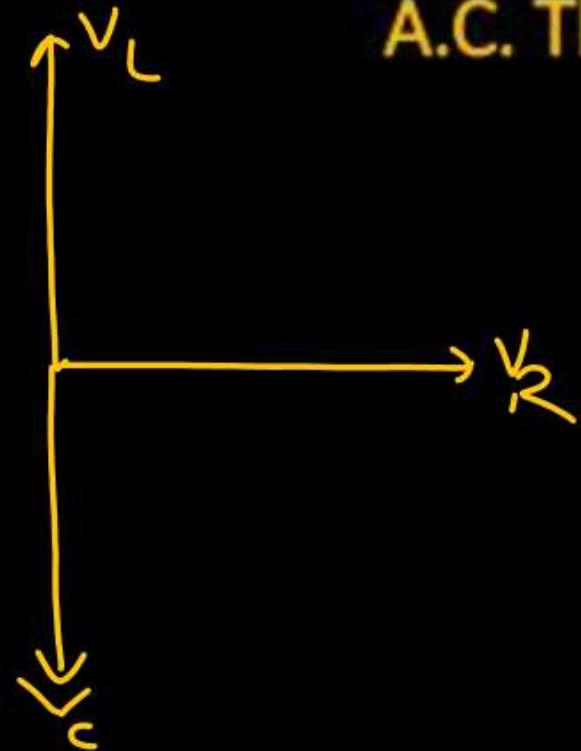

- ①  $V_L > V_C \longrightarrow$  Ind. (R-L)
- ②  $V_C > V_L \longrightarrow$  Capac. (R-C)
- ③  $V_L = V_C \longrightarrow$  Resistive (Pure)


## Concept of Power

## Concept of Power:-

- Apparent Power**:- Apparent Power ( $S$ ) is Product of rms value of Voltage ( $V$ ) and current ( $I$ ).

$$\checkmark S = VI$$

Unit- ~~KW~~  
KVA

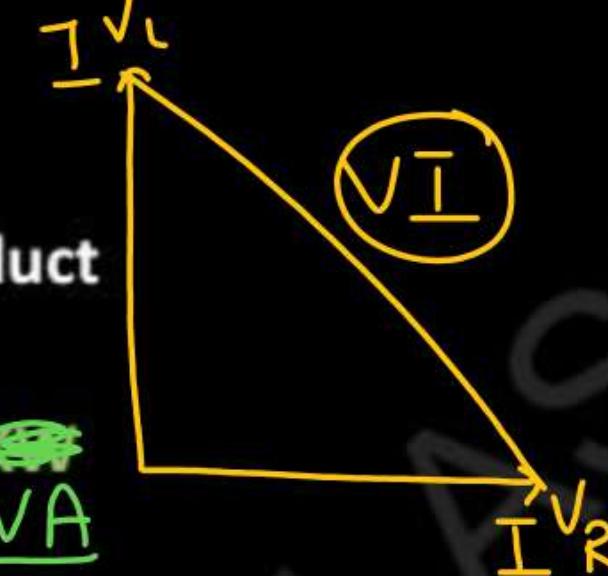

- Active/True Power** :- True Power ( $P$ ) is Product of applied Voltage ( $V$ ) and active component of current ( $I$ ).



$$\boxed{P = VI \cos \phi = S \cos \phi}$$

Unit- ~~KW~~  
kW

- Reactive Power** :- Reactive power ( $Q$ ) is Product of applied Voltage ( $V$ ) and reactive component of current ( $I$ ).

Unit- KVAR

$$P = VI \sin \phi = S \sin \phi$$

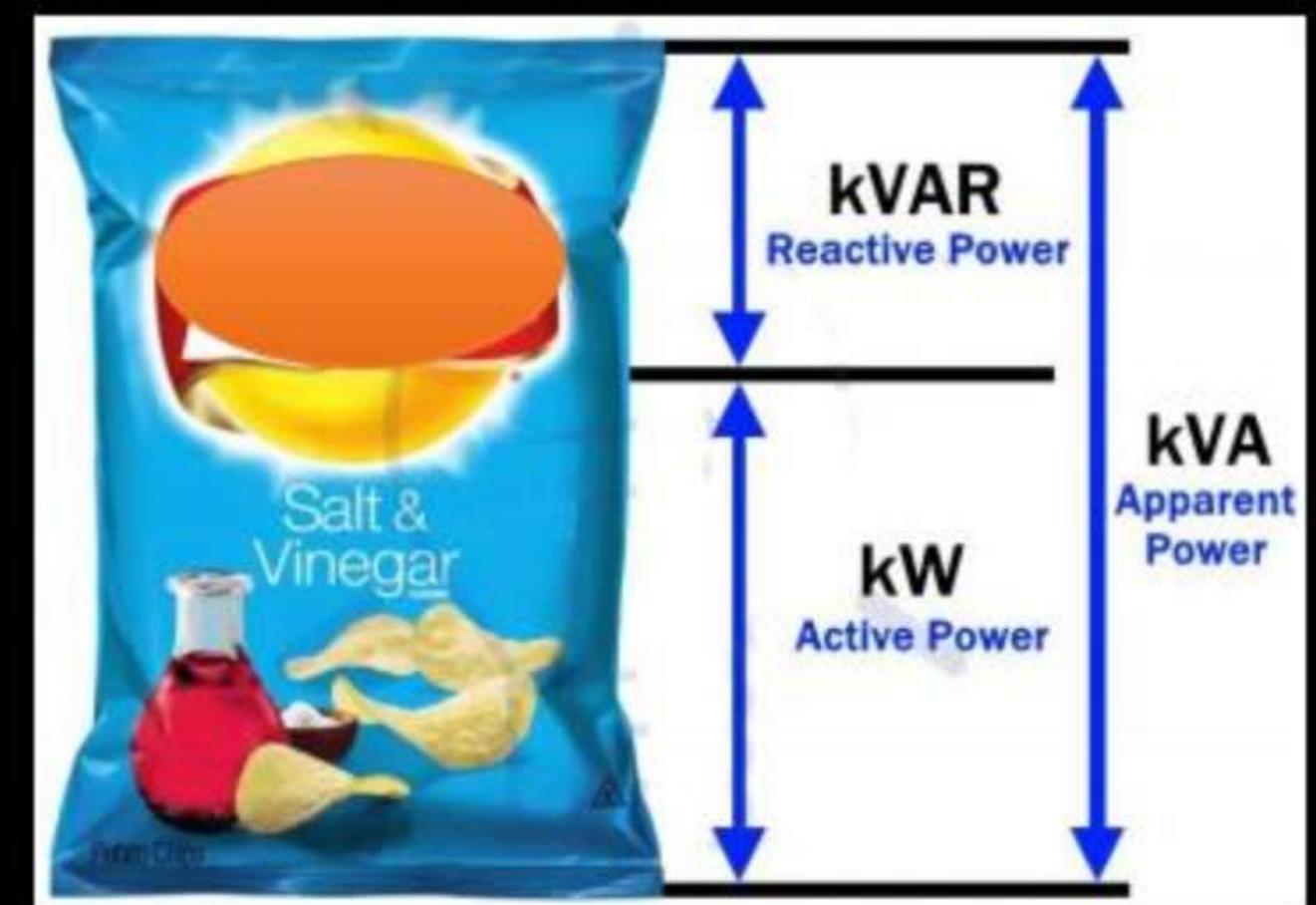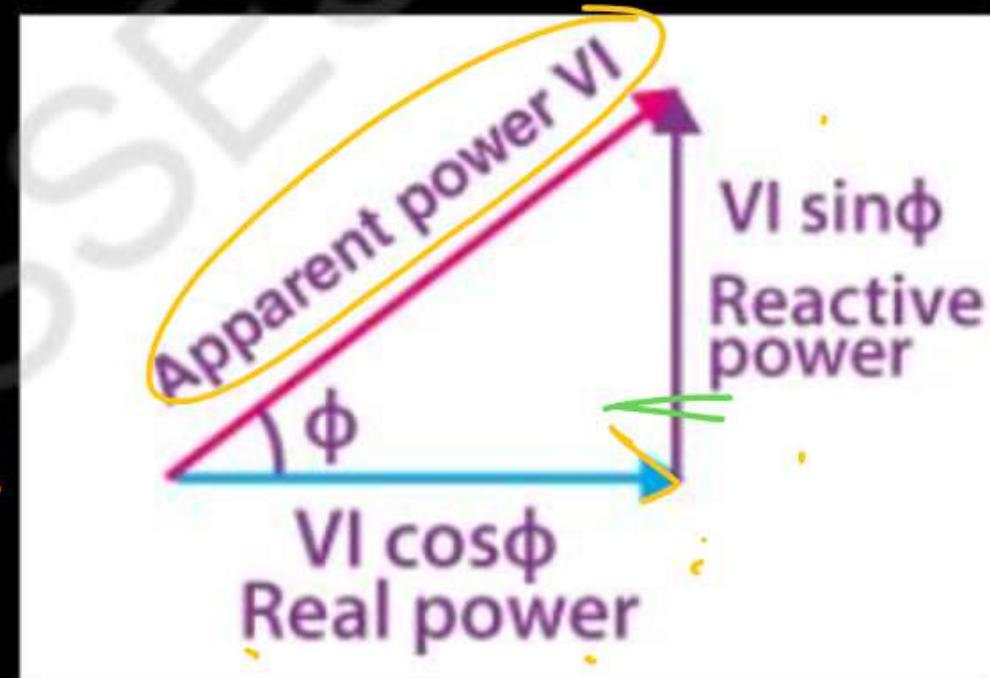

# A.C. Through Pure Inductive Circuit

**Power factor is the**

0.9

90%

0.6

60% will  
4x waste

- Ratio between true power and apparent power is called the for this circuit.
- Ratio of resistance to impedance.
- Cosine of phase angle between voltage and current.

$$\frac{V I \cos \phi}{V I} = \cos \phi = P.F$$

$$P.F = \frac{R}{Z}$$

## Cause of Low Power Factor.

- All AC motor ~~transformers~~ has low power factor.
- Most of the loads has low power factors/
- Industrial heating furnace , induction furnace has low power factor.

## Improvement of Power Factor.

- Using Phase advancers
- Using Capacitor Bank, Synchronous Condenser

## Effects of low power factor

- a) Large Copper Losses b) Large kVA rating c) Poor Voltage Regulation.



- Ex.-9 An A.C. circuit having a pure resistance of 10 ohm and is connected to an a.c. supply of 230 volt and 50Hz. Calculate (a) Current (b) Power Consume (c) Equation of voltage and current.

~~Given~~  $V = 230 \sin \omega t$ ,  $V_m = V_{rm} \sqrt{2}$ ,  $\omega = 2\pi f$   
 $I = \frac{V}{R} = \frac{230}{10} = 23 \text{ amp}$ ,  $I_m = 23\sqrt{2}$

$$\begin{aligned} &= 2\pi \times 50 \\ &= 100\pi \end{aligned}$$

$$P = I^2 R = (23)^2 \times 10$$

$$\boxed{\begin{aligned} V &= V_m \sin \omega t = 230\sqrt{2} \sin 100\pi t \\ i &= 23\sqrt{2} \sin(100\pi t) \end{aligned}}$$

- Ex.-10. A Pure inductive coil allow a current of 10A to flow from an a.c. supply of 230 volt and 50Hz. Calculate  
(a) Inductive reactance (b) Inductance of coil (c) Power Consumed (d) Equation of voltage and current.

$$i = \omega A \quad , \quad i_m = 10\sqrt{2}$$

$$V = 230V \quad , \quad V_m = 230\sqrt{2}$$

$$f = 50 \quad , \quad \omega = 100\pi$$

$$X_L = \frac{V}{I} = \frac{230}{10} = 23\Omega$$

$$X_L = \omega L$$

$$L = \frac{X_L}{\omega} = \frac{23}{100\pi} =$$



$$\begin{aligned} V &= V_m \sin \omega t \\ &= 230\sqrt{2} \sin 100\pi t \end{aligned}$$

$$i = 10\sqrt{2} \sin(100\pi t - 90^\circ)$$

Ans

Ex.-11. A 318 microfarad capacitor is connected across a supply of 230 volt and 50Hz. Calculate

- (a) Capacitive reactance (b) RMS value of Current (c) Equation of voltage and current.

H · W

Ex.-12. An Electrical circuit connected to  $v=100 \sin(628t+ 60)$  it draw current  $i=15 \sin(628t+ 30)$ , identify the circuit , also find the value of Resistance, Reactance, Power ,Power Factor. AKTU- 2020-21

$$v = 100 \sin(628t + 60)$$

$$i = 15 \sin(628t + 30)$$

Current is lagging by  $30^\circ$


Circuit is inductive.

$$V_m = 100$$

$$I_m = 15$$

$$Z = \frac{V}{I} = \frac{100}{15} = 6.67$$

$$\left| \begin{array}{l} \phi = 30^\circ (-) \\ Z = \frac{6.67}{R} \angle 30^\circ \\ = 5.77 + j3.33 \end{array} \right|$$

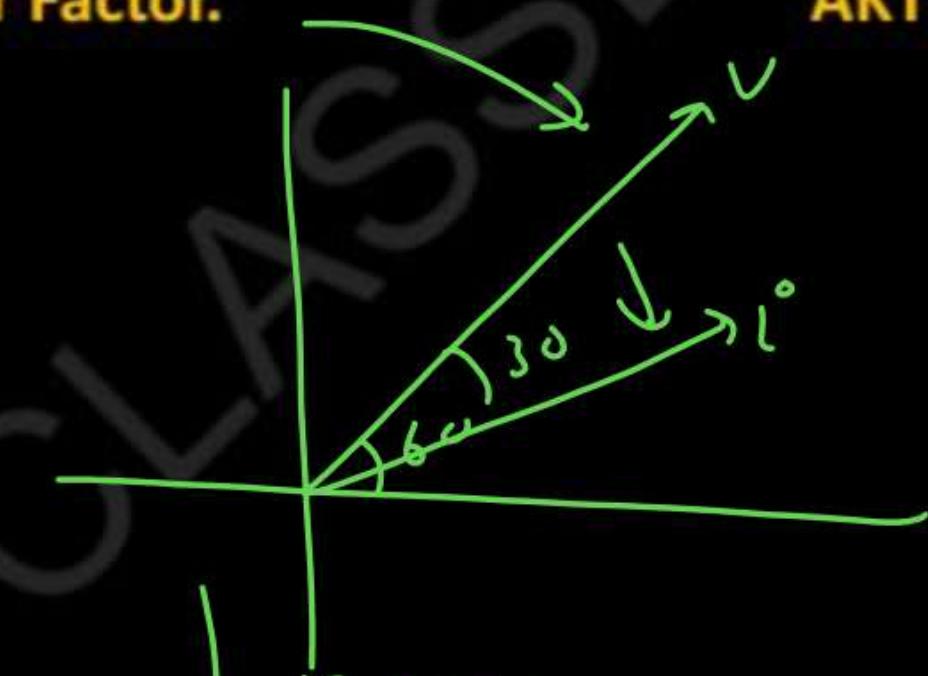

$$\left| \begin{array}{l} P = VI \cos \phi \\ = I^2 R \\ = \left(\frac{10}{\sqrt{2}}\right)^2 \cdot 5.77 = ? \end{array} \right|$$

$$\left| \begin{array}{l} P.F = \cos 30^\circ \\ = \frac{\sqrt{3}}{2} \end{array} \right|$$

Ex.-13. Given  $v = 200 \sin 377t$  volt and  $i = 8 \sin (377t - 30^\circ)$  amp for an a.c. circuit. Determine:- a.) The power factor b.) True Power, c.) Apparent Power d.) Reactive Power. AKTU- 2008-09

Circuit inductive

$$V_m = 100 \quad , \quad I_m = 8$$
$$\varphi = \frac{100}{\sqrt{2}} = I_{rms} = \frac{8}{\sqrt{2}}$$

$$P = VI \cos \varphi$$

$$= \frac{V_m I_m}{2} \cos \varphi$$

$$= \frac{100 \times 8}{2} \cos 30^\circ$$

$$= 400 \cos 30^\circ$$

$$= 346.4 \text{ W}$$

$$\varphi = 30^\circ$$

$$Q = VI \sin \varphi$$
$$= 400 \sin 30^\circ$$
$$Q = 200 \text{ VAR}$$

$$S = VI$$
$$= 400 \text{ VA}$$

Ex.-14. A 120 V, 60 Watt Lamp is to be operated on 220 V, 50 Hz supply mains, In order that lamp should operate on correct voltage Calculate value of (i) Non inductive resistance (ii) Pure Inductance (iii) Pure Capacitance

AKTU- 2005-06

$$V = V_R + V_{Lamp}$$

$$220 = V_R + 120$$


$$V_R = 220 - 120$$

$$V_R = 100$$

$$I^o = \frac{P}{V} = \frac{60}{220} = 0.5 \text{ amp}$$

$$R = \frac{V}{I^o} = \frac{100}{0.5} = 200 \Omega$$
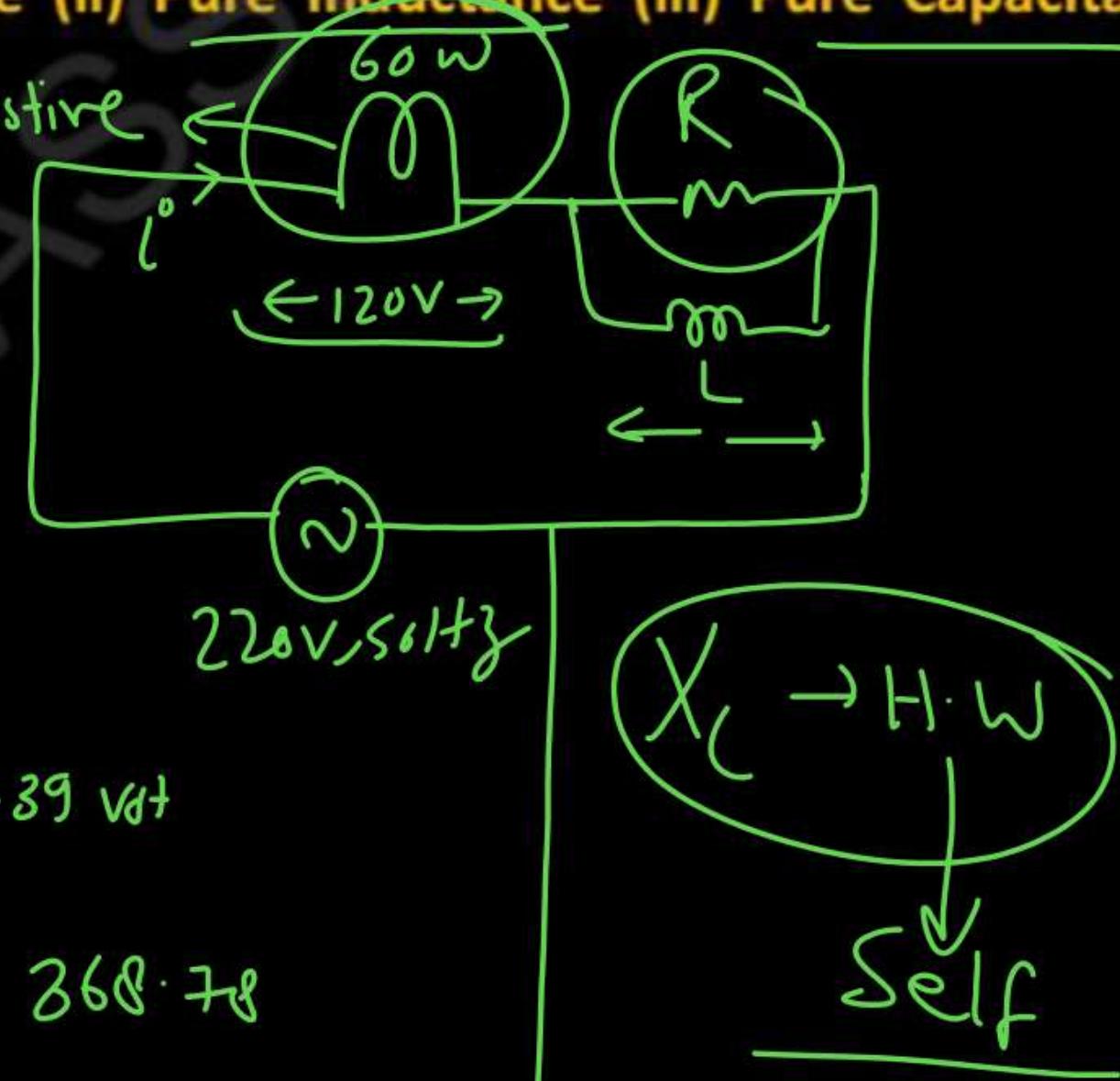
$$\begin{aligned} \vec{V} &= \vec{V}_{Lamp} + \vec{V}_L \\ 220 &= 120 + \vec{V}_L \\ V &= \sqrt{V_R^2 + V_{Lamp}^2} \\ V_L^2 &= V^2 - V_{Lamp}^2 \\ V_L^2 &= 220^2 - 120^2 \\ V_L &= \sqrt{220^2 - 120^2} = 184.39 \text{ volt} \\ X_L &= \frac{V_L}{I^o} = \frac{184.39}{0.5} = 368.78 \\ L &= \frac{X_L}{\omega} = ? \end{aligned}$$



- Ex.-15. A resistance of 120 ohms and a capacitive reactance of 250 ohms are connected in series across a A.C. voltage source. If a current of 0.9 A is flowing in the circuit find out (i) power factor (ii) supply voltage (iii) voltage across resistance and capacitance (iv) Active and reactive power.

$$V_R = IR = ?$$

$$V_C = IX_C = ?$$


$$\sqrt{V} = \sqrt{V_R^2 + V_C^2}$$

$$\theta = \tan^{-1} \frac{V_C}{V_R}$$

$$P.F. = \cos\theta$$

$$P = I^2 R = VI \cos\theta$$

$$Q = VI \sin\theta$$

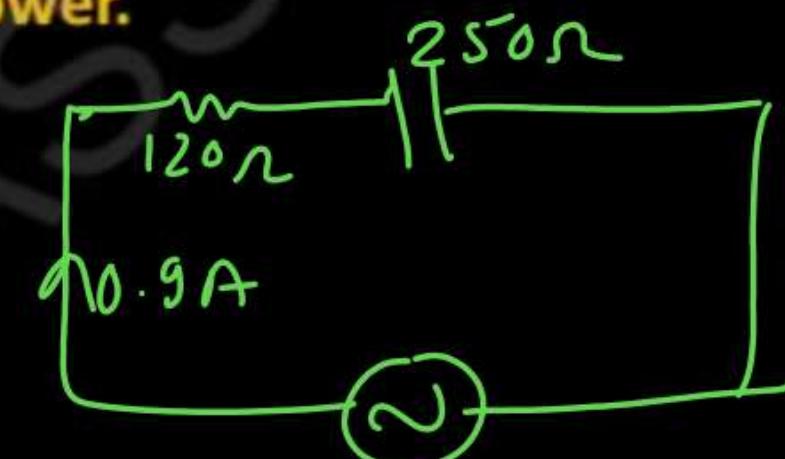

- Ex.-16. A coil having a resistance of 6 ohm and an inductance of 0.0255 H is connected across a 230v, 50 Hz a.c. supply. Calculate (i) Current (ii) power factor (iii) Active power (iv) Reactive Power (v) Apparent Power (vi) It is desired to improve power factor to 0.8 .What value of capacitance to be connected in series R and what is reduction in reactive power. AKTU- 2009-10


$$X_L = 2\pi f L \\ = 100\pi \times 0.0255 = 8\Omega \\ \boxed{Z = 6 + 8j}$$

$$I = \frac{230}{(6+8j)} = \boxed{23} \angle -53.18^\circ$$

$$P.F = \cos 53.18 = \boxed{0.599}$$

$$P = VI \cos \phi \\ Q = VI \sin \phi \\ S = VI$$
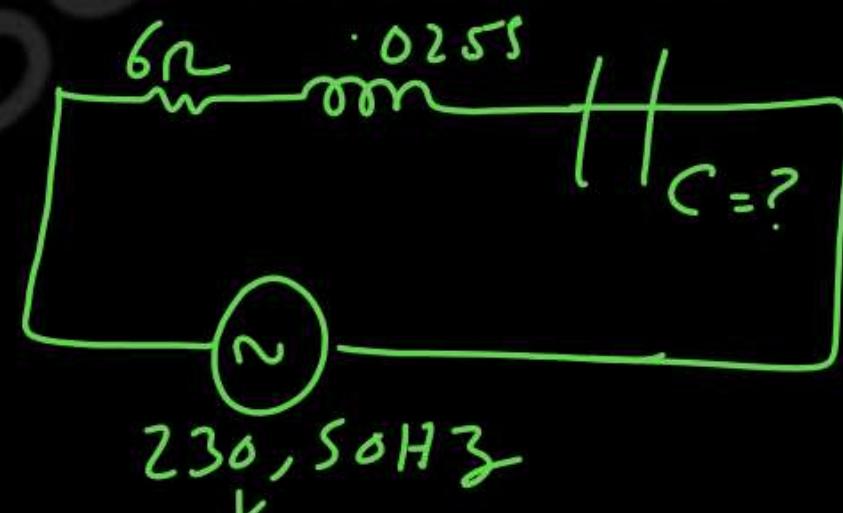
$$Z = R + j(X_L - X_C) \\ \cos \phi = \frac{R}{Z} = \frac{6}{Z} = 0.8 \\ Z = \frac{6}{0.8} = 7.5 \\ \boxed{7.5 = \sqrt{6^2 + (8-X_C)^2}} \\ X_C = 3.5 \Omega \\ X_C = \frac{1}{\omega C} \Rightarrow \boxed{k = \frac{1}{\omega X_C}}$$



- Ex.-17. A series RLC circuit is composed of 10 ohm resistance , 0.1H inductance and 50 microfarad capacitance. A voltage  $v(t) = 141.4 \cos(100\pi t)$  V is impressed upon the circuit . Determine (i) The expression for instantaneous current, (ii) The voltage drops  $V_R, V_L, V_C$  across resistor capacitor and inductor (iii) Draw the phasor diagram using all the voltage relation. AKTU- 2014-15

$$X_L < 10\pi \cdot 0.1 = 31.4\Omega$$

$$X_C = \frac{1}{100\pi \times 50 \mu F} = 63.66\Omega$$

$$X_C - X_L = 63.66 - 31.44 = 32.2\Omega$$

$$Z = R - j(X_C - X_L)$$

$$\boxed{Z = 10 - 32.2j} \rightarrow RLO \quad \theta = ?$$

$$I = \frac{V}{Z} = \frac{141.4 / \angle 0^\circ}{(10 - 32.2j)} = ?$$

$$I_m = \sqrt{2} I_{rm}$$



$$\omega = \omega_0 f = 2\pi f$$

$$f = 50$$

$$V_m = 141.4$$

$$V_{rms} = \frac{141.4}{\sqrt{2}}$$

$$I = I_m \sin(\omega t + \phi)$$

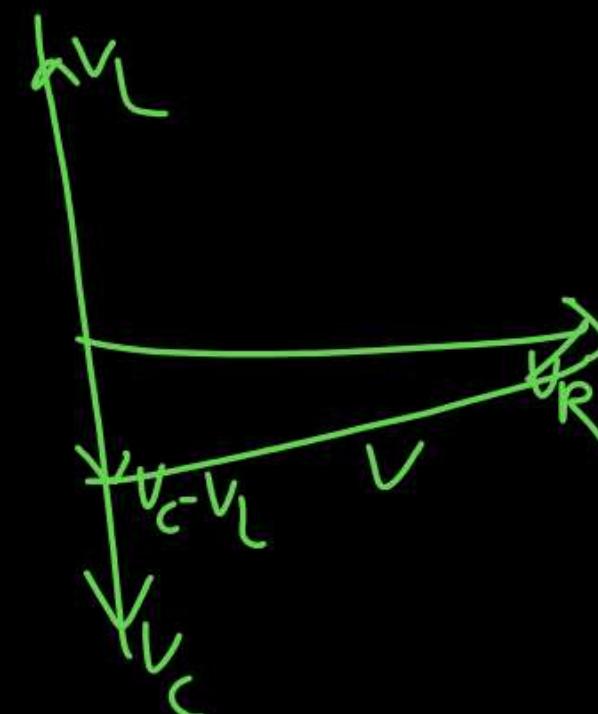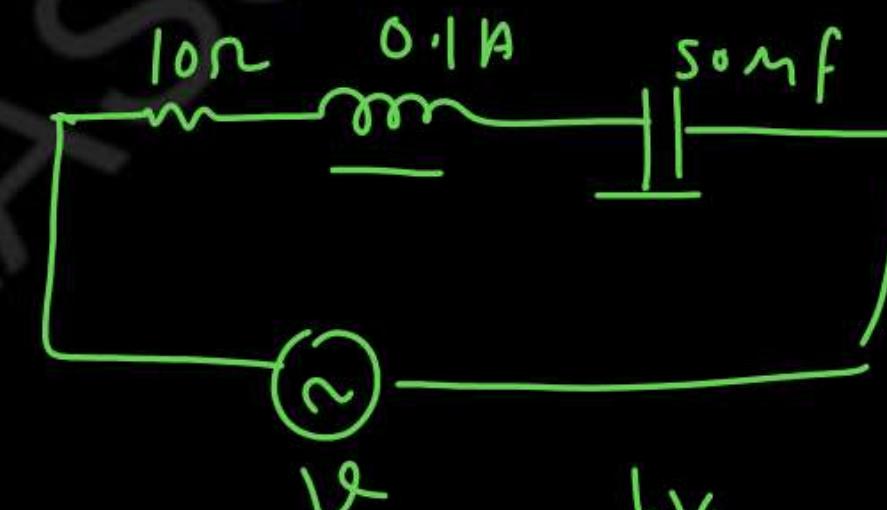

# Resonance in Series RLC circuit

## Condition of Resonance in Series RLC circuit:-

- Power Factor is unity
- Voltage and current are in same phase
- A series resonant circuit has the capability to draw heavy current and power from the mains; it is also called **acceptor circuit**, 2 marks

## Parameters at Resonance Frequency:

### (i) Resonance Frequency

$$(X_L - X_C) = 0$$

$$X_L = X_C$$



$$2\pi f L = \frac{1}{2\pi f C}$$

$$4\pi^2 f^2 = \frac{1}{LC}$$

$$Z_{\min} \quad I = \frac{V}{Z}$$

$$f_r^2 = \frac{1}{4\pi^2 LC}$$


$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

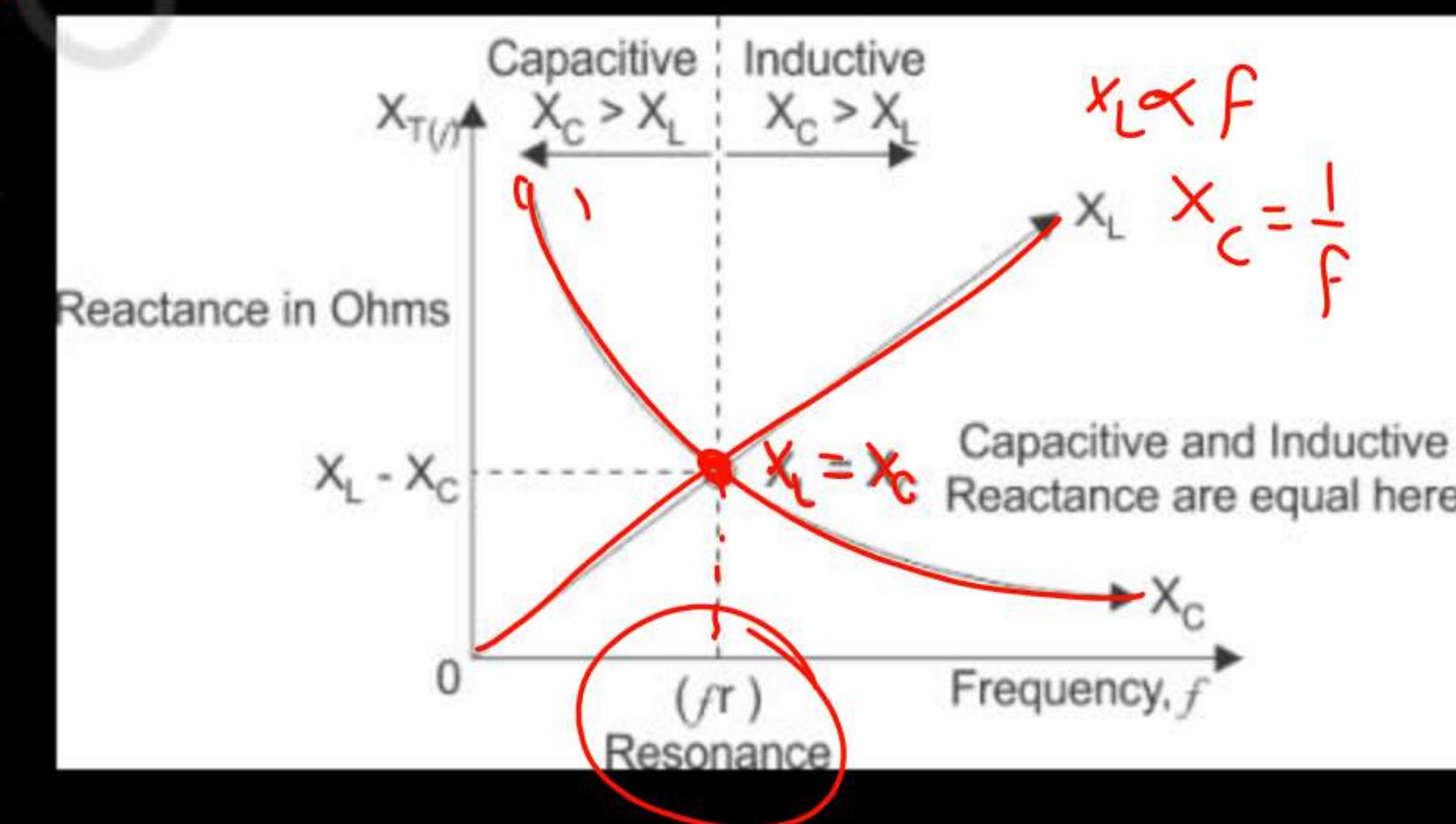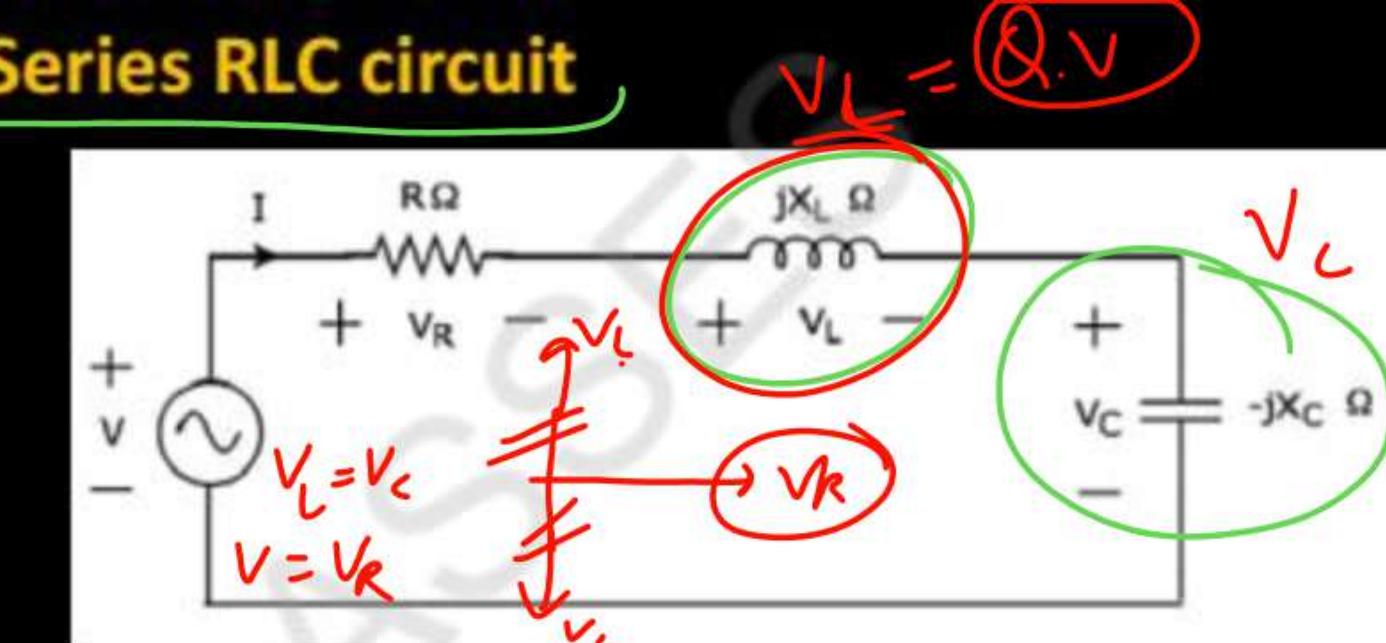

# Resonance in Series RLC circuit

- **Parameters at Resonance Frequency:**

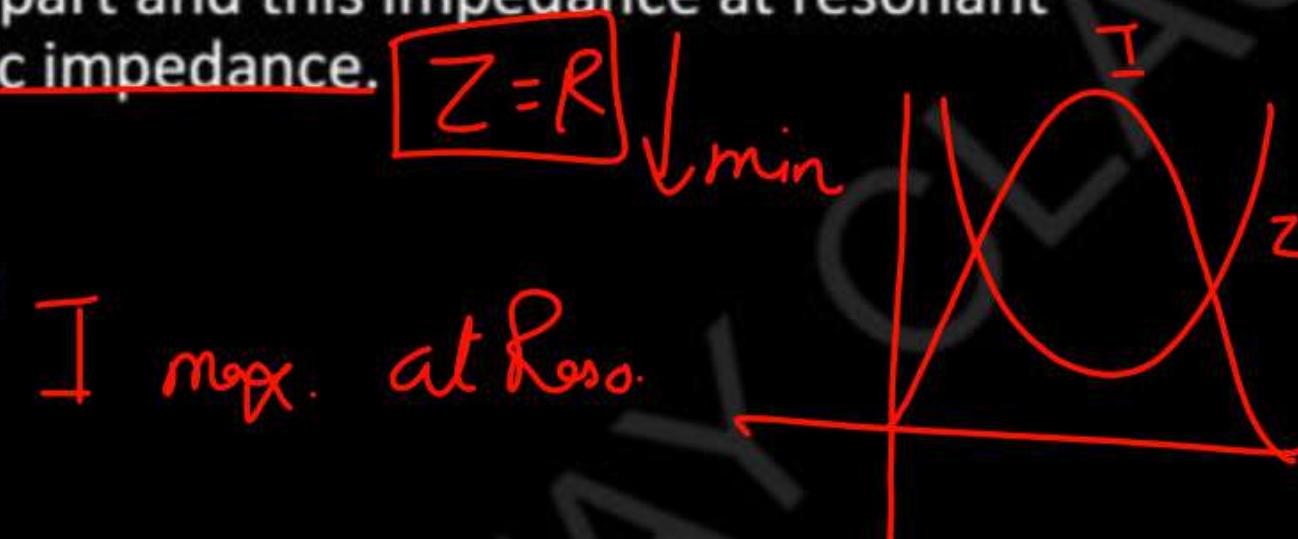- **(ii) Impedance at Resonance:** At resonance, the total impedance of series RLC circuit is equal to resistance i.e  $Z = R$ , impedance has only real part but no imaginary part and this impedance at resonant frequency is called dynamic impedance.





- **(iii) Current at Resonance:**

$I_{\text{max}} \text{ at Reso.}$

- **(iv) Quality Factor:-** The ratio of a voltage developed across the inductance or Capacitance at resonance to the applied voltage

$$Q = \frac{V_L \text{ or } V_C}{V} = \frac{I \times X_L}{I \times R} = \boxed{\frac{\omega L}{R} = Q}$$

## Resonance Curve:

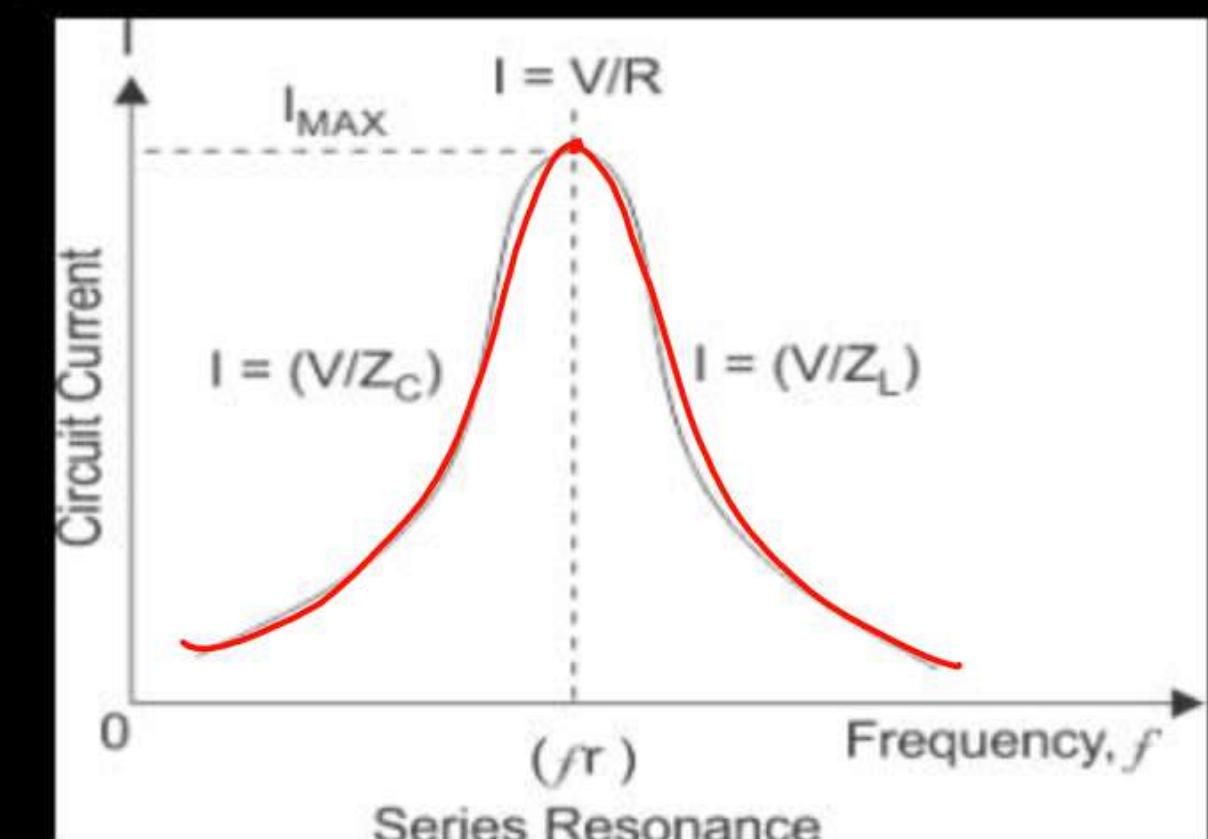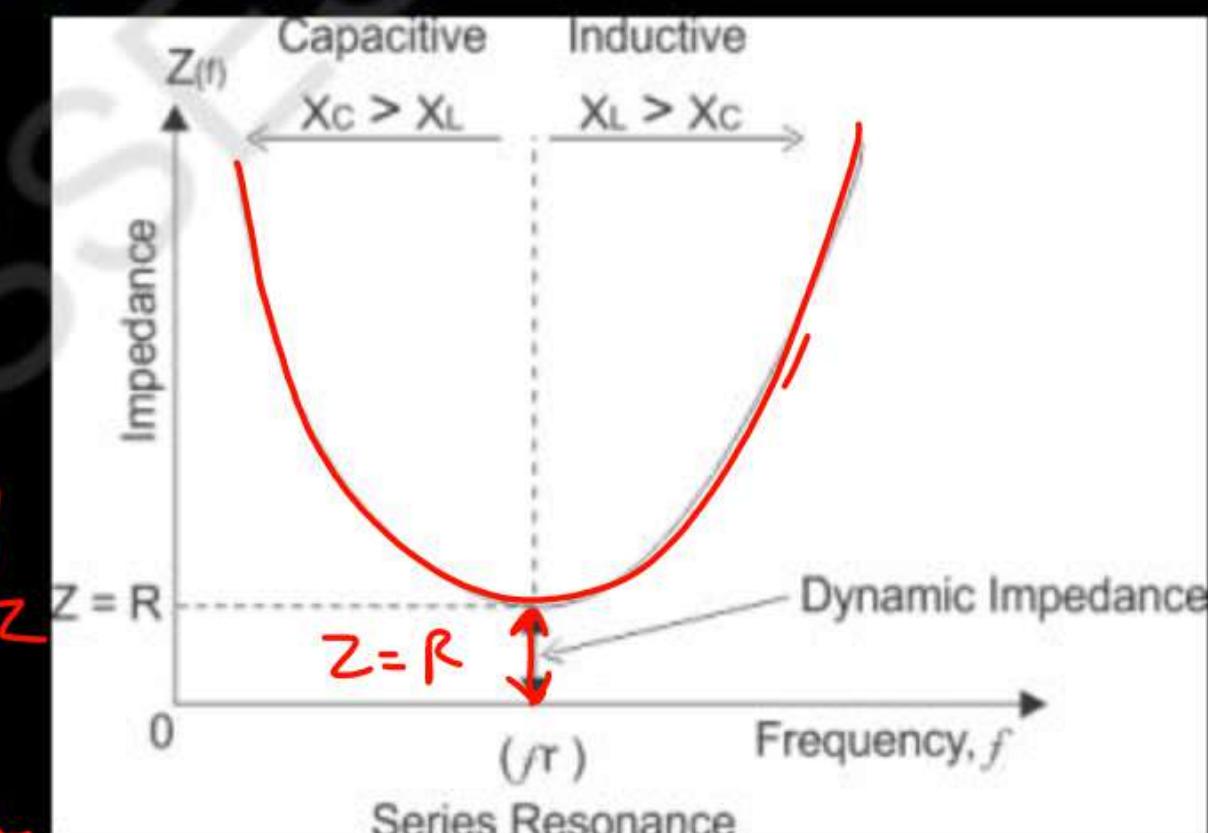

- Series resonance RLC circuit is called as voltage magnification circuit, because the magnitude of voltage across the inductor and the capacitor is equal to  $Q$  times the input sinusoidal voltage  $V$ .
- Application of Series RLC Resonant Circuit
- Since **resonance in series RLC circuit** occurs at particular frequency, so it is used for filtering and tuning purpose as it does not allow unwanted oscillations that would otherwise cause signal distortion, noise and damage to circuit to pass through it.

# Bandwidth of Series RLC Circuit at resonance

The bandwidth of any system is the range of frequencies for which the current or output voltage is equal to 70.7% of its value at the resonant frequency, and it is denoted by BW.

Frequency  $f_1$  is the frequency at which the current is 0.707 times the current at resonant value, and it is called the **lower cut-off frequency**. The frequency  $f_2$  is the frequency at which the current is 0.707 times the current at resonant value (i.e. maximum value), and is called the **upper cut-off frequency**. The bandwidth, or BW, is defined as the frequency difference between  $f_2$  and  $f_1$ .

$$\boxed{I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}}$$



also

$$I = \frac{I_m}{\sqrt{2}}$$

at Resonance  $Z = R$

$$I_m = \frac{V}{R}$$
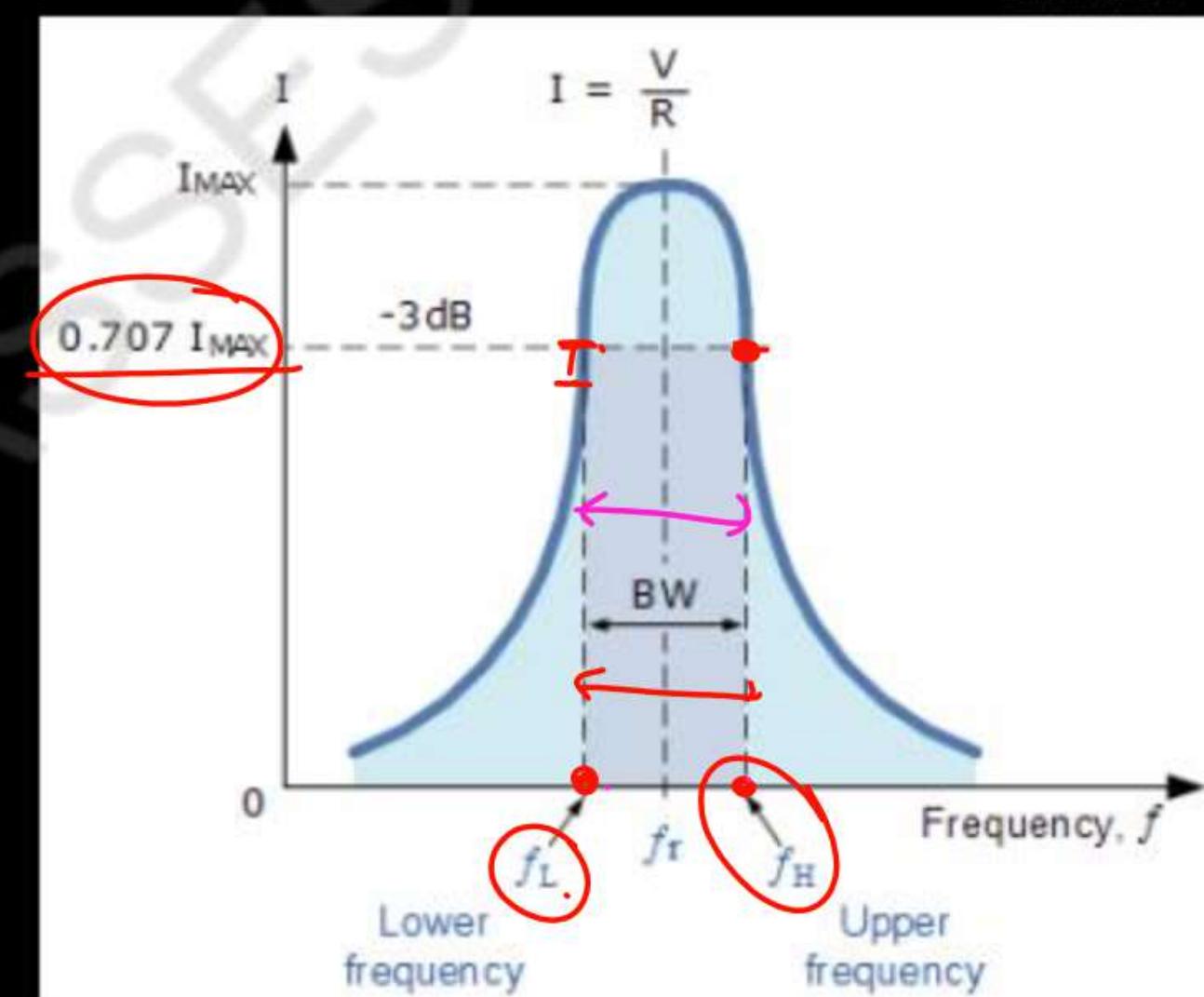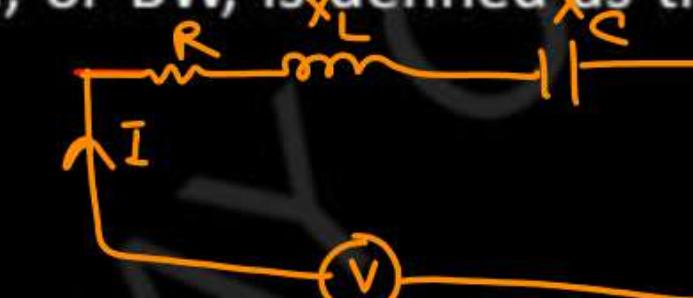
$$\boxed{\bar{I} = \frac{V}{R\sqrt{2}}}$$



$$\frac{X}{R\sqrt{2}} = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\sqrt{R^2 + (X_L - X_C)^2} = R\sqrt{2}$$

$$R^2 + (X_L - X_C)^2 = 2R^2$$

$$(X_L - X_C)^2 = R^2$$

$$X_L - X_C = \pm R$$

$$\omega L - \frac{1}{\omega C} = \pm R$$

$$\text{So } \omega_1 L - \frac{1}{\omega_1 C} = +R - \textcircled{1}$$

$$\omega_2 L - \frac{1}{\omega_2 C} = -R - \textcircled{2}$$

## Bandwidth of Series RLC Circuit at resonance

Add  $\textcircled{1}$  &  $\textcircled{2}$

$$L(\omega_1 + \omega_2) - \frac{1}{C} \left( \frac{1}{\omega_1} + \frac{1}{\omega_2} \right) = 0$$

$$L(\omega_1 + \omega_2) - \frac{1}{C} \left( \frac{\omega_2 + \omega_1}{\omega_1 \omega_2} \right) = 0$$

$$L - \frac{1}{C} \omega_1 \omega_2 = 0$$

$$L = \frac{1}{C} \omega_1 \omega_2$$

$$\boxed{\omega_1 \omega_2 = \frac{1}{LC}}$$

$$4\pi^2 f_1 f_2 = \frac{1}{LC}$$

$$f_1 f_2 = \frac{1}{4\pi^2 LC} = f_r^2$$

$$\boxed{f_r = \sqrt{f_1 f_2} = \frac{1}{2\pi\sqrt{LC}}}$$

Subtract  $\textcircled{1}$  &  $\textcircled{2}$

$$L(\omega_1 - \omega_2) - \frac{1}{C} \left( \frac{1}{\omega_1} - \frac{1}{\omega_2} \right) = 2R$$

$$L(\omega_1 - \omega_2) - \frac{1}{C} \left( \frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right) = 2R$$

$$L + \frac{1}{C} \omega_1 \omega_2 = \frac{2R}{\omega_2 - \omega_1}$$


$$L + \frac{1}{C} \times \frac{1}{LC} = \frac{2R}{\omega_2 - \omega_1}$$

$$2L = \frac{2R}{\omega_2 - \omega_1}$$

$$\omega_2 - \omega_1 = \frac{R}{L}$$

$$\boxed{f_2 - f_1 = \frac{R}{2\pi L}}$$

$$\boxed{B.W. = \frac{R}{2\pi L}}$$

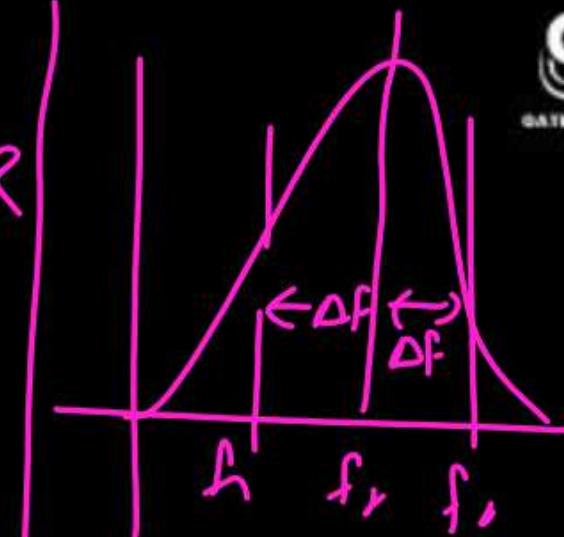

$$f_1 = f_r - \Delta f = f_r - \frac{R}{4\pi L}$$

$$f_2 = f_r + \Delta f = f_r + \frac{R}{4\pi L}$$

$$\boxed{\Delta f = \frac{R}{4\pi L}}$$

## Condition of Resonance in Parallel RLC circuit:-

- **Parallel Resonance** means when the circuit current is in phase with the applied voltage of an AC circuit containing an inductor and a capacitor connected together in parallel.

- **Parameters at Resonance Frequency:**

- **(i) Resonance Frequency**

$$I_C = I_L \sin \phi_L$$

$$I_L = \frac{V}{Z_L}$$

$$\sin \phi_L = \frac{X_L}{Z_L} \text{ and } I_C = \frac{V}{X_C}$$

$$\frac{V}{X_C} = \frac{V}{Z_L} \times \frac{X_L}{Z_L} \text{ or } X_L X_C = Z_L^2 \text{ or}$$

$$\frac{\omega L}{\omega C} = Z_L^2 = (R^2 + X_L^2) \text{ or}$$

$$\frac{L}{C} = R^2 + (2\pi f_r L)^2 \text{ or}$$



$$\begin{aligned} \frac{L}{C} &= Z_L^2 = R^2 + X_L^2 \\ X_L^2 &= \left( \frac{L}{C} - R^2 \right) \Rightarrow X_L = \sqrt{\frac{L}{C} - R^2} \end{aligned}$$

$$2\pi f_r L = \sqrt{\frac{L}{C} - R^2} \text{ or}$$

$$f_r = \frac{1}{2\pi L} \sqrt{\frac{L}{C} - R^2} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

If R is very small as compared to L, then

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

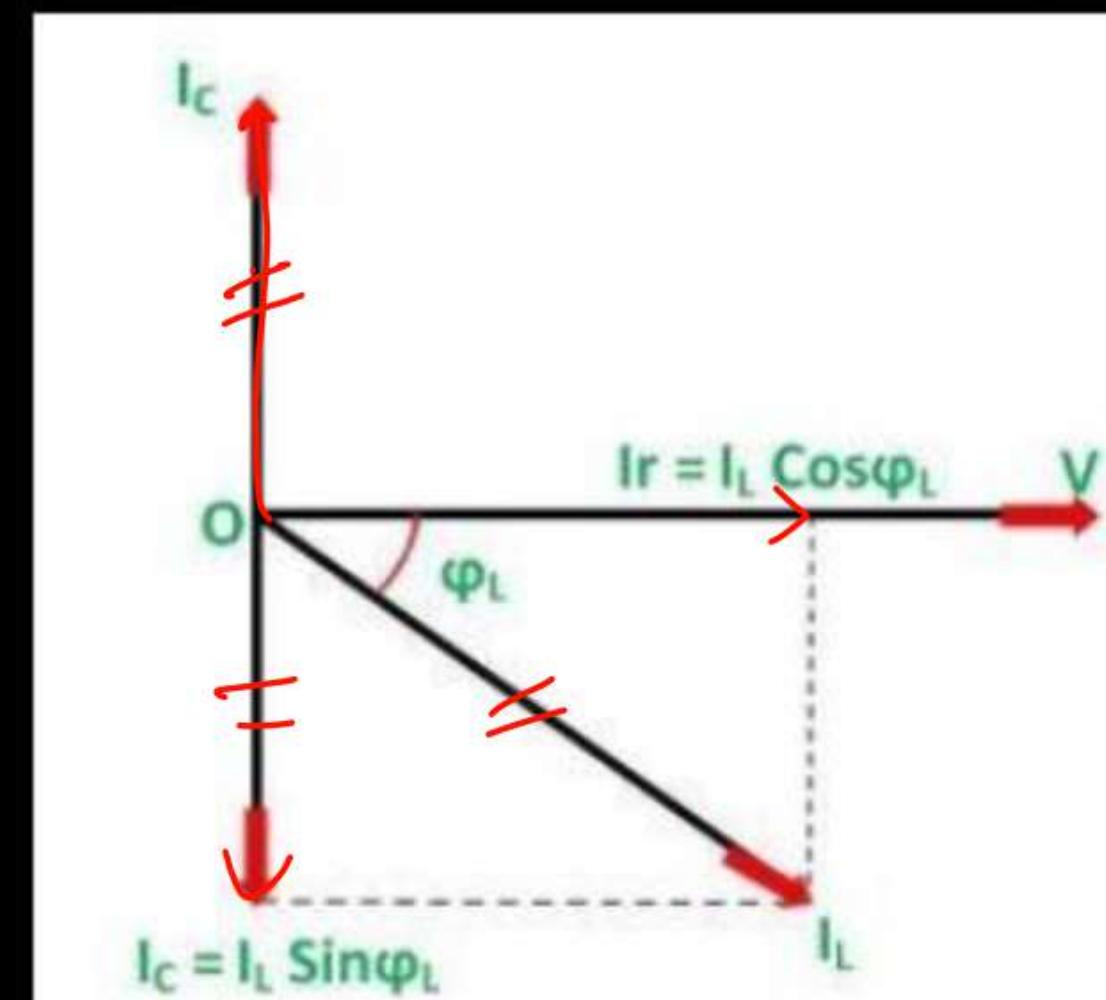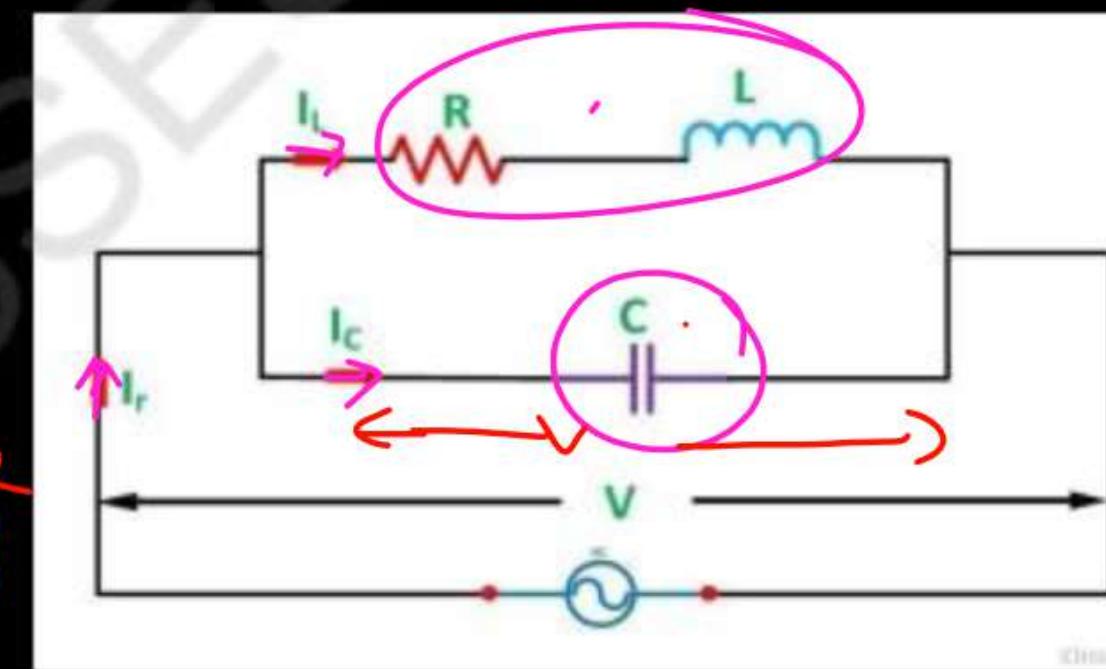

# Resonance in Series RLC circuit

- (ii) Impedance at Parallel Resonance:

- At parallel resonance line current  $I_r = I_L \cos\phi$  or

$$\frac{V}{Z_r} = \frac{V}{Z_L} \times \frac{R}{Z_L} \quad \text{or} \quad \frac{1}{Z_r} = \frac{R}{Z_L^2} \quad \text{or}$$

$$\frac{1}{Z_r} = \frac{R}{L/C} = \frac{CR}{L} \quad (\text{as } Z_L^2 = \frac{L}{C})$$



$Z_r = \frac{L}{CR}$

$$I_r \cos\phi = I_r$$

$I_{mp} = \text{max.}$   
 $\text{Current} = \text{min}$

- The circuit impedance is purely resistive because there is no frequency term present in it. Circuit impedance  $Z_r$  will be in Ohms.
- The value of  $Z_r$  will be very high because the ratio  $L/C$  is very large at parallel resonance.
- The value of **circuit current,  $I_r = V/Z_r$  is very small** because the value of  $Z_r$  is very high.
- parallel resonant circuit can draw a very small current and power from the mains, therefore, it is also called as **Rejector Circuit**.

## Resonance Curve:

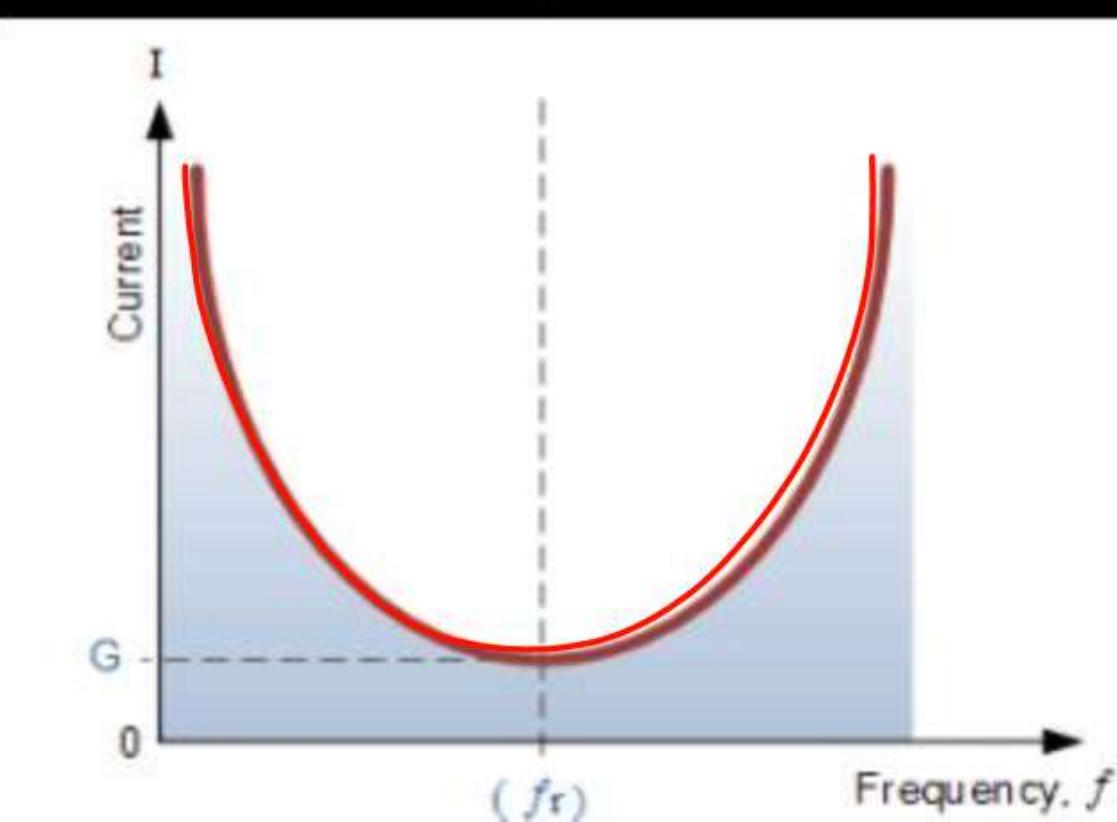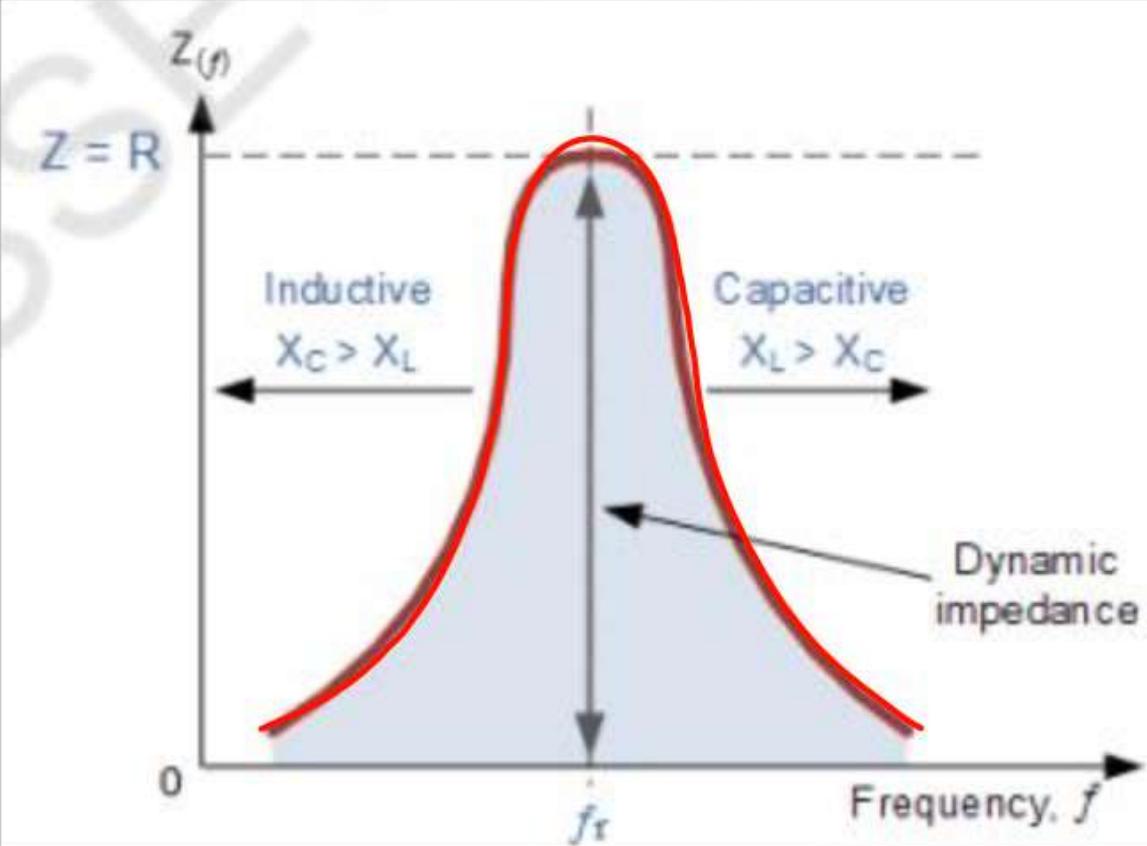

# Quality Factor at Parallel Resonance

- The ratio of a Current across the inductance or Capacitance at resonance to the Current at resonance.
- Parallel resonance RLC circuit is called as **Current magnification** circuit.

$$Q = \frac{I_{L-C}}{I} = \frac{\cancel{X_L}}{\cancel{X_C}} = \frac{Z_r}{X_L} = \frac{X/R_C}{\omega L} = \boxed{\frac{1}{\omega R_C} = Q}$$

$$= \frac{X_L/X_C}{\cancel{X}} = \frac{Z_r}{X_C} = \frac{Y_R X}{L} = \boxed{\frac{\omega L}{R} = Q}$$

- Ex.-18 A Series RLC circuit consisting a resistance of 20 ohm , inductance of 0.2 H and Capacitance of  $150\mu F$  is connected across 230V, 50 Hz source. Calculate (i) Impedance (ii) Current (III) Power Factor (iv) Frequency Required to Make power factor Unity (v) Quality Factor AKTU- 2012-13

↓  
Resonance

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{0.2 \times 150 \times 10^{-6}}} = ?$$

$$\theta = \frac{\omega L}{R} = \frac{2\pi f_r \cdot 0.2}{20} \text{ Ans}$$


- Ex.-19. A 20 ohm resistor is connected in series with an inductor and a capacitor across a variable frequency 25 V supply. When the Frequency is 400 Hz , the current is at the maximum value of 0.5 A and the potential difference across the capacitor is 150 V Calculate the resistance and inductance of the inductor.  
AKTU- 2001-02

$$I_m = 0.5$$

$$f_r = 400 \text{ Hz} , V = 25 \text{ V} \text{ at } 400 \text{ Hz}$$

$$Z = R = \frac{V}{I} = \frac{25}{0.5} = 50 \Omega$$
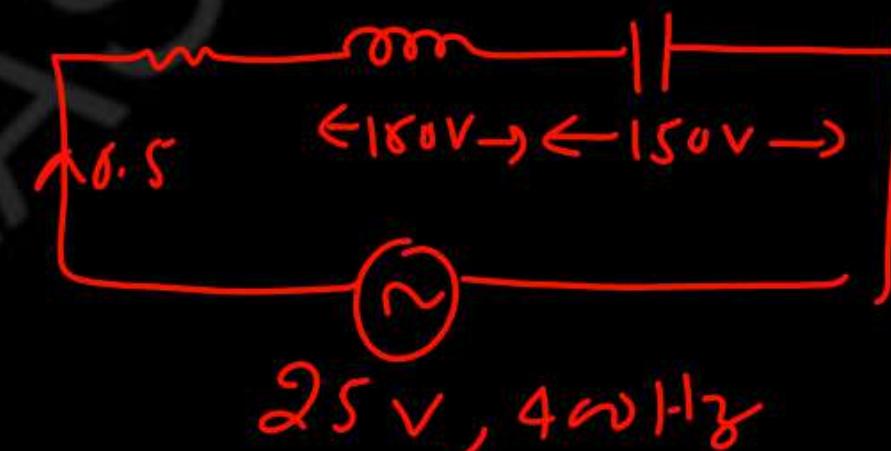
$$X_L = \frac{V_L}{I} = \frac{150}{0.5} = 300 \Omega = X_C$$



## • Ex.-20.

A series R – L – C circuit consists of R = 1000 Ohm, L = 100 mH and C = 10  $\mu$ F.

The applied voltage across the circuit is 100 V.

AKTU 2021-22

- (i) Find the resonant frequency of the circuit.
- (ii) Find the quality factor of the circuit at the resonant frequency.
- (iii) At what angular frequencies do the half power points occur?
- (iv) Calculate the bandwidth of the circuit.

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$Q = \frac{\omega L}{R}$$

$$f_1 = f_r + \Delta f = f_r + \frac{R}{4\pi L}$$

$$f_2 = f_r - \Delta f = f_r - \frac{R}{4\pi L}$$

$$\text{BW} = f_2 - f_1$$

$\theta_0$

- Ex.-21. A Series circuit consists of a resistance of 10 ohm and inductance of 50mH and a variable capacitance in series across a 100V , 50 Hz supply. Calculate (i) Value of capacitance to produce resonance (ii) Voltage across the capacitance (iii) Q- Factor. AKTU 2018-19

$$X_L = 2\pi \times 50 \times 50 \times 10^{-3} = 15.7 \Omega$$


At Resonance.

$$Z = R = 10 \Omega$$

$$I_m = \frac{V}{Z} = \frac{100}{10} = 10 \text{ amp}$$

$$V_L = I X_L = V_C$$

$$X_C = \frac{V_C}{I} = ?$$

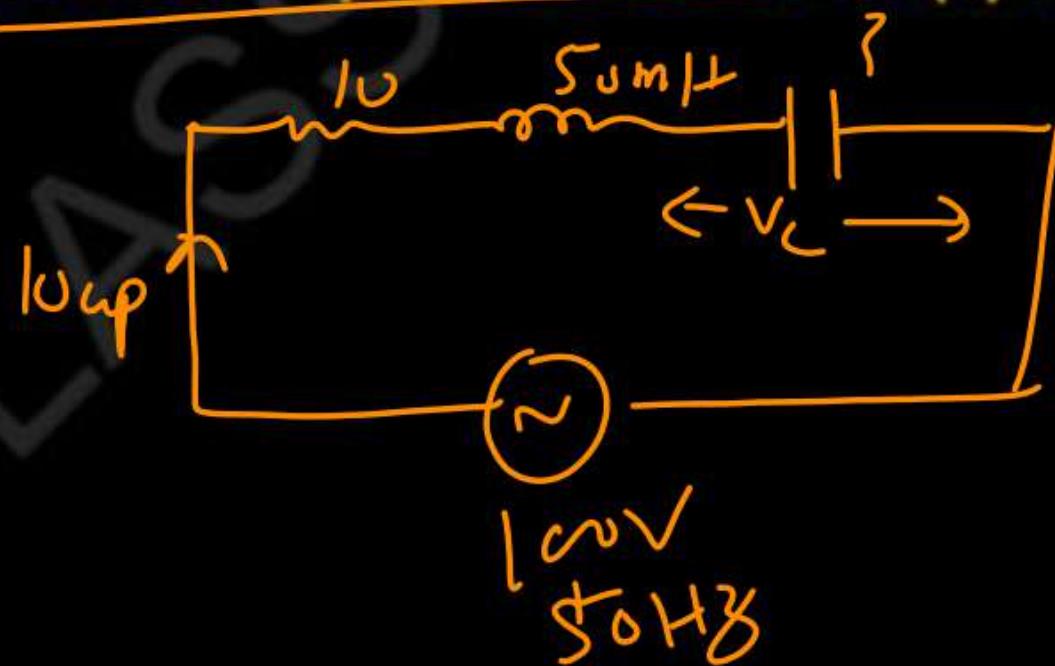


## Concept of Admittance

- **Admittance:-**

$$Y = \frac{1}{Z} = \frac{1}{\sqrt{R^2 + X_L^2}}$$
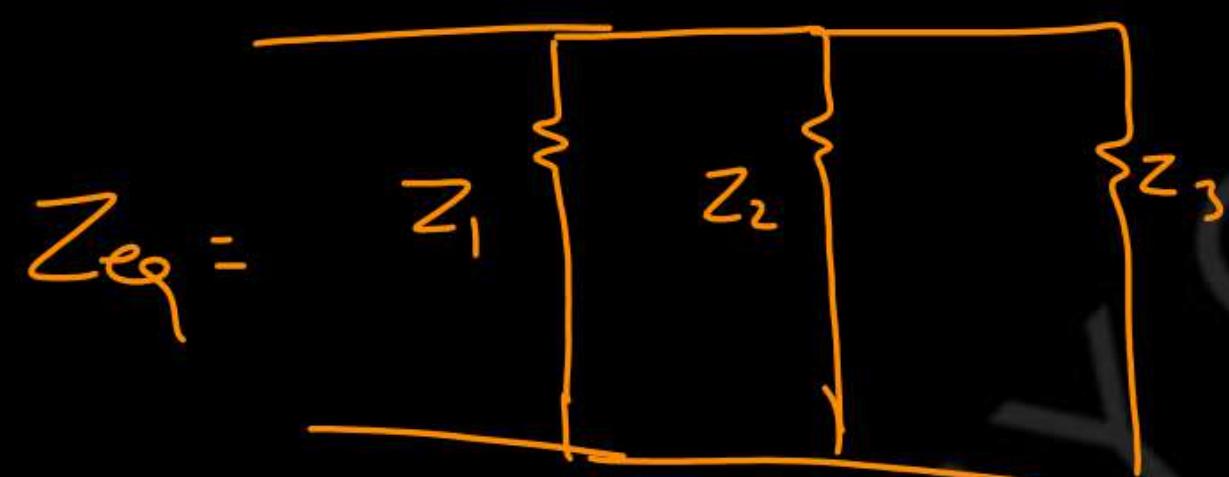
$$\frac{z_1 z_2 z_3}{(2+3j) + (5+6j) + (7+8j)}$$




$$\frac{1}{Z_{eq}} = \frac{1}{z_1} + \frac{1}{z_2} + \frac{1}{z_3}$$

$$= z_1^{-1} + z_2^{-1} + z_3^{-1} + \dots$$

$$\frac{1}{Z_{eq}} = [(2+3j)^{-1} + (5+6j)^{-1} + (7+8j)^{-1}]$$

$Z_{eq} = [Ans]^{-1}$

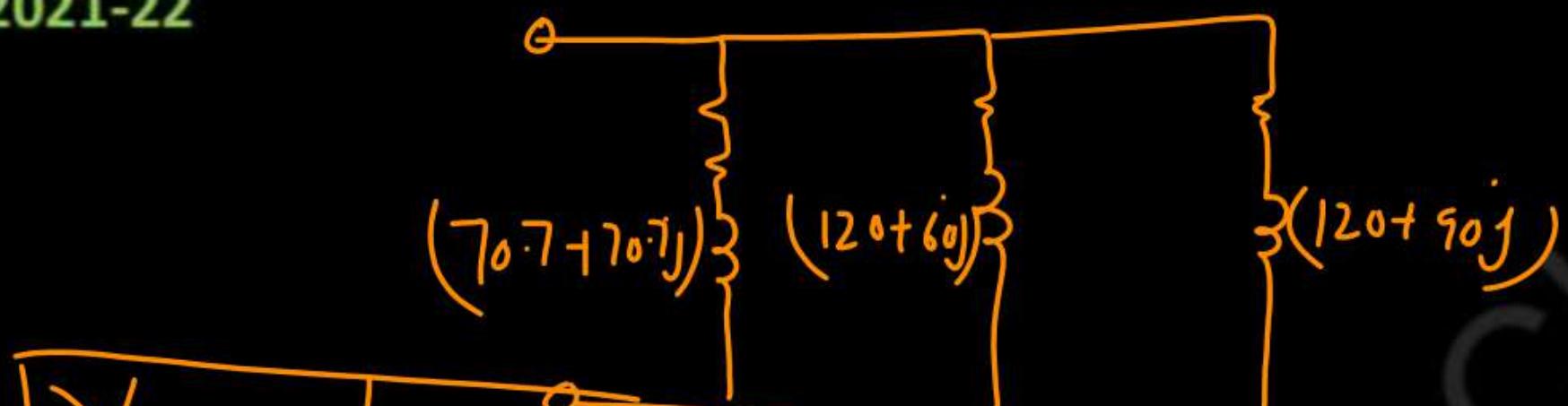- Ex.-23. Three impedances of  $(70.7+j70.7)$  ohm,  $(120+j160)$  ohm and  $(120+j90)$  ohm are connected in parallel across a 250 V supply. Determine (i) admittance of the circuit (ii) supply Current and (iii) power factor AKTU-2021-22



$$Y_{eq} = \frac{1}{Z_{eq}} = \left[ Z_1^{-1} + Z_2^{-1} + Z_3^{-1} \right]^{-1}$$

$Z_{eq} = A\omega^{-1}$

$$I = \frac{V}{Z} = V \cdot Y_{eq}$$

$$I = \gamma \angle \theta$$

$$\cos \phi = P.F.$$

- Ex.-24. Two coils having resistance  $5 \Omega$  and  $10 \Omega$  and inductances  $0.04 \text{ H}$  and  $0.05 \text{ H}$  respectively are connected in parallel across a  $200 \text{ V}, 50 \text{ Hz}$  supply. Calculate: i. Conductance, susceptance and admittance of each coil. ii. Total current drawn by the circuit and its power factor. iii. Power absorbed by the circuit.

AKTU 2021-22

$$G = \frac{1}{R} , S = \frac{1}{X} , Y = \frac{1}{Z}$$

$$X_L = 2\pi f L \times 0.04 = 12.56 \Omega$$

$$X_L = 2\pi f L \times 0.05 = 15.70 \Omega$$

$$Z_1 = 5 + 12.5j$$

$$Z_2 = 10 + 15.70j$$

$$Z_{eq} = \frac{R}{1+jX_L}$$

$$\begin{aligned} Y_{eq} &= Z_1^{-1} + Z_2^{-1} \\ &= (5+12.56j)^{-1} + (10+15.70j)^{-1} \\ &= (0.027 - 0.068j) \end{aligned}$$

- Ex.-25 In series parallel circuit A and B are in parallel and in series with C . The impedances are  $Z_A = 4+3j$  ohm,  $Z_B = 4-j5$  ohm and  $Z_C = 2+j8$  ohm . If the current  $I_C = 25+j0$  amp Calculate (i) Branch voltage (ii) Branch Currents (iii) Total Power (iv) Phasor Diagram

AKTU 2015-16

- Ex.-26. In the circuit shown in figure find (i) Current in each branch (ii) Voltage  $V_{ab}$  and  $V_{bc}$  (iii) Power Loss in the circuit.

AKTU- 2001-02

$$Z_1 = 4 + 8j, Z_2 = -8j, Z_3 = -4j$$

$$Z_{eq} = (Z_1 || Z_2) + Z_3$$

=

$$\underline{Z_{eq}} = 16 - 12j$$

$$I = \frac{V}{Z_{eq}} = \frac{120}{16 - 12j}$$


$$V_{ab} = (-j4)(\underline{-8j})$$

~~Current distribution~~

$$I_1 = I \times \frac{(4 + 8j)}{(4 + 8j) - j8}$$

$$I_1 = (16 - 12j)(1 + 2j)$$




$$V_{bc} = I_1 \times (-8j)$$

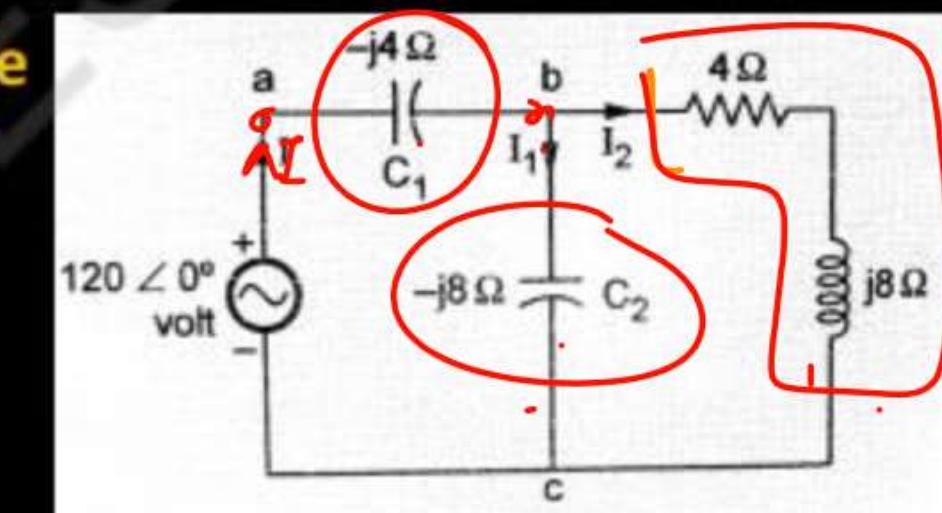

$$P = I^2 R$$

$$= I^2 \times 16$$

# Generation of Three Phase Supply

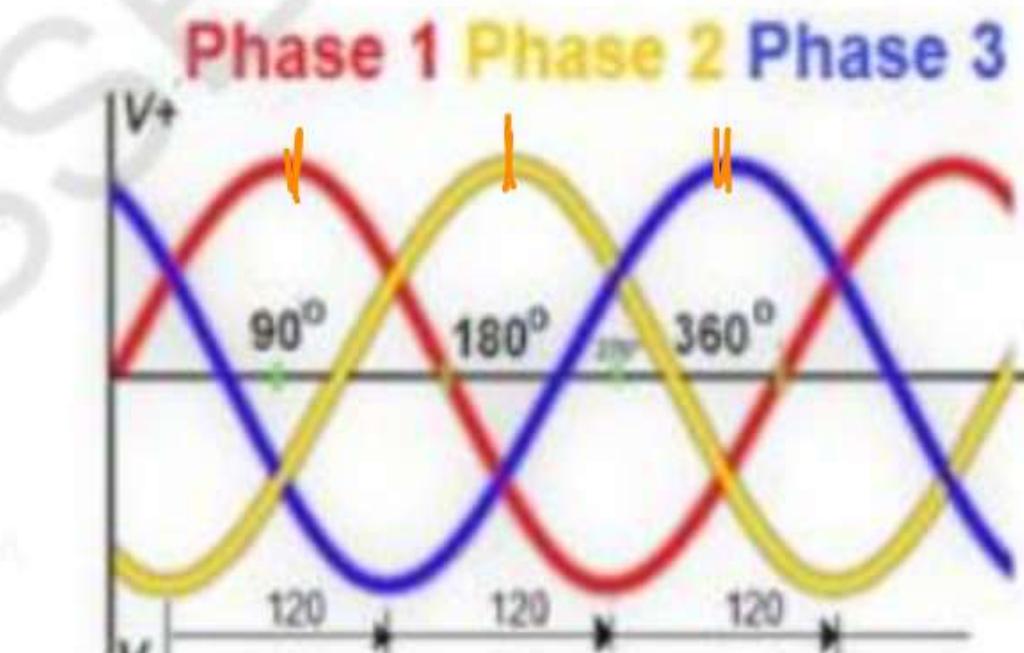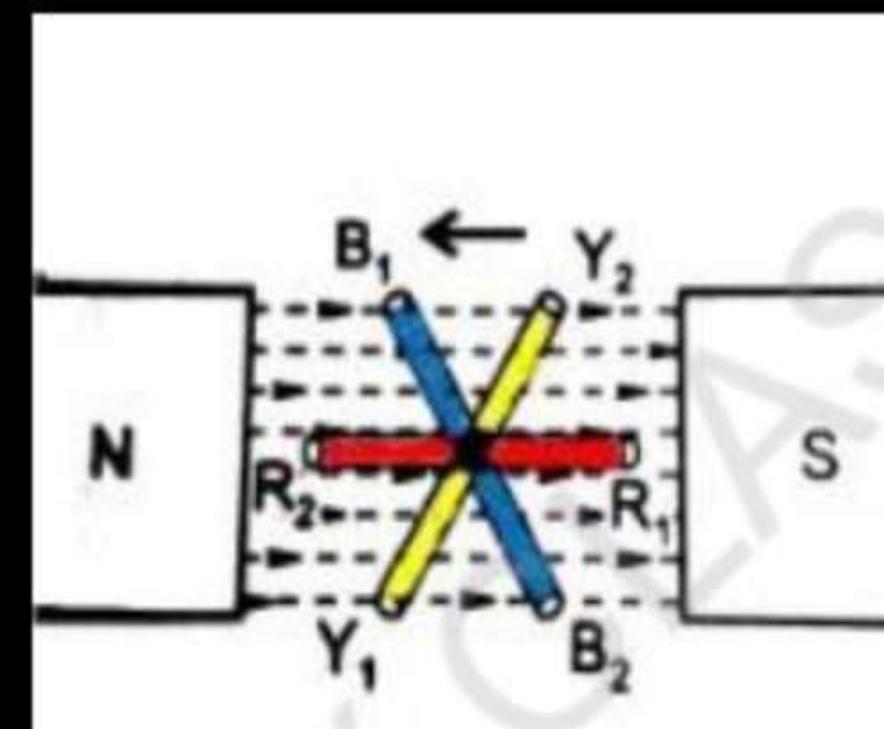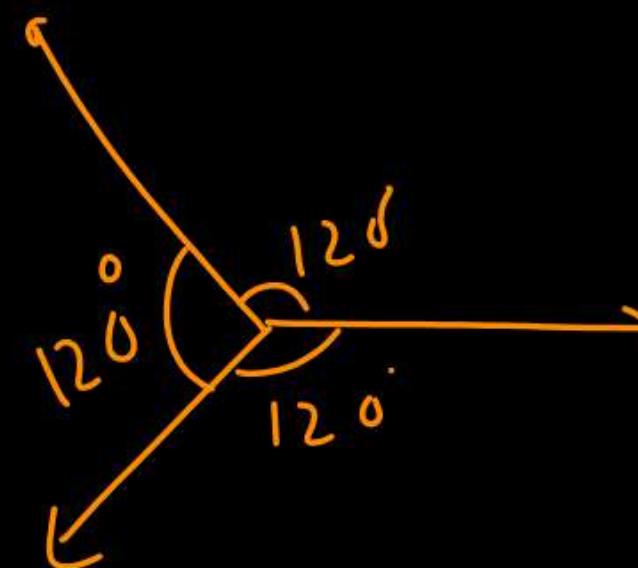


$$E_R = E_m \sin \omega t$$

$$E_Y = E_m \sin(\omega t - 120^\circ)$$

$$E_B = E_m \sin(\omega t - 240^\circ)$$

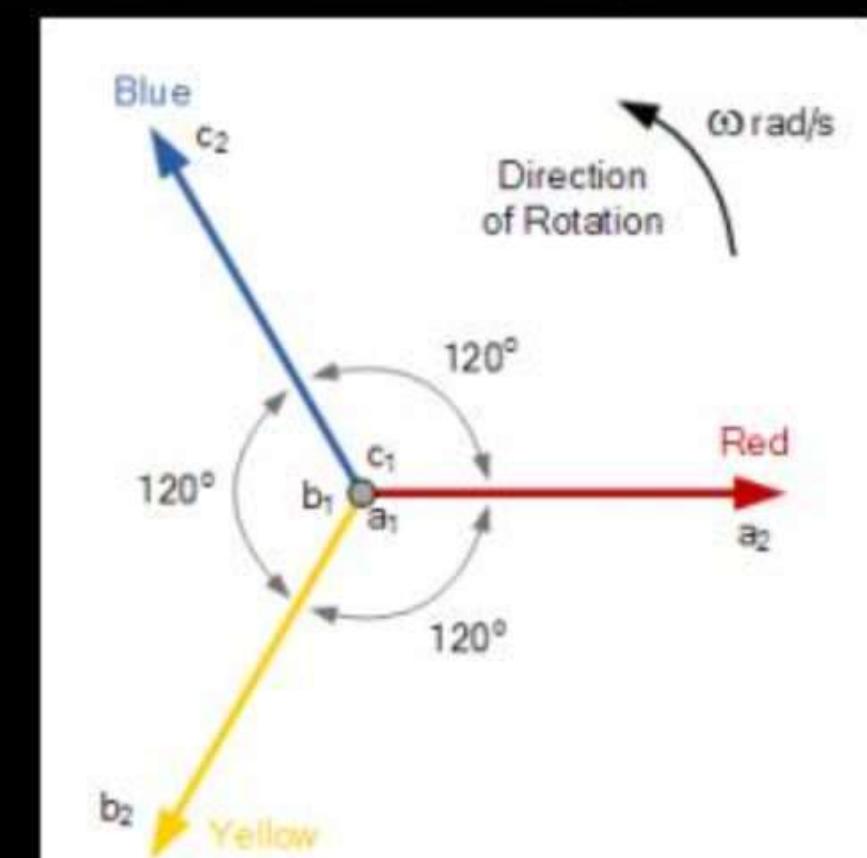Sum of all three phasors at any instant is always zero





## R-Y-B Important Definitions

- **Phase Sequence** – The phase sequence is defined as the order in which the emf in three phase or coils of an alternator attains the positive maximum value. It is determined by the direction of rotation of alternator.
- **Naming the Phases** – The name of the three phases are given by the natural colors viz. Red (R), Yellow (Y) and Blue (B). Thus, the phase sequence being RYB.
- **Balanced Three-Phase Supply System** – In a balanced three-phase supply system, the three phase voltages are equal in magnitude and frequency.


### Advantages of Three Phase Supply

- The three phase power has a constant magnitude while the power in single phase system is the function of supply frequency i.e. pulsates from zero to maximum value at twice the supply frequency.
- In the 3-phase system, a rotating magnetic field can be created in stationary windings.
- For the same rating, three phase machines are smaller and simpler in construction
- To transmit the same amount of power over certain distance at a given voltage, the 3-φ system requires less (or  $3/4$ ) of the weight of copper than that required by the 1-φ system.
- The voltage regulation of three phase transmission lines is better than that of 1-phase line.
- A single phase load can be supplied by a three phase system but, the converse is not true.
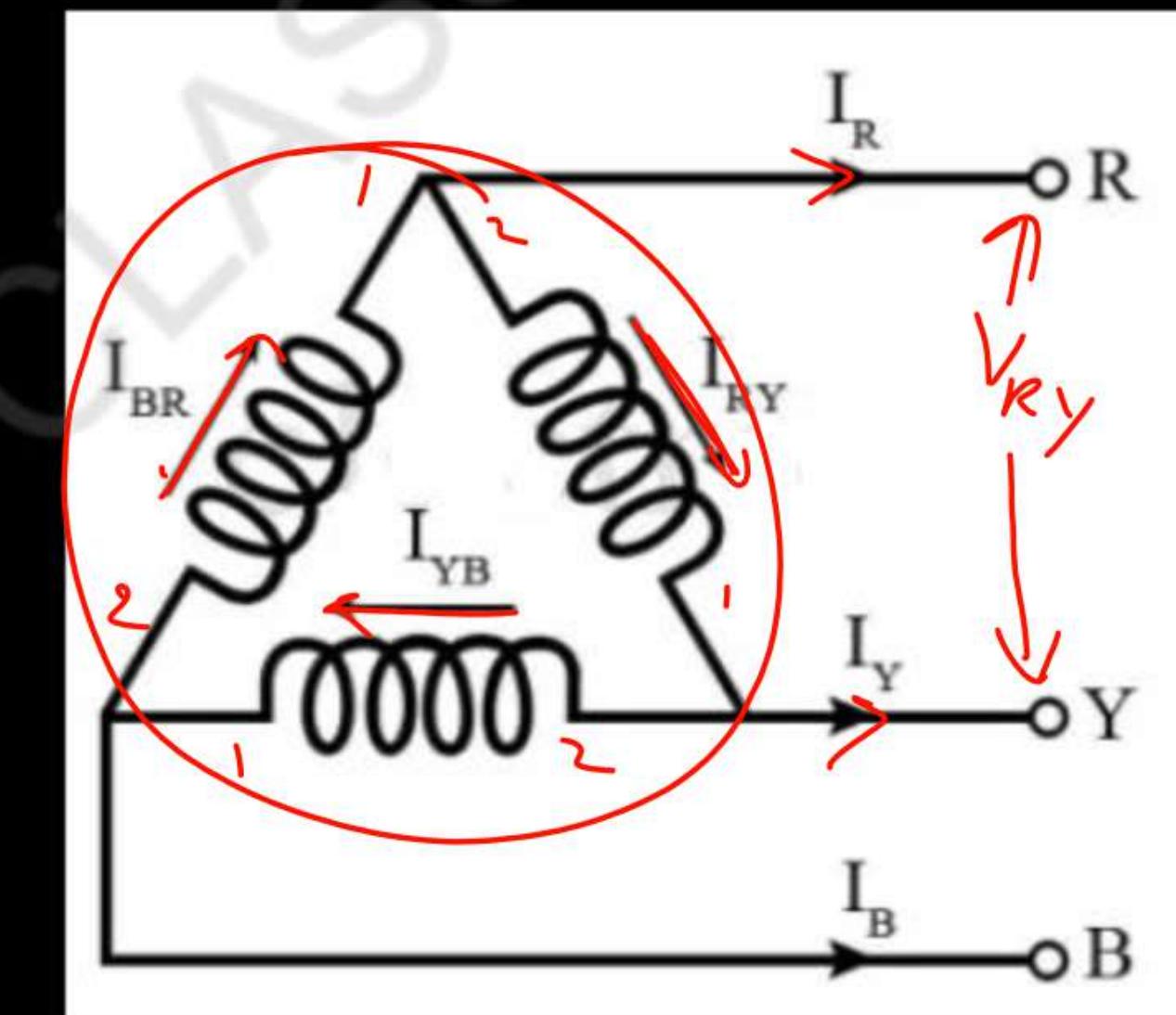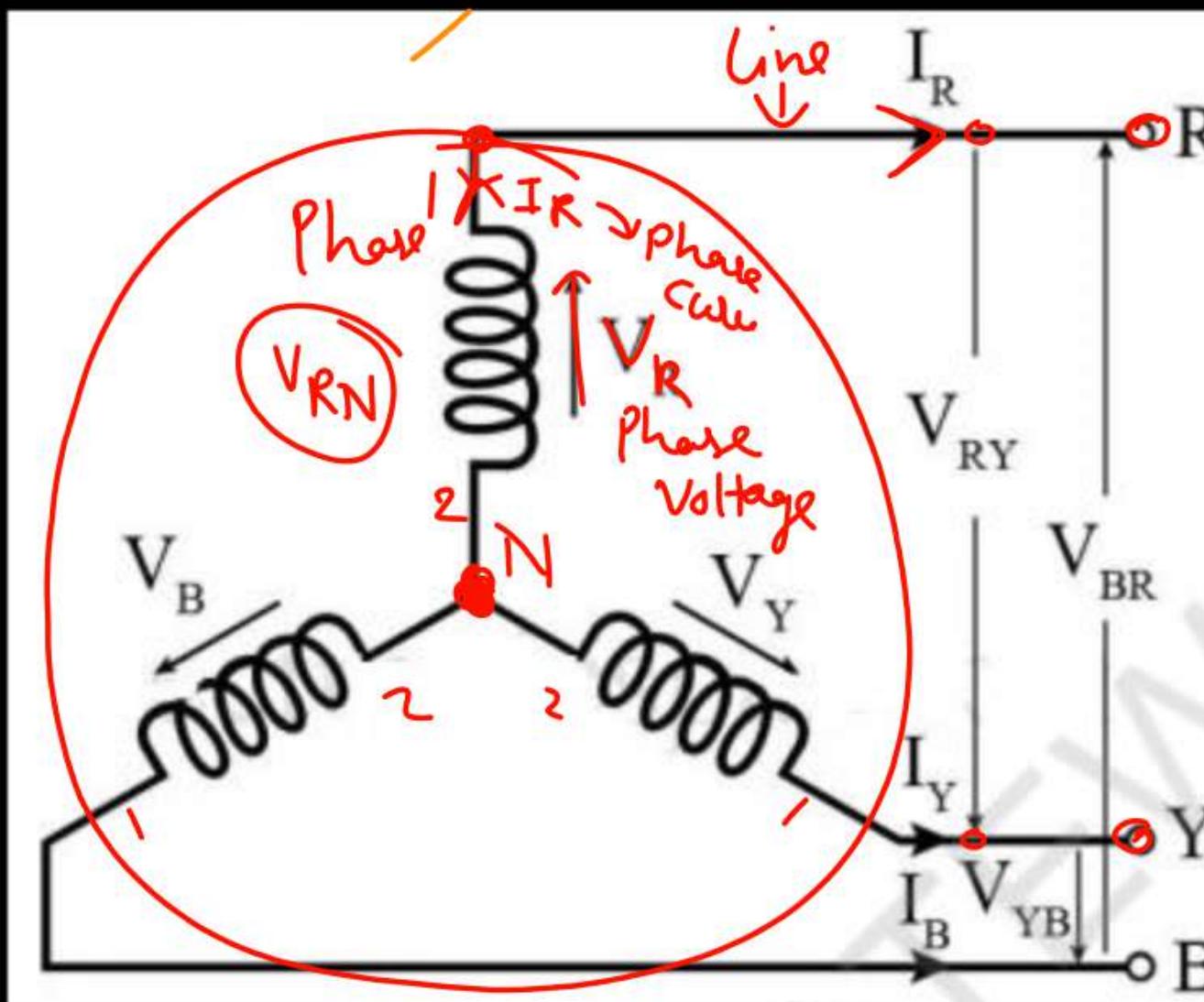
# Types of Connections (Line and Phase Values)


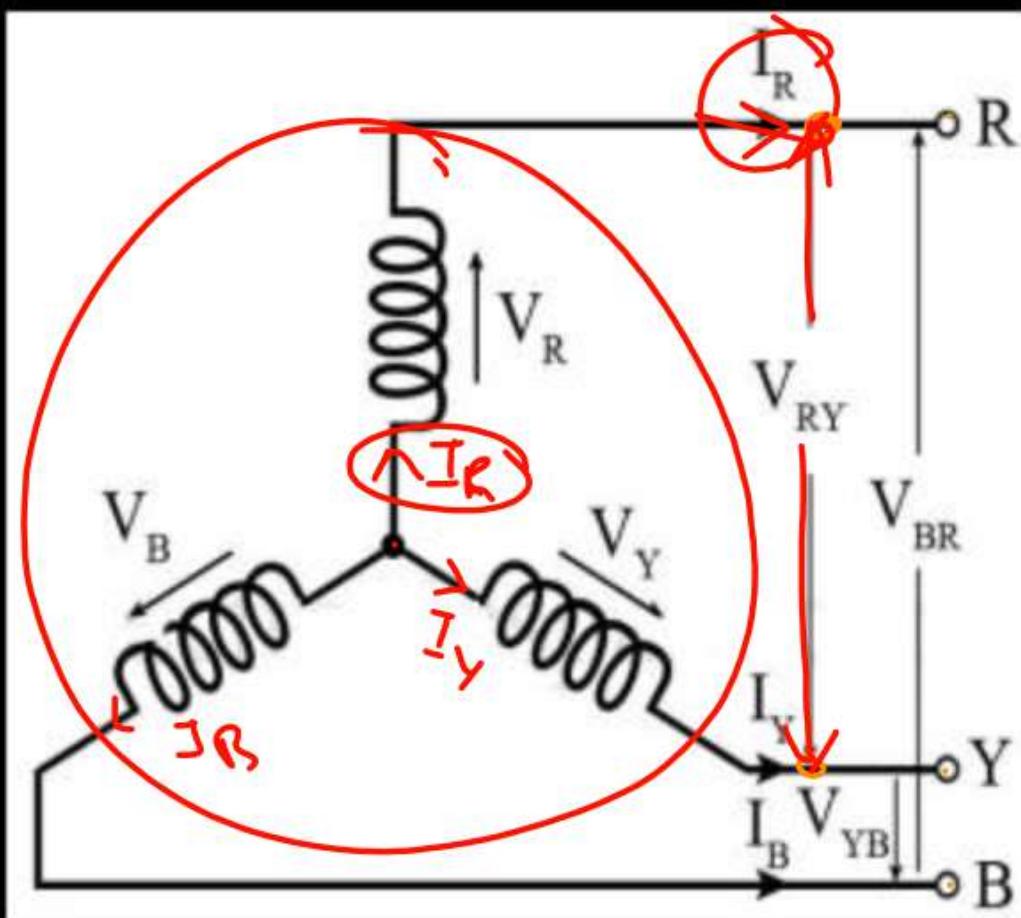
# Relation Between Line and phase Values in Star Connection



$$\text{Power} = 3V_{ph}\bar{V}_{ph}\cos\phi$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L \cos\phi$$

$$P = \sqrt{3} V_L I_L \cos\phi$$

$$Q = \sqrt{3} V_L I_L \sin\phi$$

In case of  $\Delta$  Connection

$$I_{ph} = I_L$$

$$\text{Line Voltage } V_L = V_{RY} = V_{YB} = V_{BR}$$


$$V_{ph} = V_{RNY} = V_{YN} = V_{BN}$$

$$\begin{aligned} V_{RY} &= V_{RN} + V_{NY} \\ &= V_{RN} - V_{YN} \\ &= V_R - V_Y \end{aligned}$$

$$V_{RY} = \sqrt{V_R^2 + V_Y^2 + 2V_R V_Y \cos 60^\circ}$$


$$= \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph} V_{ph} \cos 60^\circ}$$

$$S = \sqrt{3} V_{ph} I_L$$

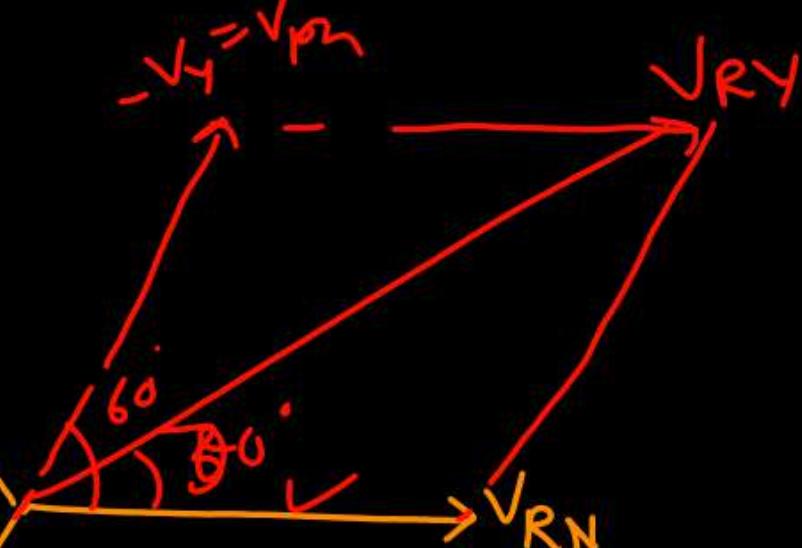

$$V_L = \sqrt{3} V_{ph}$$
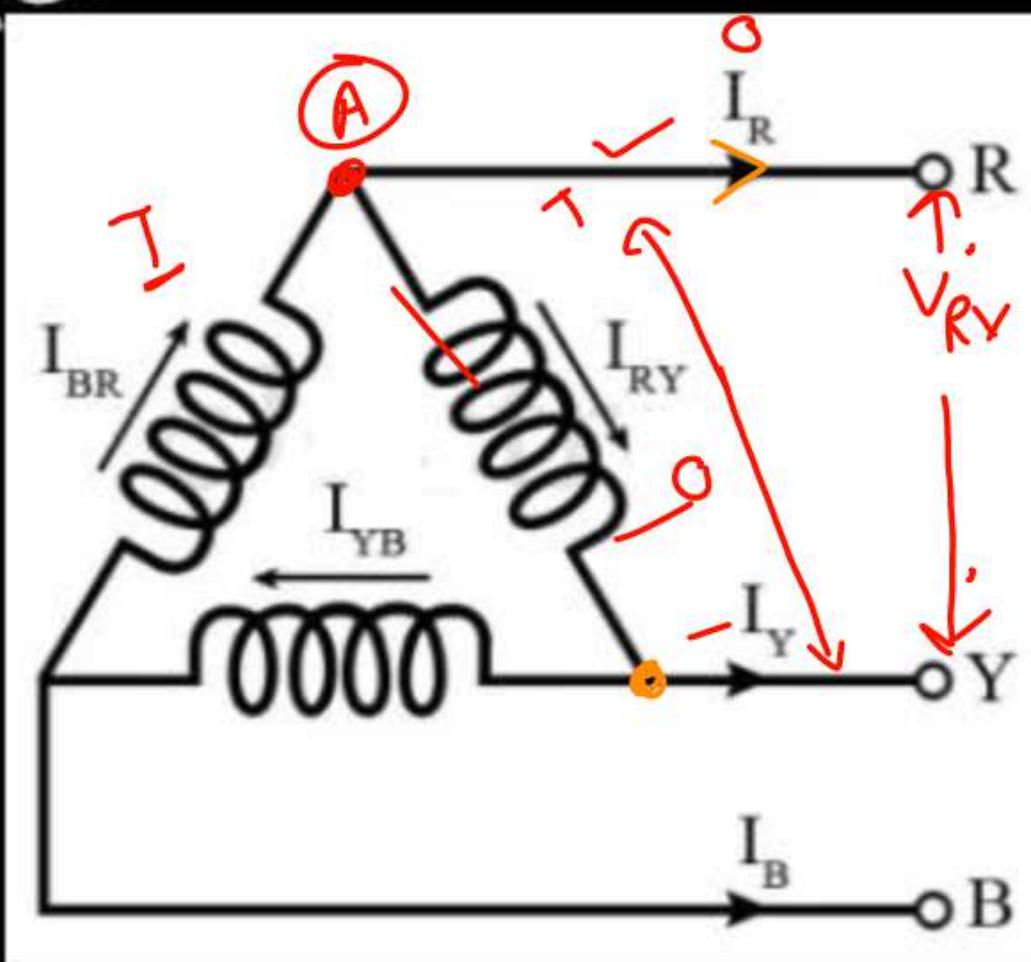
# Relation Between Line and phase Values in Delta Connection




$$P = 3V_p I_p \cos\phi$$

$$P = 3V_L \frac{I_L}{\sqrt{3}} \cos\phi$$

$$= \sqrt{3} V_L I_L \cos\phi$$

$$\boxed{I_L = \sqrt{3} I_p}$$

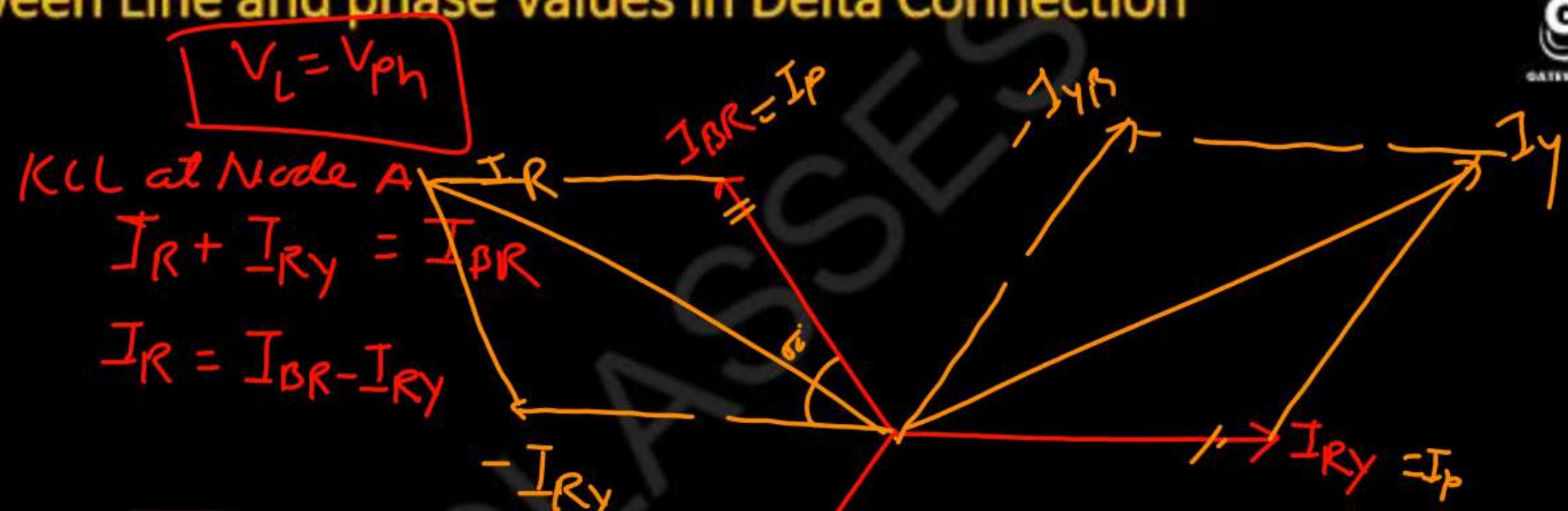

$$I_R = \sqrt{|I_{BR}|^2 + |I_{Ry}|^2 + 2|I_{BR}| |I_{Ry}| \cos 60^\circ}$$

$$I_L = \sqrt{I_p^2 + I_p^2 + 2I_p^2 \times \frac{1}{2}}$$

$$I_{YB} = I_p$$

$$I_y = I_{Ry} - I_{YB}$$

$$\begin{aligned} P &= \sqrt{3} V_L I_L \cos \phi \\ &= 3 V_{ph} I_{ph} \cos \phi \quad \text{kW} \end{aligned}$$


$$\begin{aligned} Q &= \sqrt{3} V_L I_L \sin \phi \\ &= 3 V_{ph} I_{ph} \sin \phi \quad \text{kVAR} \end{aligned}$$

$$\begin{aligned} S &= \sqrt{3} V_L I_L \\ &= 3 V_{ph} I_{ph} \quad \text{kVA} \end{aligned}$$

Various methods are used for measurement of three phase power in three phase circuits on the basis of number of wattmeters used. We have three methods to discuss:


- Single wattmeter method.
- Two wattmeters method
- Three wattmeters method

$$P = 3 W_1$$

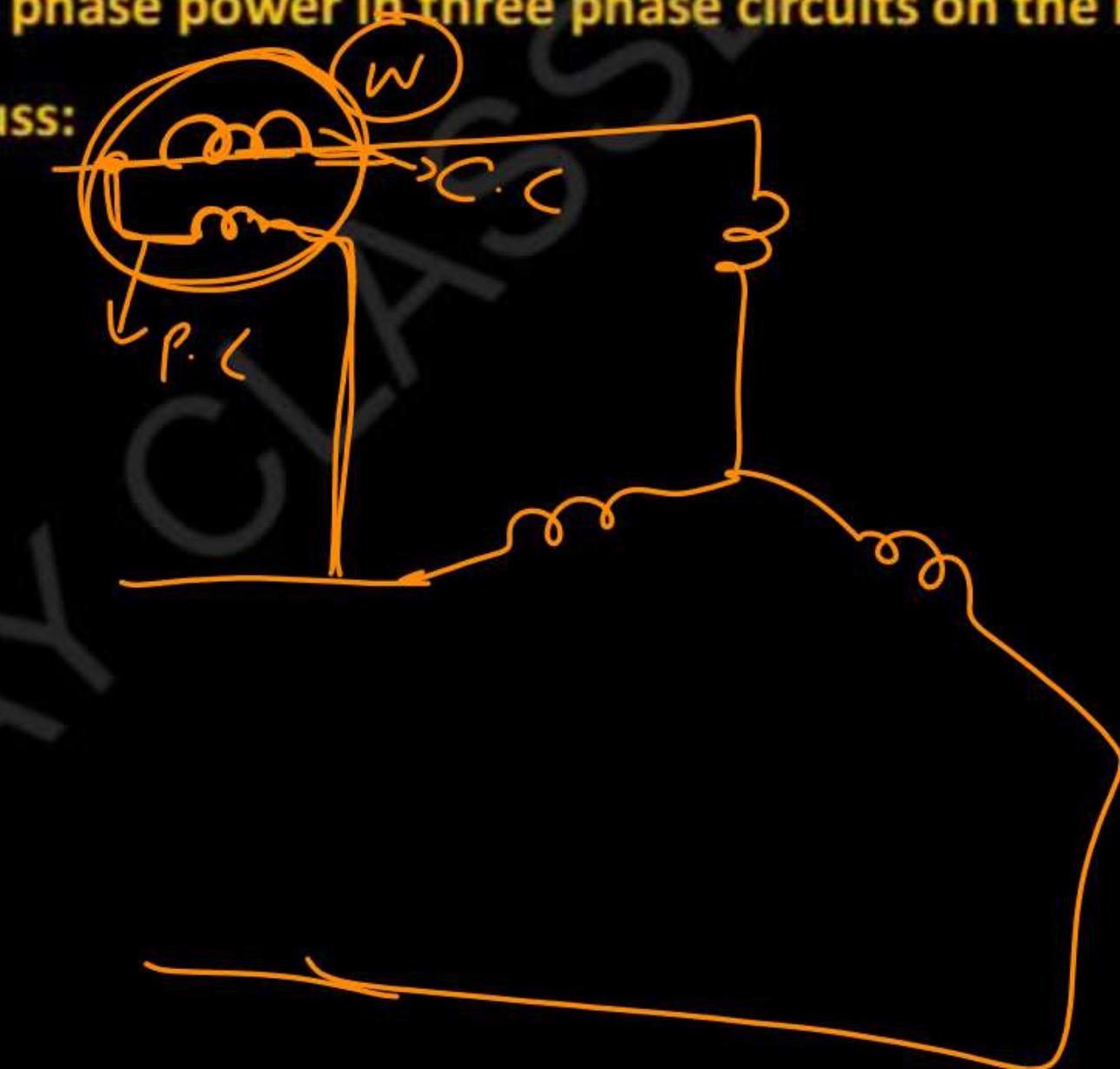


## Three wattmeter method

$$P = W_1 + W_2 + W_3$$

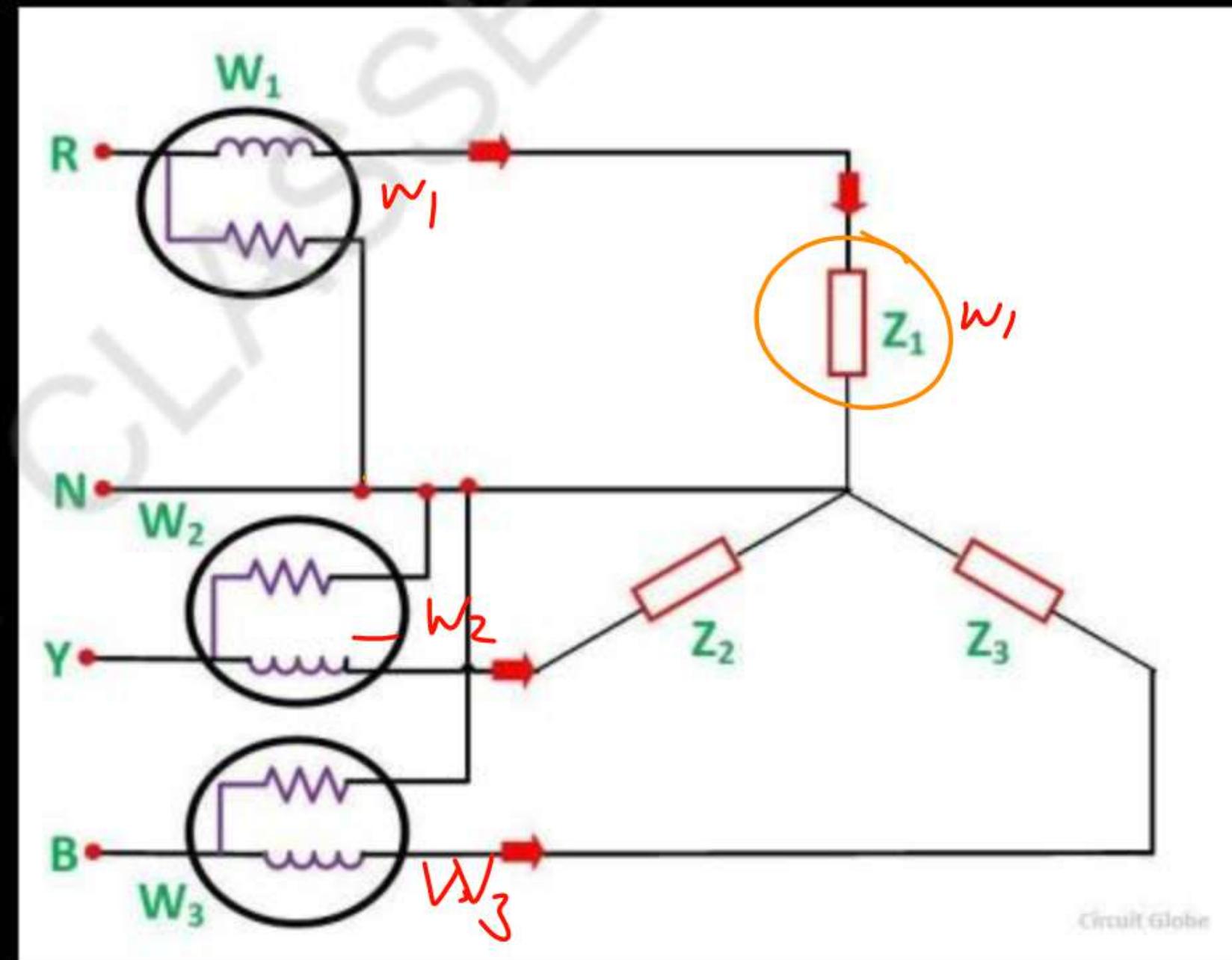

# Two Wattmeter Method (Star Connection)

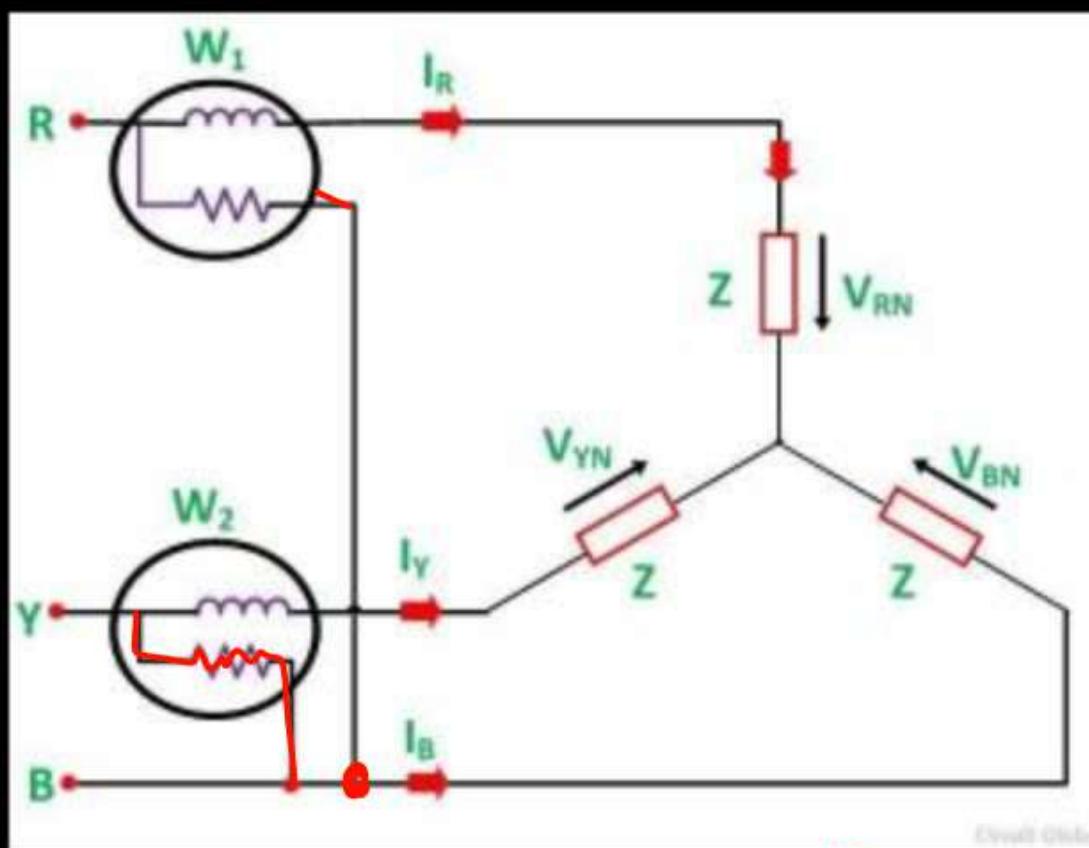

$$W_1 \rightarrow I_R, V_{RB}, \theta = 30^\circ - \phi$$

$$W_2 \rightarrow I_Y, V_{YB}, \theta = 30^\circ + \phi$$

$$V_{RB} = V_R - V_B$$

$$V_{YB} = V_Y - V_B$$

$$W_1 = V_{RB} I_R (\cos(30^\circ - \phi))$$


$$W_2 = V_{YB} I_Y (\cos(30^\circ + \phi))$$

$$W_1 + W_2 = V_L I_L [(\cos(30^\circ - \phi) + \cos(30^\circ + \phi))]$$

~~$$= V_L I_L [2 \cos 30^\circ \cos \phi]$$~~

~~$$= V_L I_L [\cos 30^\circ + \sin 30^\circ \sin \phi + \cos 30^\circ \cos \phi - \sin 30^\circ \sin \phi]$$~~
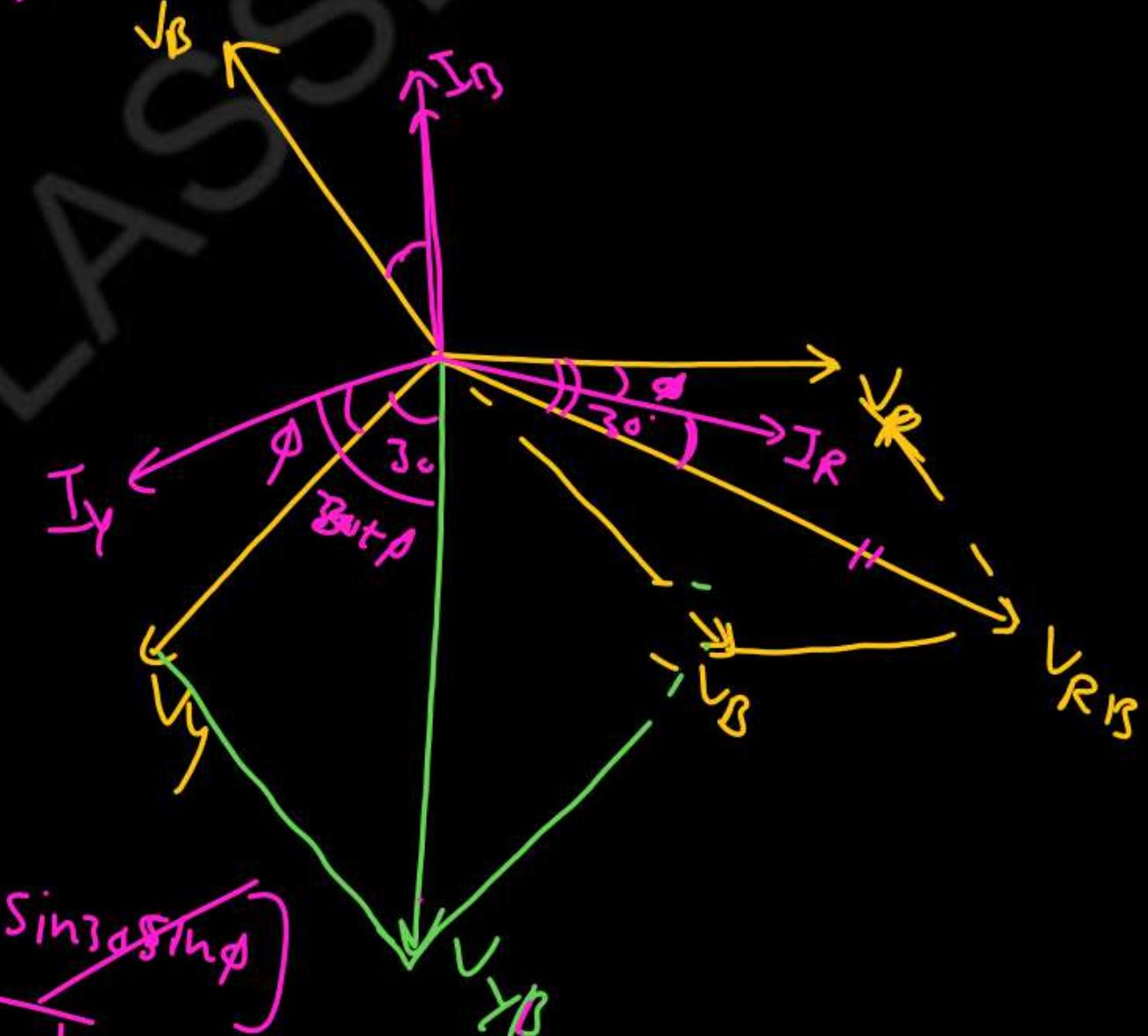
$$= \sqrt{3} V_L I_L \cos \phi = P_{3-\phi}$$



## Two Wattmeter Method (Delta Connection )

Self

# Power Factor calculation by Two Wattmeter Method

$$W_1 = V_L I_L \cos(30 - \phi)$$

$$W_2 = V_L I_L \cos(30 + \phi)$$

$$W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi$$

$$W_1 - W_2 = V_L I_L [\cos(30 - \phi) - \cos(30 + \phi)]$$

$$= V_L I_L [2 \sin 30 \sin \phi] \quad (\downarrow \text{Previous formula})$$

$$\boxed{W_1 - W_2 = V_L I_L \frac{1}{2} \sin \phi}$$

$$\frac{W_1 + W_2}{W_1 - W_2} = \frac{\sqrt{3} V_L I_L \cos \phi}{V_L I_L \sin \phi}$$

$$\tan \phi = \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right)$$

$$\boxed{\phi = \tan^{-1} \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right)}$$

## Numerical Examples

- Ex.-27 A balanced star connected load of  $(8 + j6)$  ohm per phase is connected to a balanced 3-phase, 400 V supply. Find the line current, phase current, power factor, power and total volt-amperes. AKTU- 2021-22

$$V_L = 400\text{V}, \quad Z_{Ph} = (8 + 6j) \text{ /phase}$$

$$\text{Line Voltage } V_{Ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231$$

$$\text{Line Current } I_L = \frac{V_{Ph}}{Z_{Ph}} = \frac{400}{\sqrt{3} \times (8 + 6j)} = 23.09 \angle -36.86^\circ \text{ A}$$

$$\text{PF} = \cos \phi = \cos 36.86^\circ = 0.8$$

$$S = 3V_{Ph}I_L = 3 \times 231 \times 23.09$$

## Numerical Examples

Capa.

- Ex.-28. A balanced 3-Phase star connected load takes 30KW at a leading current of 48A from a 3-φ source of 500V, 50Hz. Find the circuit parameters per phase.

AKTU- 2021-22

$$V_L = 500 \text{ V}$$

$$V_{ph} = \frac{500}{\sqrt{3}} = 288.67 \text{ V}$$

$$Z_{ph} = \frac{V_{ph}}{I_p} = \frac{288.67}{48} = 6.01 \Omega$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$\cos \phi = \frac{P}{\sqrt{3} \times 500 \times 48} = 0.7$$

$$P = 30 \text{ kW}$$

$$I_L = 48 \text{ A}$$

$$\phi = 45^\circ 57'$$

$$Z = 6.01 \angle -45.57^\circ$$

$$Z = \underbrace{4.33}_R - \underbrace{4.165j}_{X_L}$$

$$R - jX_L$$

- Ex.-29. A balanced delta connected load of  $(12 + j 9) \Omega$ / phase is connected to 3- phase 400 V supply. Calculate line current, power factor and power drawn by it.

AKTU- 2014-15

Self

- Ex.-30. A 3-φ, 500 V motor has a power factor of 0.4 (lagging). Two wattmeters are connected to measure the input and show the total input power to be 30 kW. Find out the readings of each wattmeter AKTU- 2021-22

$$\text{Cos } \phi = 0.4 \quad , \quad V_L = \text{sin } \phi \\ P = 30 \text{ kW} = W_1 + W_2 \quad \text{--- (1)}$$

$$\tan \phi = \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right)$$

$$W_1 - W_2 = \frac{\tan \phi}{\sqrt{3}} (W_1 + W_2) \quad \text{--- (2)}$$

Solve Eqn (1) & (2)

$$W_1 = ?$$

$$W_2 = ?$$

- Ex.-31. A Star Connected three phase load has a resistance of 8 ohm and an inductive reactance of 6 ohm . It is fed from 400 V 3 phase supply. Determine line current , power factor active and reactive power. Draw phasor diagram showing phase and line voltages and currents. If power is measured by two wattmeter method what will be the reading of both wattmeters. AKTU- 2004-05

$$Z = 8 + 6j, V_L = 400V \Rightarrow$$

$$V_{ph} = \frac{400}{\sqrt{3}} = 231V$$

$$I_L = \bar{I}_{ph} = \frac{V_{ph}}{Z} = \frac{231}{(8+6j)} = 23.09 \angle -36.86^\circ$$

$$W_1 = V_L I_L \cos(30^\circ - \phi)$$

$$W_2 = V_L I_L \cos(30^\circ + \phi)$$

- Ex.-32. A balanced star connected inductive load is connected to a **400V, 50Hz** supply. Two wattmeters are used to measure power indicate **8000W** and **4000W** respectively. Determine (i) Line Current (ii) Impedance of each phase (iii) power factor (iv) Resistance and inductance of each phase AKTU- 2009-10

$$\omega_1 + \omega_2 = 8\omega\omega + 4\omega\omega = 12\omega\omega$$

$$\omega_1 - \omega_2 = 4\omega\omega$$

$$\tan\phi = \sqrt{3} \left( \frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right)$$

$$= \sqrt{3} \left( \frac{4\omega\omega}{12\omega\omega} \right)$$

$$\tan\phi = 0.577$$

$$\cos\phi = \omega_1 (\tan^{-1}(0.577))$$

$$= 0.86$$

$$P = \sqrt{3} V_L I_L \cos\phi, \quad V_L = 4\omega\omega$$

$$I_L = \frac{P}{\sqrt{3} V_L \cos\phi} = I_{ph}$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = Z \angle 0$$

$$= R + jX$$

For more Subject/pdf Notes  
Download **Gateway Classes** Application  
From Google Play store

Link in Description

# Thank You



# Gateway Classes



**Full Courses Available in App**

**AKTU B.Tech I- Year : All Branches**

**AKTU B.Tech II- Year**

- Branches :**
- 1. CS IT & Allied**
  - 2. EC & Allied**
  - 3. ME & Allied**
  - 4. EE & Allied**

**Download App Now**



**Download App**

**Full  
Courses**

- ✓ V. Lectures**
- ✓ Pdf Notes**
- ✓ AKTU PYQs**
- ✓ DPP**